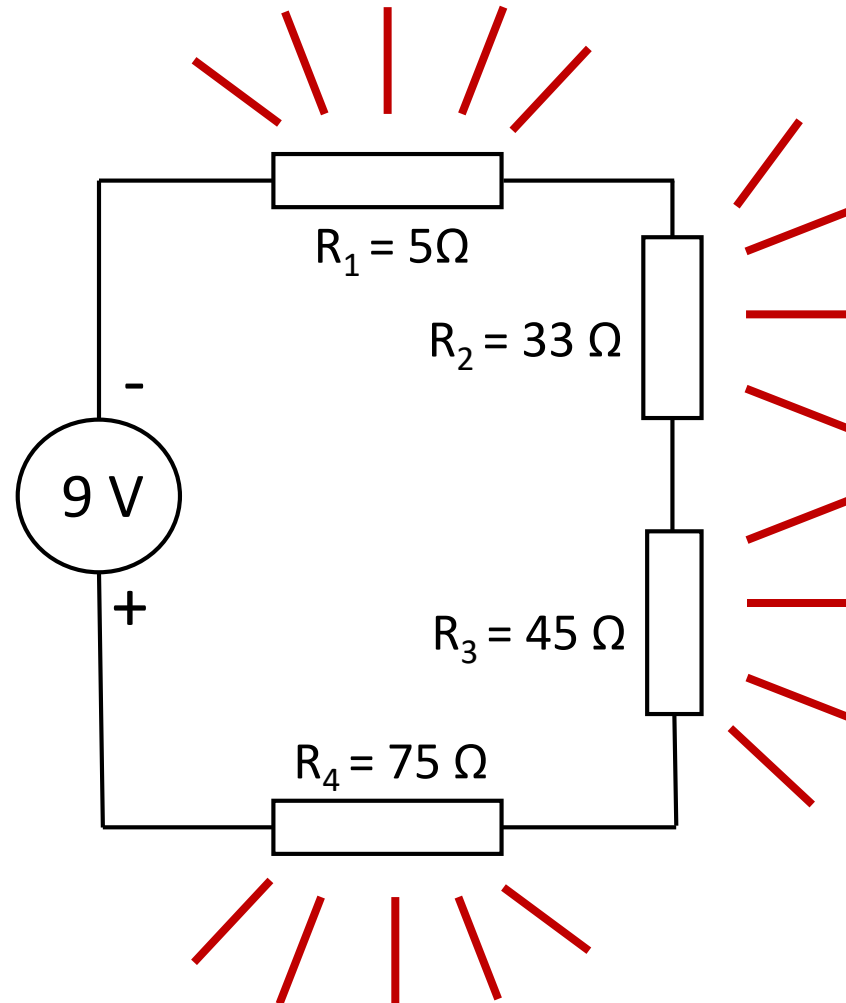


1.

Find electric power in all resistors in the circuit below.




1.

Find electric power in all resistors in the circuit below.

SOLUTION

$$i = \frac{V}{R_1 + R_2 + R_3 + R_4} = 57 \text{ mA} \text{ / Ohm's law, the current in the circuit}$$

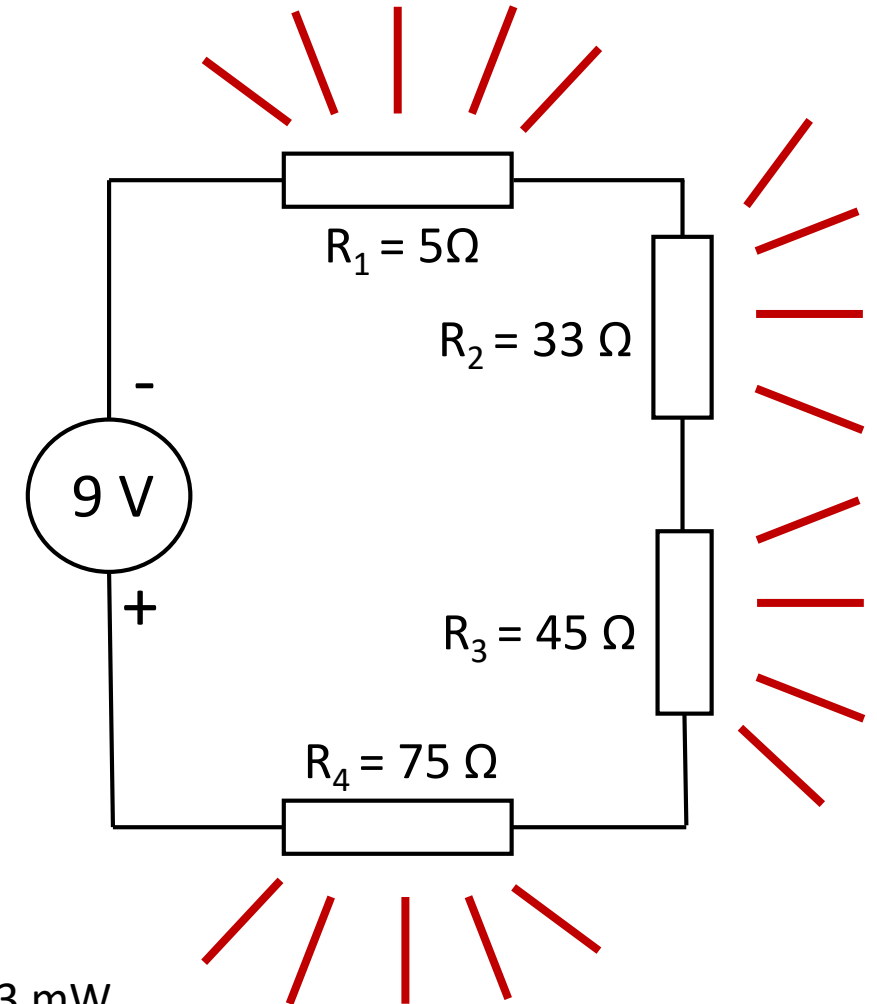
$$P = i \cdot V = i^2 R \text{ / Electric power in the resistor}$$



Answer: $P_1 = 16 \text{ mW}$; $P_2 = 107 \text{ mW}$; $P_3 = 146 \text{ mW}$; $P_4 = 243 \text{ mW}$.

2.

Find powers on all elements

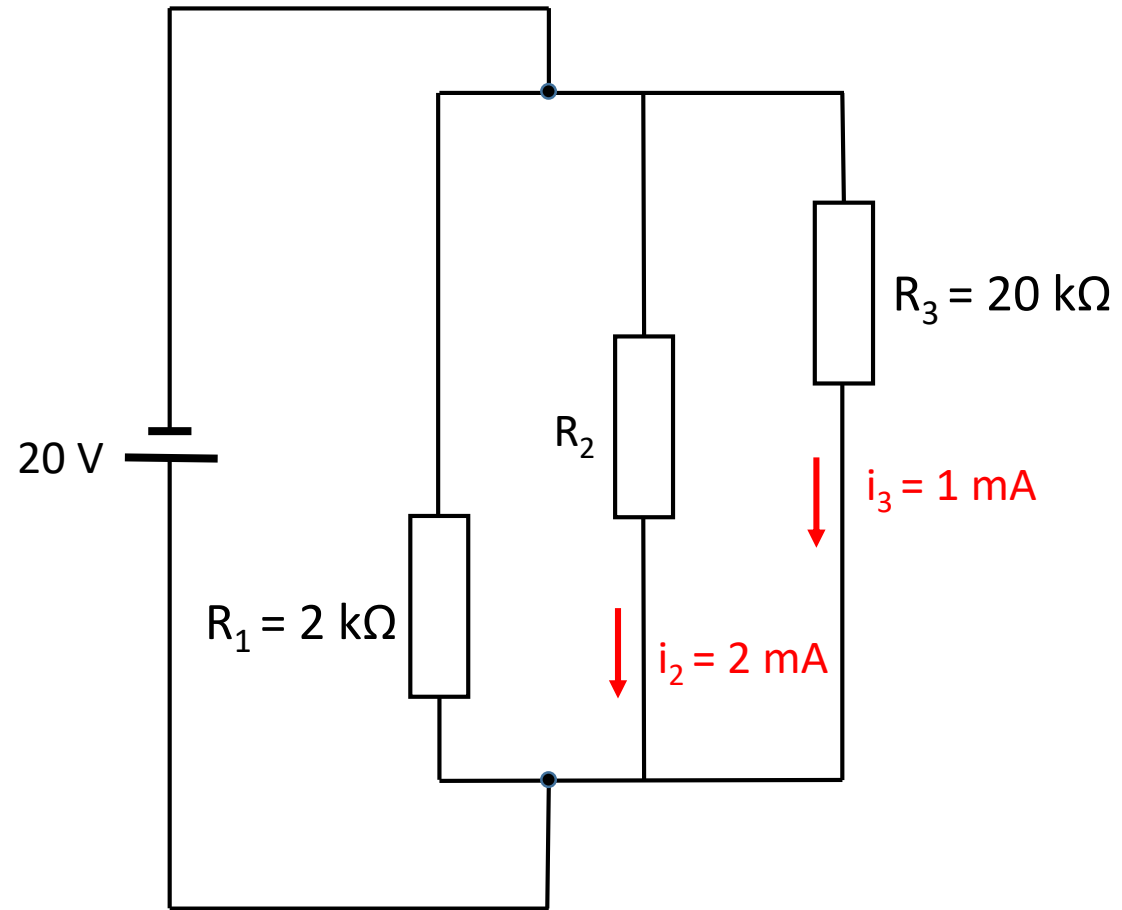

2.

Find powers on all elements

SOLUTION

$$R_2 = \frac{V}{i_2} = 10 \text{ k}\Omega$$

/ Ohm's law


$$i_1 = \frac{V}{R_1} = 10 \text{ mA}$$

$$P_1 = \frac{V^2}{R_1} = 0.2 \text{ W}$$

$$P_2 = V \cdot i_2 = 0.04 \text{ W}$$

$$P_3 = V \cdot i_3 = 0.02 \text{ W}$$


$$P = P_1 + P_2 + P_3 = 0.26 \text{ W}$$

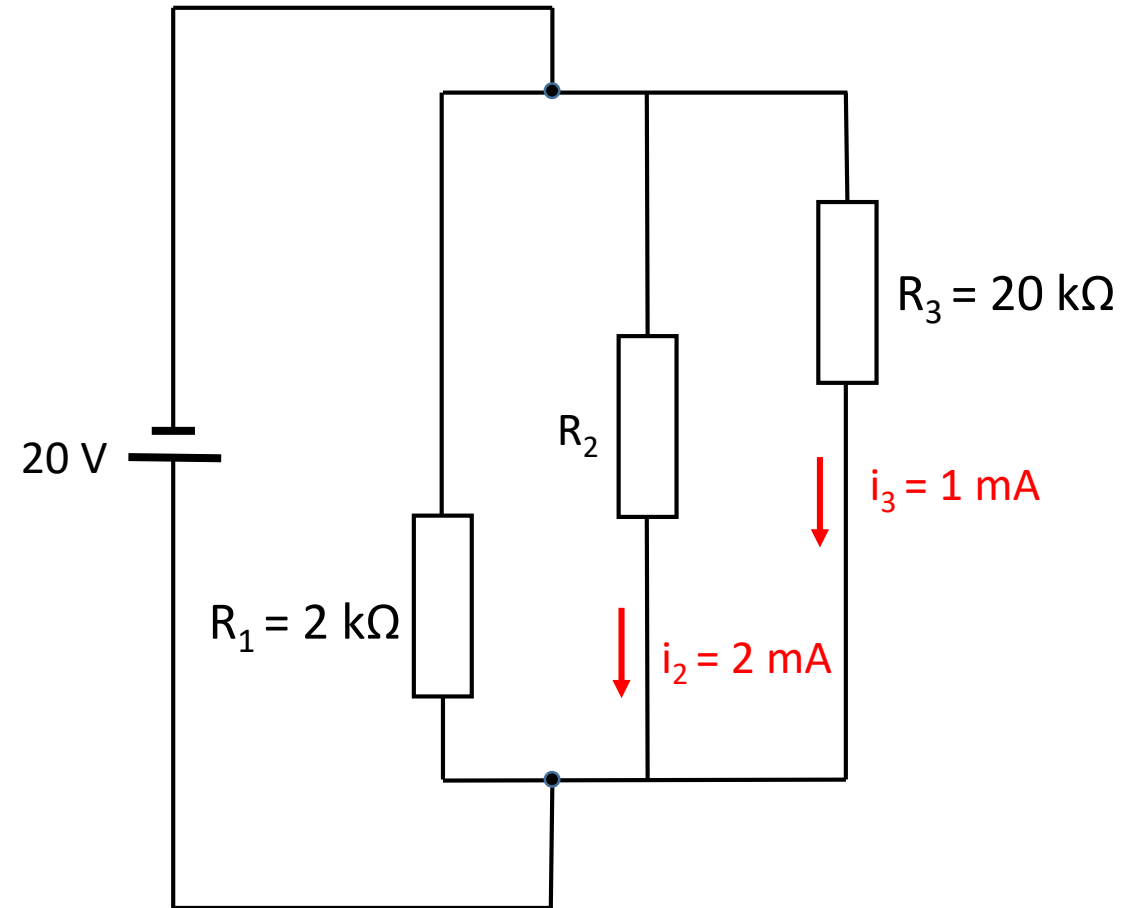

Answer: $P_1 = 0.2 \text{ W}$; $P_2 = 0.04 \text{ W}$; $P_3 = 0.01 \text{ W}$. Total power is 0.26 W


3.

Find the equivalent resistance

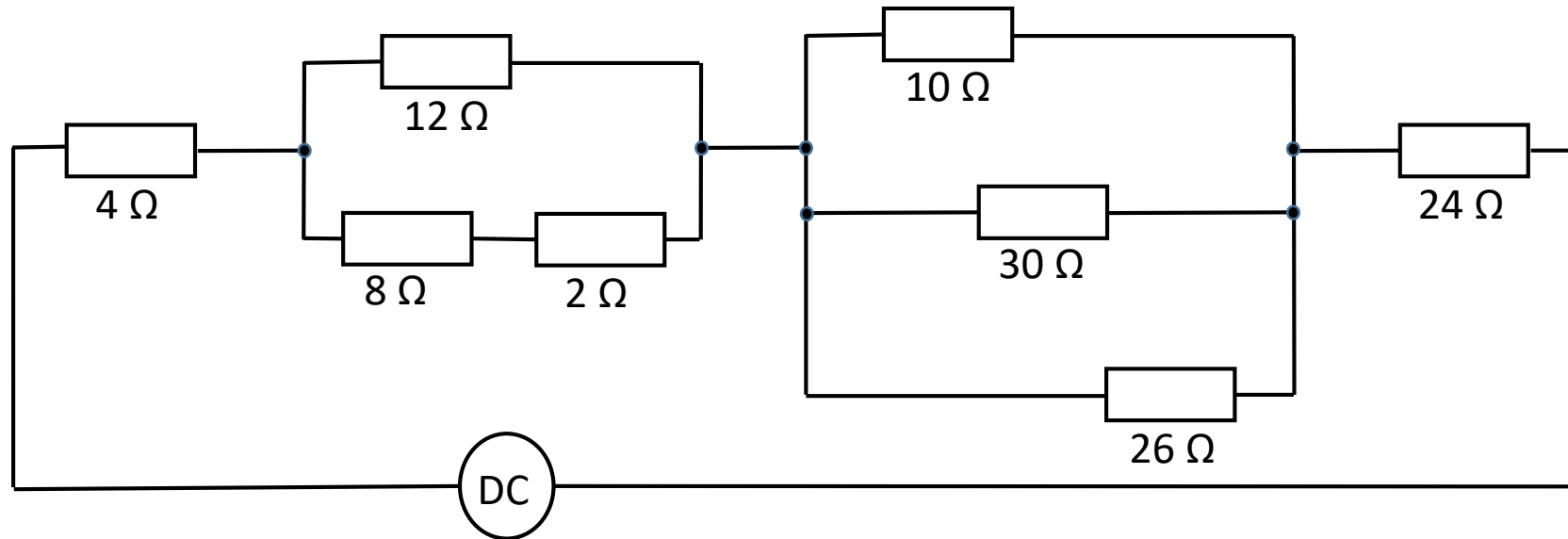


3.

Find the equivalent resistance


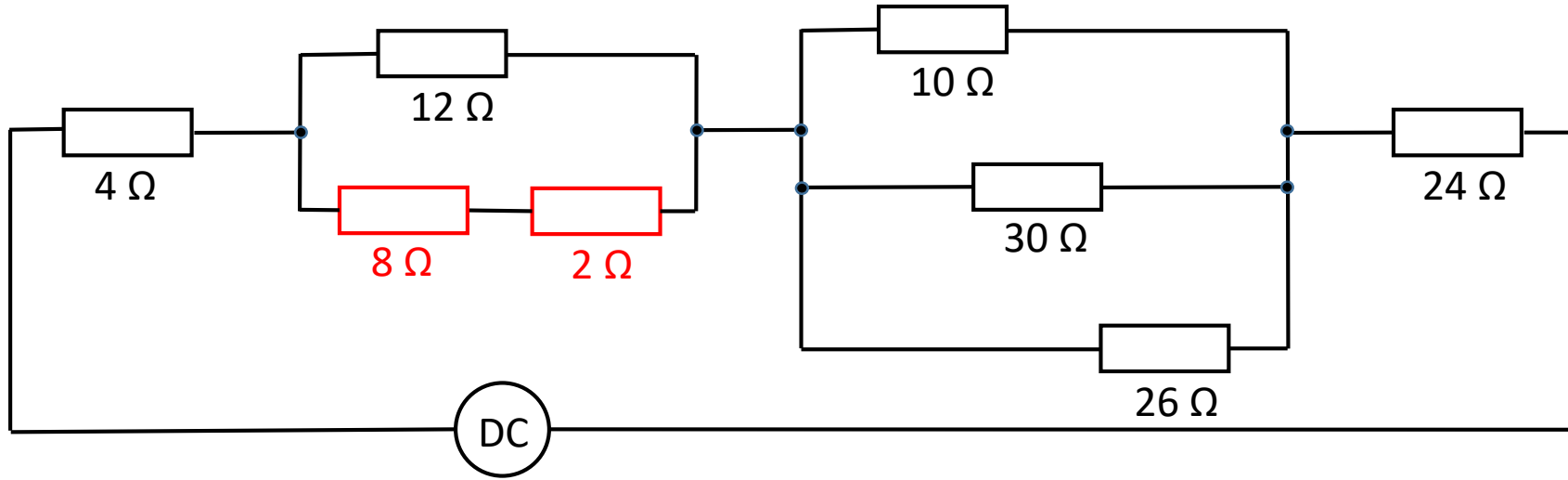


SOLUTION

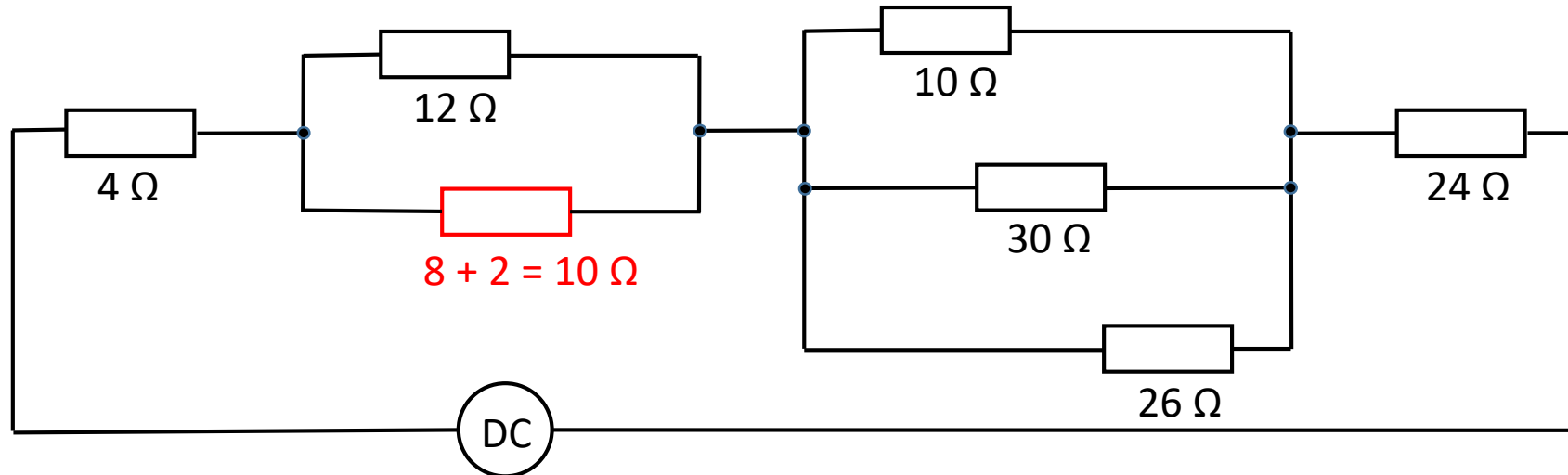

3.



Find the equivalent resistance

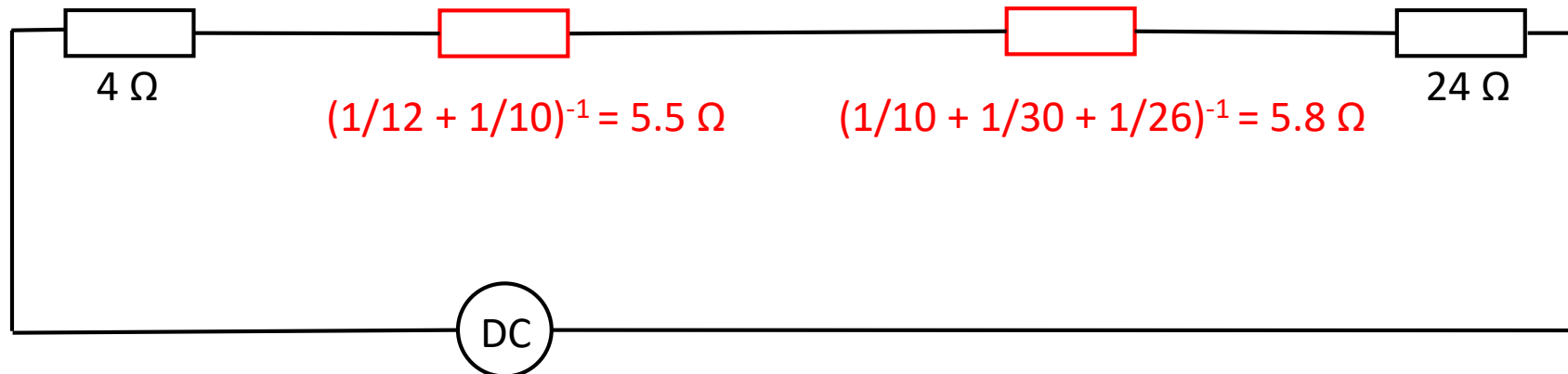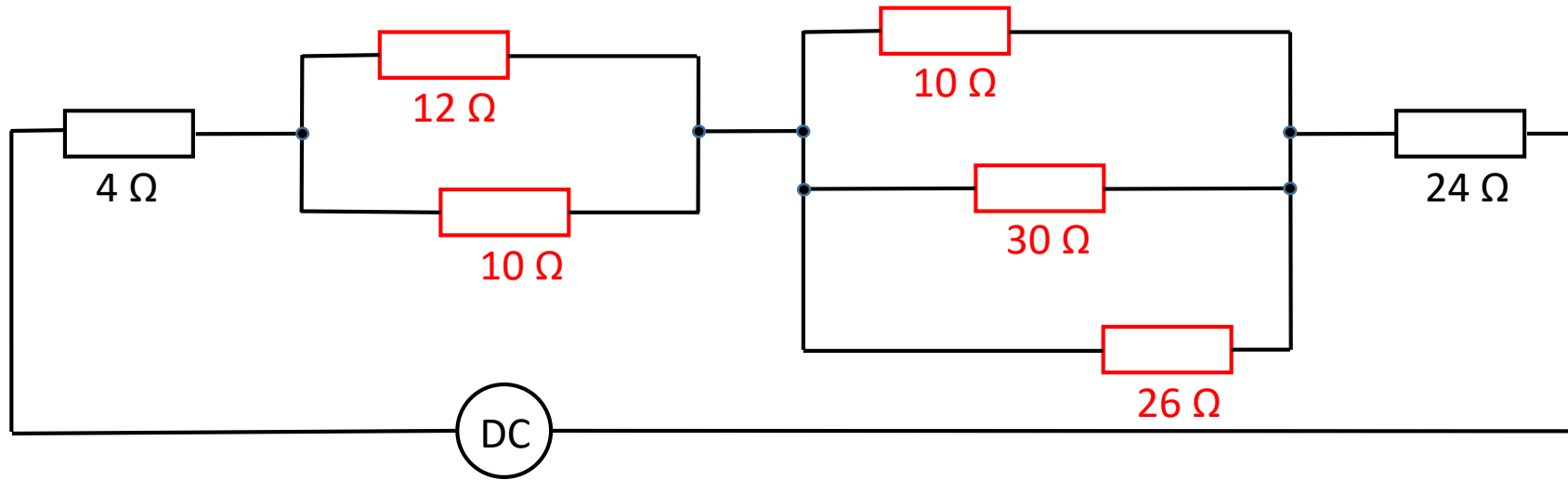

SOLUTION

3.


Find the equivalent resistance

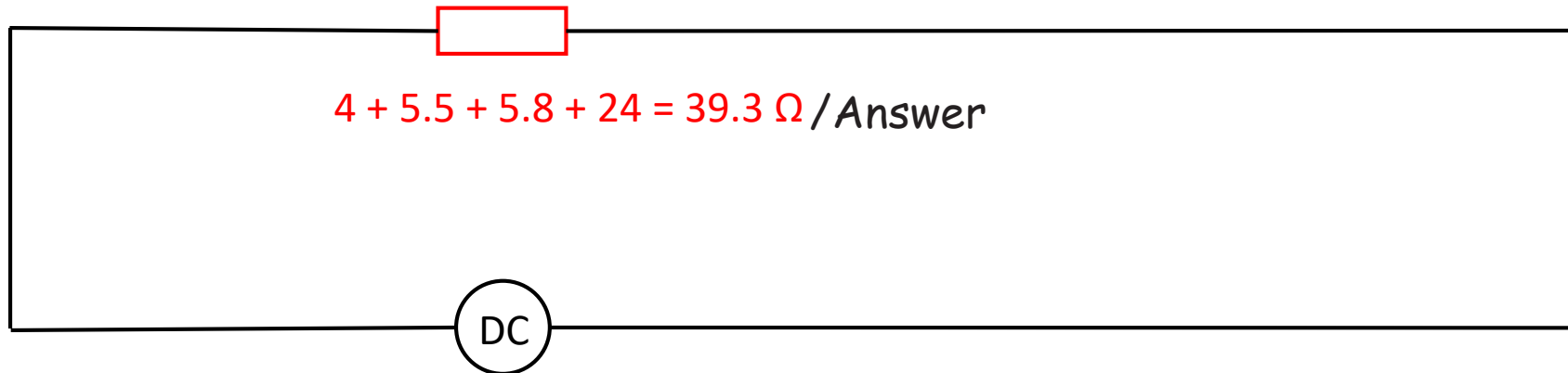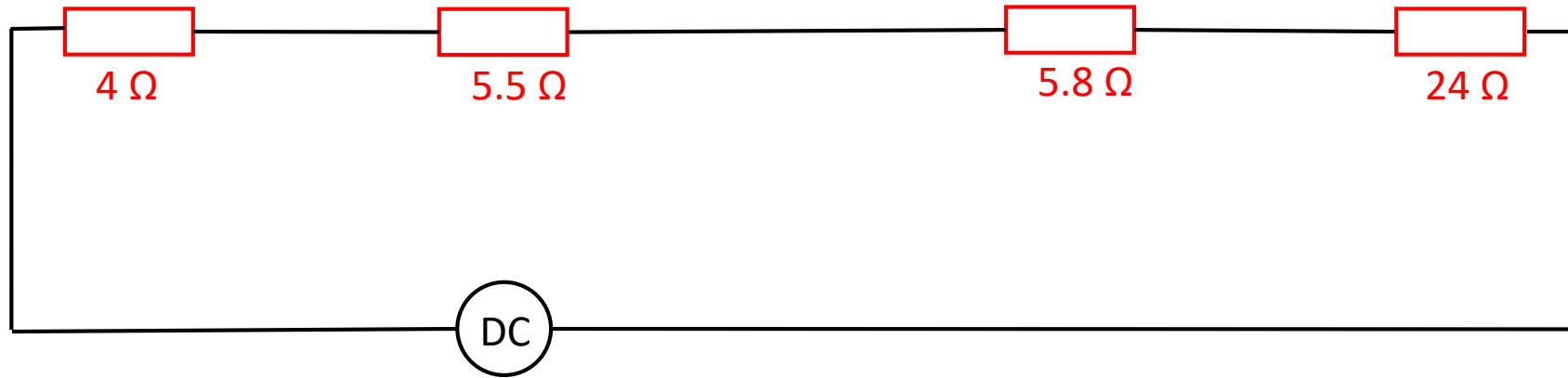

SOLUTION

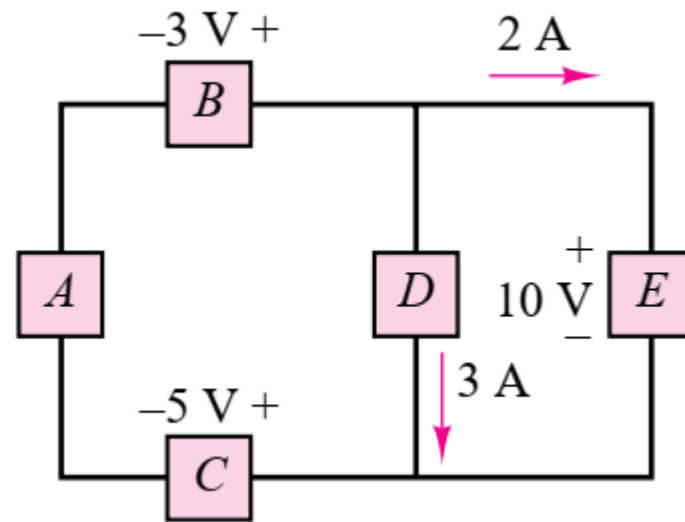4.

Determine which components are absorbing power and which are delivering power




4.

By KCL, the current through element B is 5 A, to the right.

$$-v_a - 3 + 10 + 5 = 0 \quad / \text{By KVL}$$

$$v_a = 12 \text{ V}$$

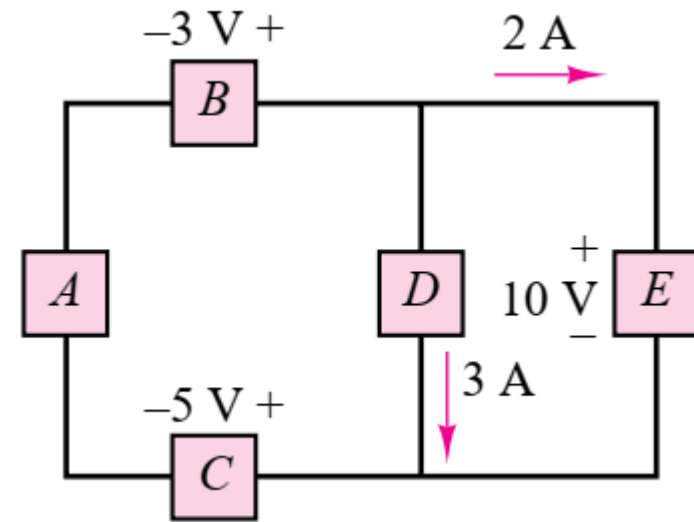

Answer:

A supplies $(12 \text{ V})(5 \text{ A}) = 60 \text{ W}$

B supplies $(3 \text{ V})(5 \text{ A}) = 15 \text{ W}$

C absorbs $(5 \text{ V})(5 \text{ A}) = 25 \text{ W}$

D absorbs $(10 \text{ V})(3 \text{ A}) = 30 \text{ W}$

E absorbs $(10 \text{ V})(2 \text{ A}) = 20 \text{ W}$


Total power supplied $= 60 \text{ W} + 15 \text{ W} = 75 \text{ W}$

Total power absorbed $= 25 \text{ W} + 30 \text{ W} + 20 \text{ W} = 75 \text{ W}$

Total power supplied = Total power absorbed, so conservation of power is satisfied

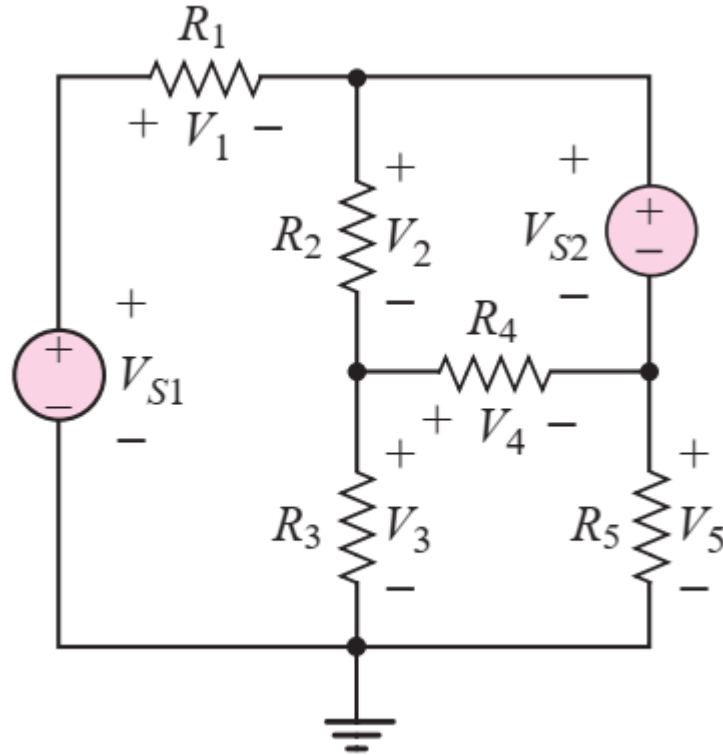5.

Use KVL to determine the unknown voltages V_1 and V_4 in the circuit.



Given:

$$V_{S1} = 12 \text{ V}$$

$$V_{S2} = -4 \text{ V}$$

$$V_2 = 2 \text{ V}$$

$$V_3 = 6 \text{ V}$$

$$V_5 = 12 \text{ V}$$

5.

Application of KVL clockwise
around each of the three meshes:

$$V_{S1} - V_1 - V_2 - V_3 = 0 \quad \text{/mesh 1}$$

$$V_2 - V_{S2} + V_4 = 0 \quad \text{/mesh 2}$$

$$V_3 - V_4 - V_5 = 0 \quad \text{/mesh 3}$$

$$12 - V_1 - 2 - 6 = 0$$


$$V_1 = 4 \text{ V} \quad \text{/Answer}$$

$$2 - (-4) + V_4 = 0$$

$$V_4 = -6 \text{ V} \quad \text{/Answer}$$

$$6 - (-6) - V_5 = 0$$

$$V_5 = 12 \text{ V}$$

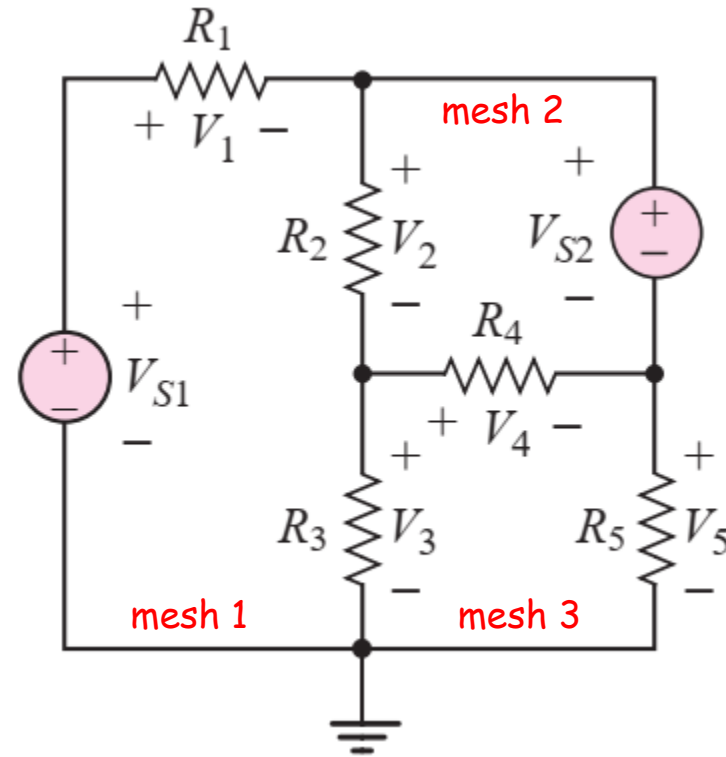

Given:

$$V_{S1} = 12 \text{ V}$$

$$V_{S2} = -4 \text{ V}$$


$$V_2 = 2 \text{ V}$$

$$V_3 = 6 \text{ V}$$


$$V_5 = 12 \text{ V}$$

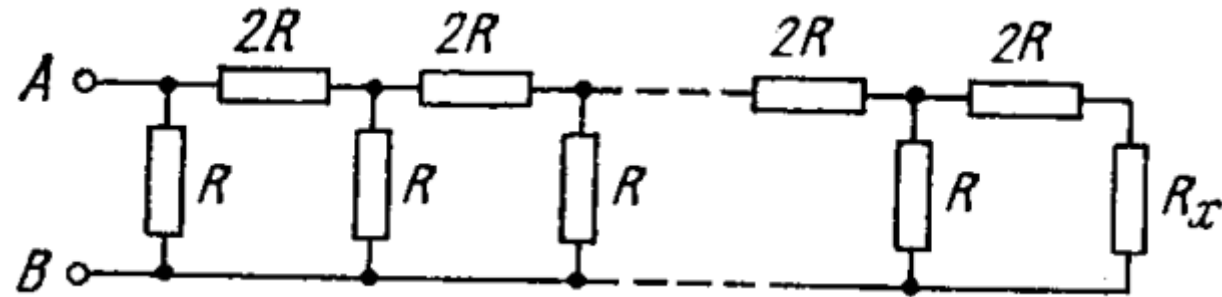6.

At what size of the resistor R_x the equivalent resistance between points A and B is independent on the number of meshes?



6.

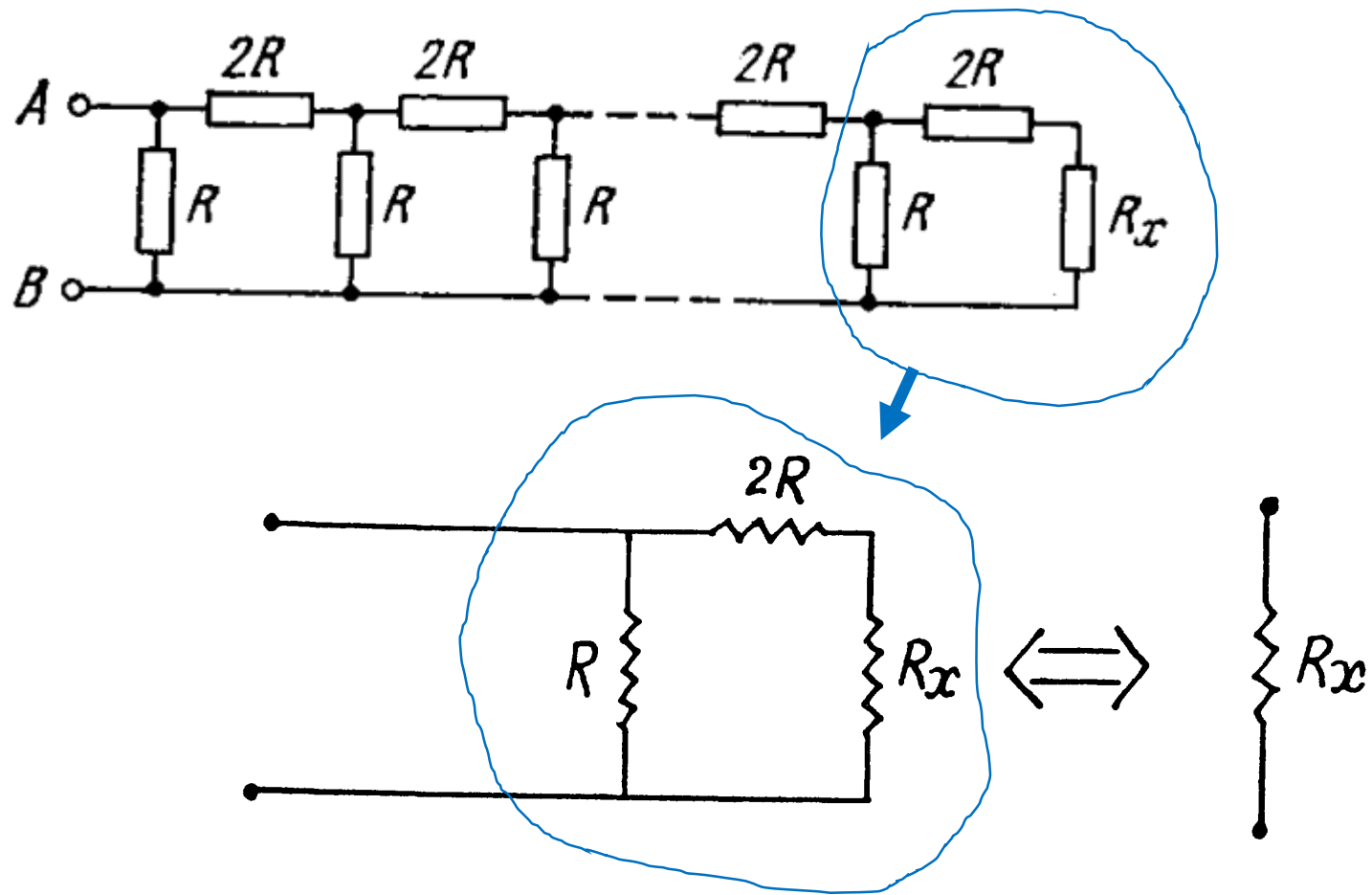

$$R_x = \frac{(R_x + 2R) R}{R_x + 2R + R}$$

$$R_x^2 + 2R R_x - 2R^2 = 0$$

On solving and rejecting the negative root of the quadratic equation, we have,

$$R_x = R(\sqrt{3} - 1) / \text{Answer}$$