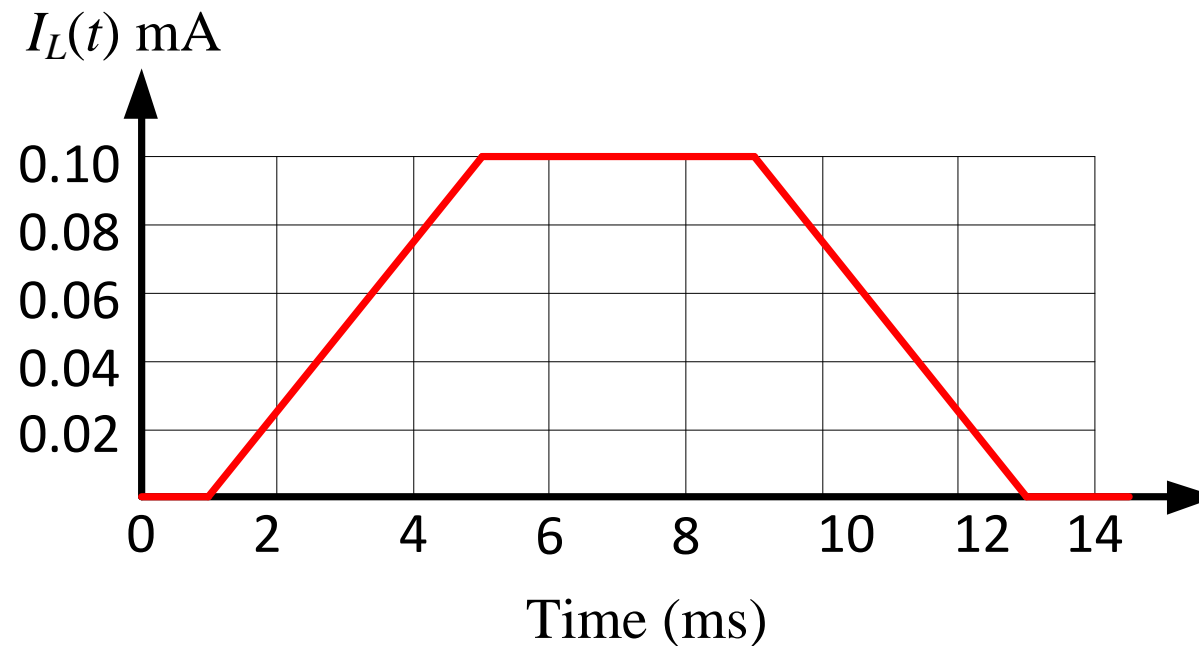


1.


For ideal inductor calculate the voltage across the inductor ( $L = 1000$  mH) from knowledge of its current.

$$i_L(t) = \begin{cases} 0 \text{ mA} & t < 1 \text{ ms} \\ -\frac{0.1}{4} + \frac{0.1}{4}t \text{ mA} & 1 \leq t \leq 5 \text{ ms} \\ 0.1 \text{ mA} & 5 \leq t \leq 9 \text{ ms} \\ 13 \times \frac{0.1}{4} - \frac{0.1}{4}t \text{ mA} & 9 \leq t \leq 13 \text{ ms} \\ 0 \text{ mA} & t > 13 \text{ ms} \end{cases}$$



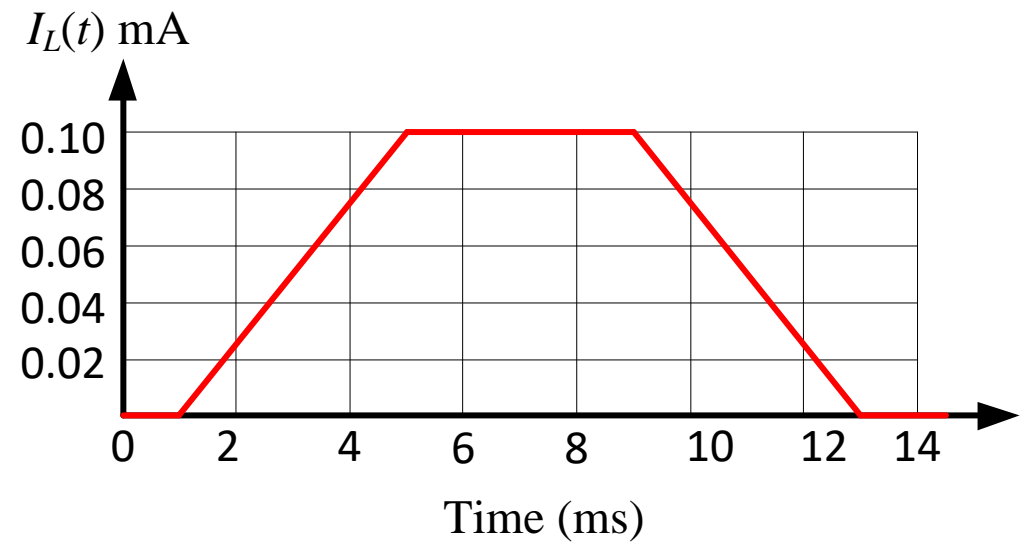
1.

$$i_L(t) = \begin{cases} 0 \text{ mA} & t < 1 \text{ ms} \\ -\frac{0.1}{4} + \frac{0.1}{4}t \text{ mA} & 1 \leq t \leq 5 \text{ ms} \\ 0.1 \text{ mA} & 5 \leq t \leq 9 \text{ ms} \\ 13 \times \frac{0.1}{4} - \frac{0.1}{4}t \text{ mA} & 9 \leq t \leq 13 \text{ ms} \\ 0 \text{ mA} & t > 13 \text{ ms} \end{cases}$$




$$v_L(t) = L \frac{di_L}{dt}$$

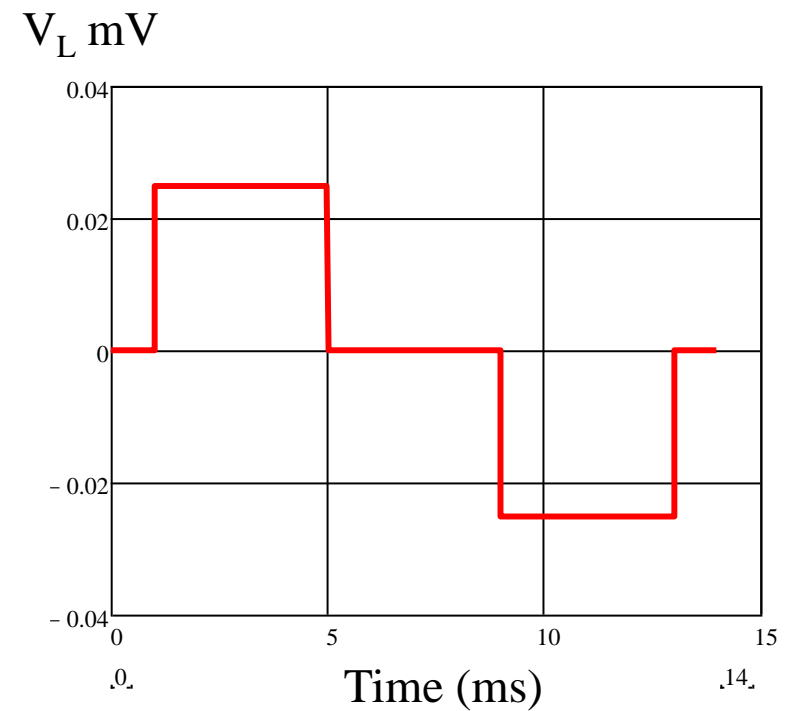Answer:  $V_L(t) = \begin{cases} 0 & \text{if } t \leq 1 \text{ ms} \\ 0.025 & \text{if } 1 < t \leq 5 \text{ ms} \\ 0 & \text{if } 5 < t \leq 9 \text{ ms} \\ -0.025 & \text{if } 9 < t \leq 13 \text{ ms} \\ 0 & \text{otherwise} \end{cases}$



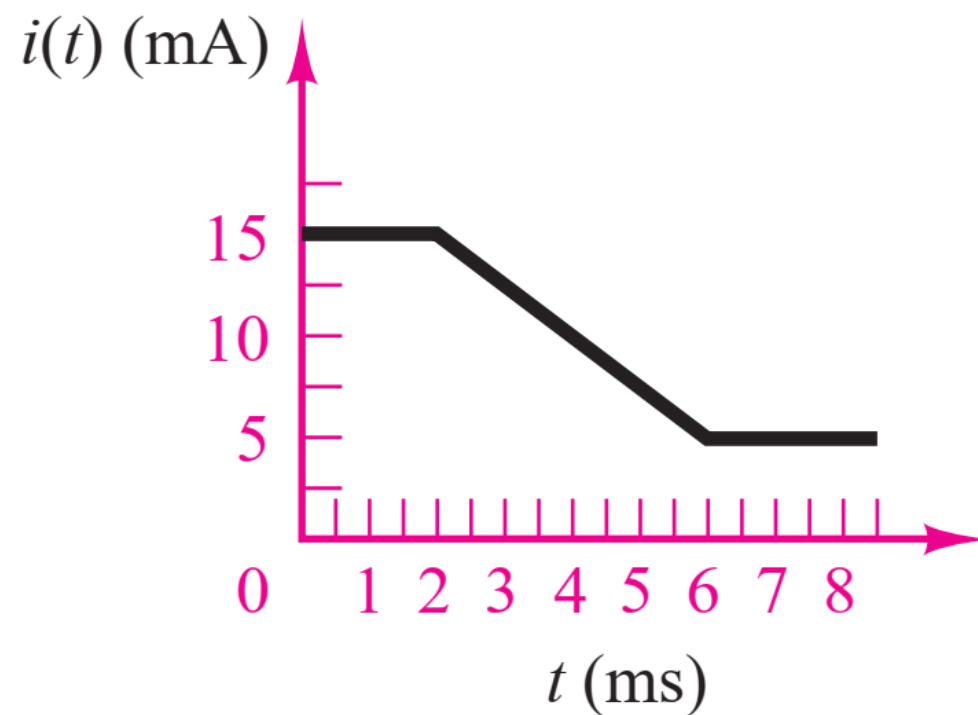2.

Calculate and plot the inductor energy and power for a 50-mH inductor subject to the current waveform shown below. What is the energy stored at  $t = 3$  ms? Assume  $i(-\infty) = 0$ .



2.

Calculate and plot the inductor energy and power for a 50-mH inductor subject to the current waveform shown below. What is the energy stored at  $t = 3$  ms? Assume  $i(-\infty) = 0$ .

$$I(t) := \begin{cases} 15 & \text{if } 0 \leq t < 2 \\ \frac{-10}{4} \cdot t + 20 & \text{if } 2 \leq t < 6 \\ 5 & \text{if } 6 \leq t \end{cases}$$



$$V(t) := \begin{cases} 0 & \text{if } 0 \leq t < 2 \\ \frac{-10}{4} & \text{if } 2 \leq t < 6 \\ 0 & \text{if } 6 \leq t \end{cases}$$



$$W(t) = (1/2) \cdot L \cdot I(t)^2$$

$$W(3 \text{ ms}) = 3.91 \mu\text{J}$$






$$P(t) = I(t) \cdot V(t)$$

$$V(t) = L \cdot \left( \frac{d}{dt} I(t) \right)$$

$$W(t) = \frac{1}{2} \cdot 50 \cdot 10^{-3} \cdot I(t)^2$$

$$P(t) = I(t) \cdot V(t)$$

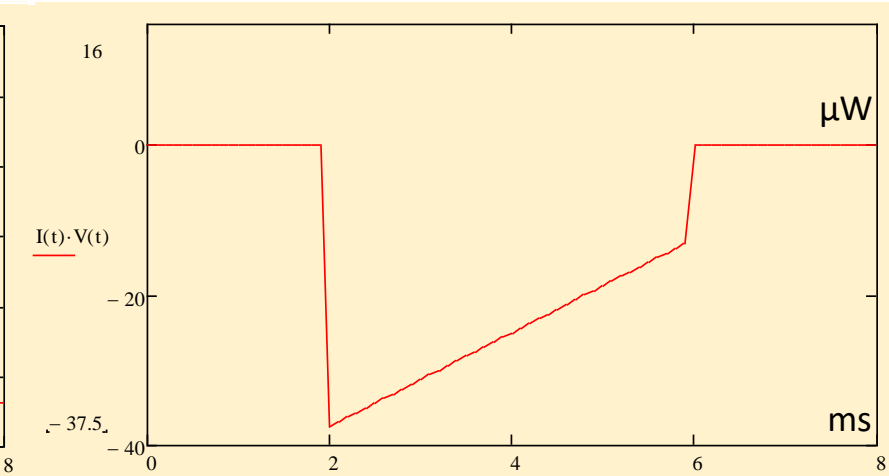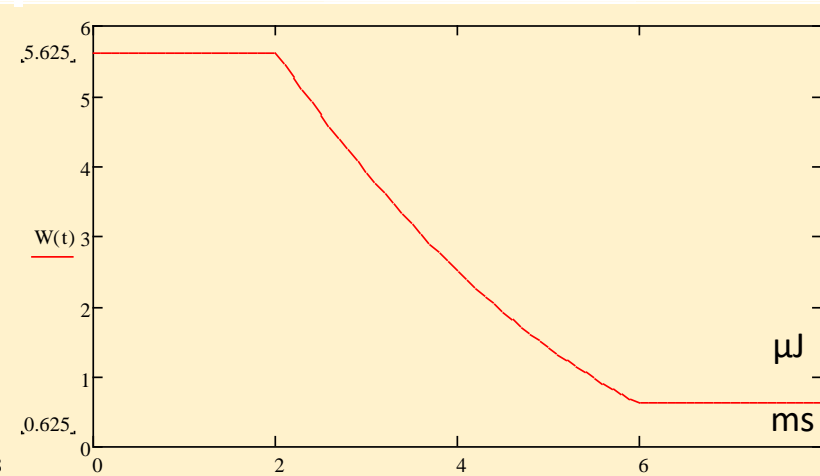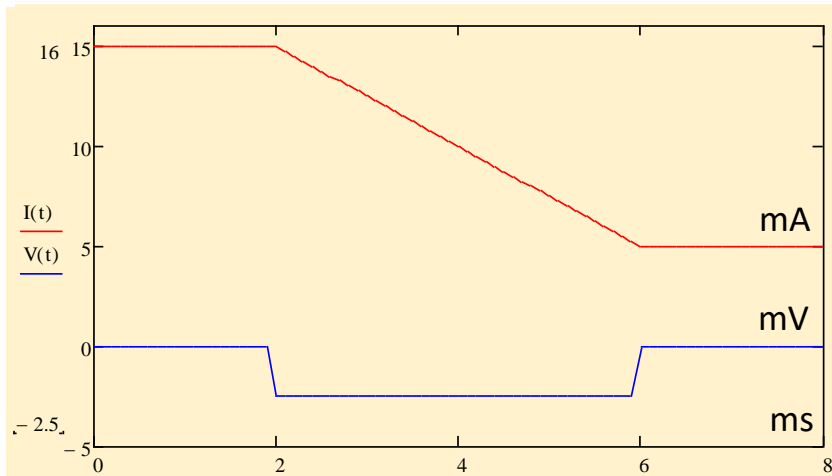


3.

The voltage across a 200-mH inductor is given by the expression

$$u(t) = (1 - 3t)e^{-3t} \text{ mV} \quad t \geq 0$$

$$u(t) = 0 \text{ mV} \quad t < 0$$

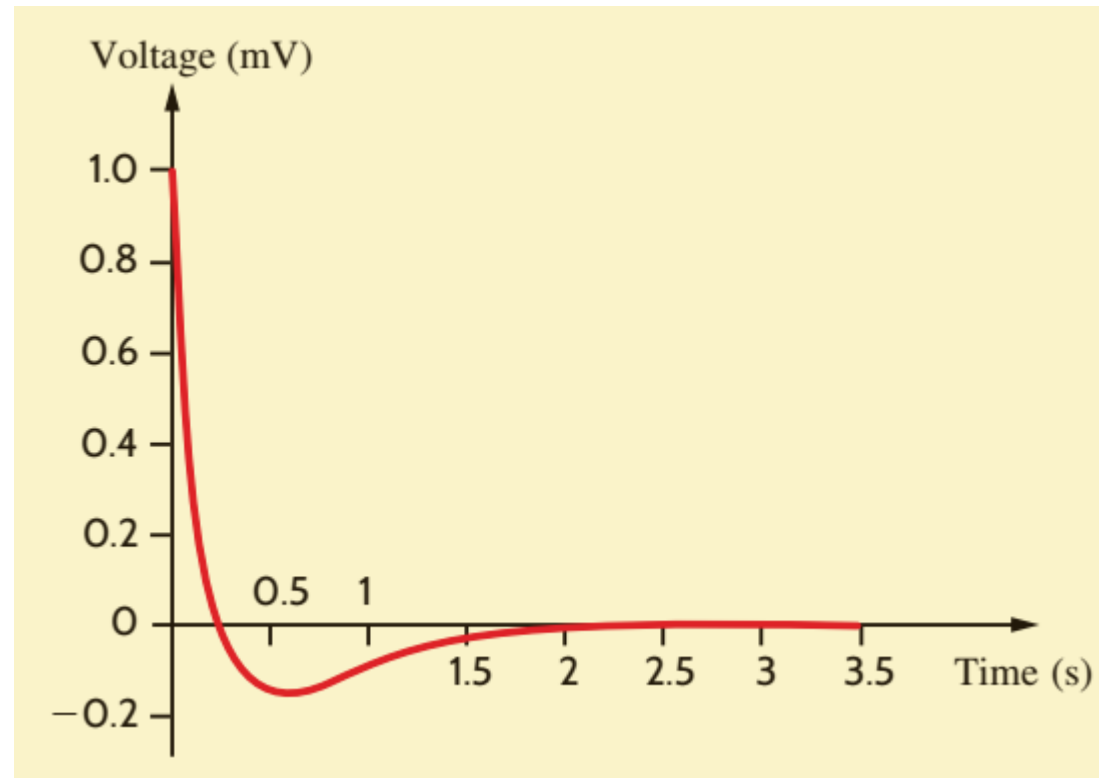Find the waveforms for the current, energy, and power



3.

The voltage across a 200-mH inductor is given by the expression

$$u(t) = (1 - 3t)e^{-3t} \text{ mV} \quad t \geq 0$$

$$u(t) = 0 \text{ mV} \quad t < 0$$

Current (mA):


$$i(t) = \frac{1}{L} \cdot \int_0^t v(x) dx = \frac{10^3}{200} \cdot \int_0^t (1 - 3x) \cdot e^{-3x} dx = 5 \cdot t \cdot e^{-3t}$$

Power ( $\mu\text{W}$ ):


$$P(t) = i(t) \cdot v(t) = 5 \cdot t \cdot (1 - 3t) \cdot e^{-6t}$$

Energy ( $\mu\text{J}$ ):

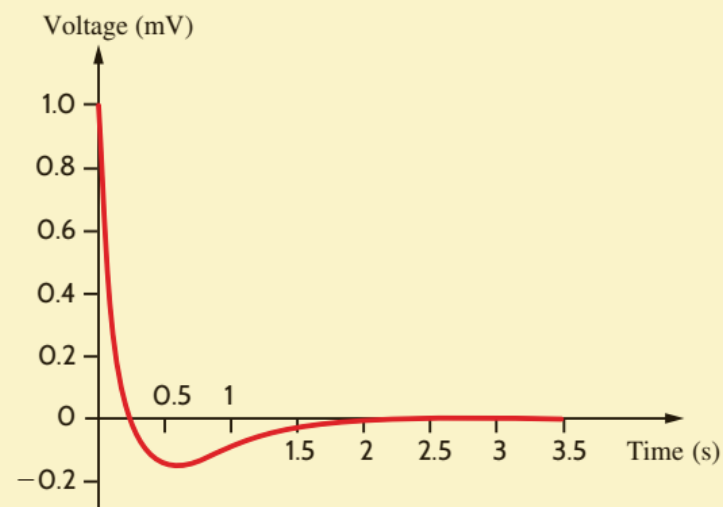
$$W(t) = \frac{1}{2} \cdot L \cdot i(t)^2 = 2.5 \cdot t^2 \cdot e^{-6t}$$




(a)

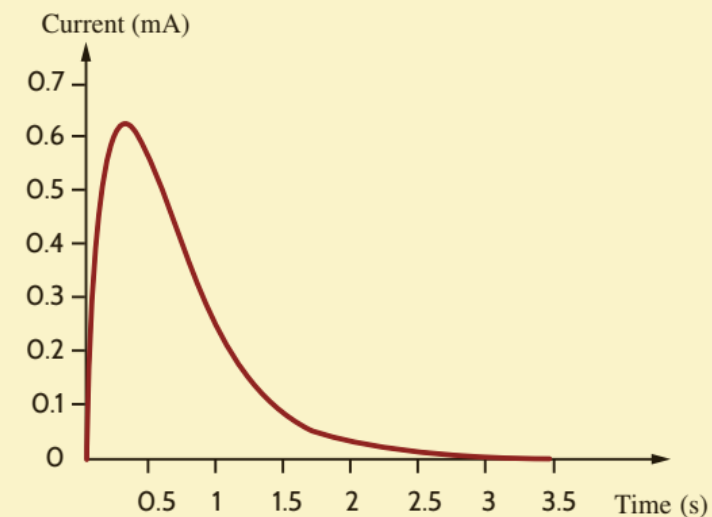

(b)

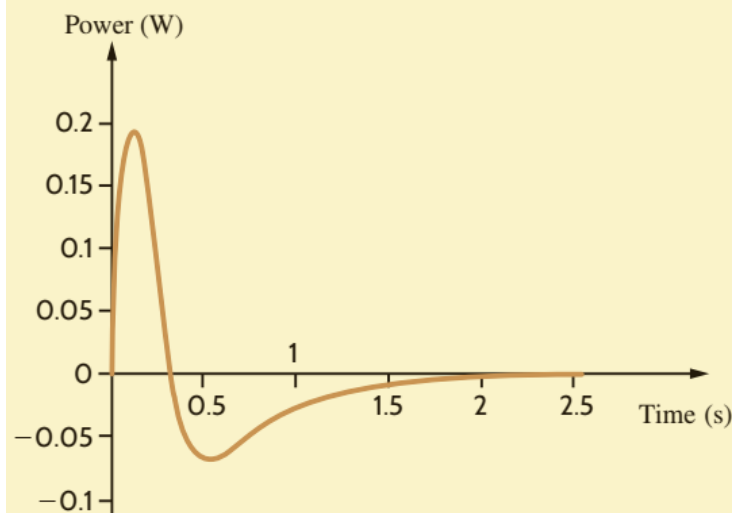


(c)

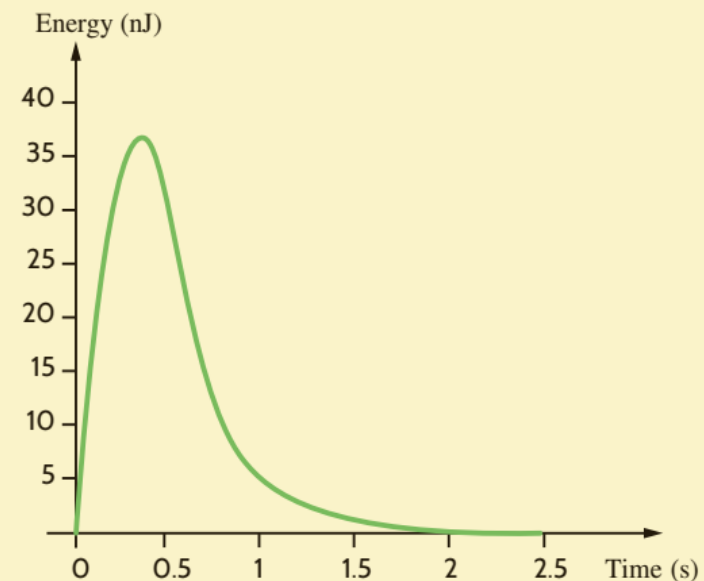

(d)

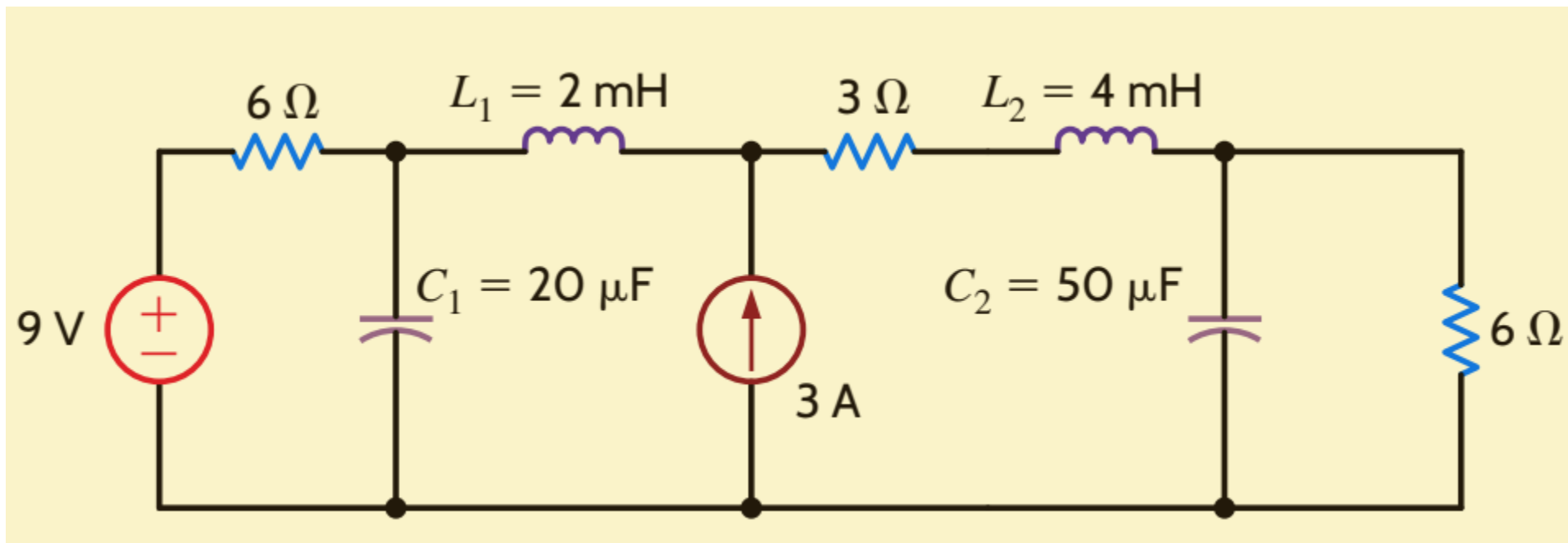4.

Find the total energy stored in the circuit



4.

Currents:

$$\begin{cases} I_{L2} = I_{L1} + 3 \\ 6 I_{L1} + 3 I_{L2} + 6 I_{L2} = 9 \end{cases}$$

Solution:  $I_{L1} = -1.2 \text{ A}$ ,  $I_{L2} = 1.8 \text{ A}$

Voltages:

$$V_{C1} = -6I_{L1} + 9 = 16.2 \text{ V}$$

$$V_{C2} = 6I_{L1} = 10.8 \text{ V}$$

Energies:

$$W_c = \frac{1}{2} CV^2$$

$$W_L = \frac{1}{2} LI^2$$


$$W_{c1} = 2.62 \text{ mJ}$$

$$W_{L1} = 1.44 \text{ mJ}$$

$$W_{c2} = 2.92 \text{ mJ}$$

$$W_{L2} = 6.48 \text{ mJ}$$

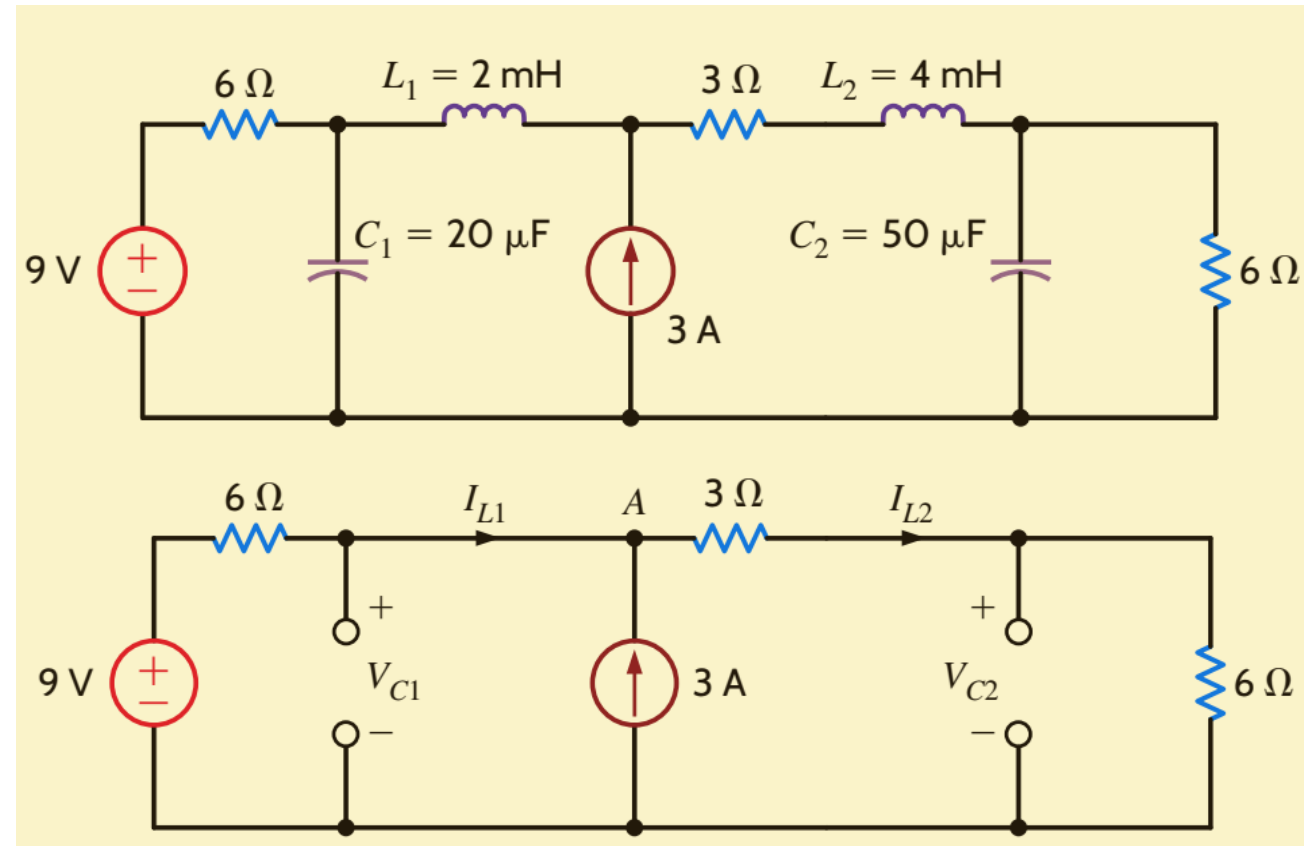Find the total energy stored in the circuit




The total stored energy is 13.46 mJ



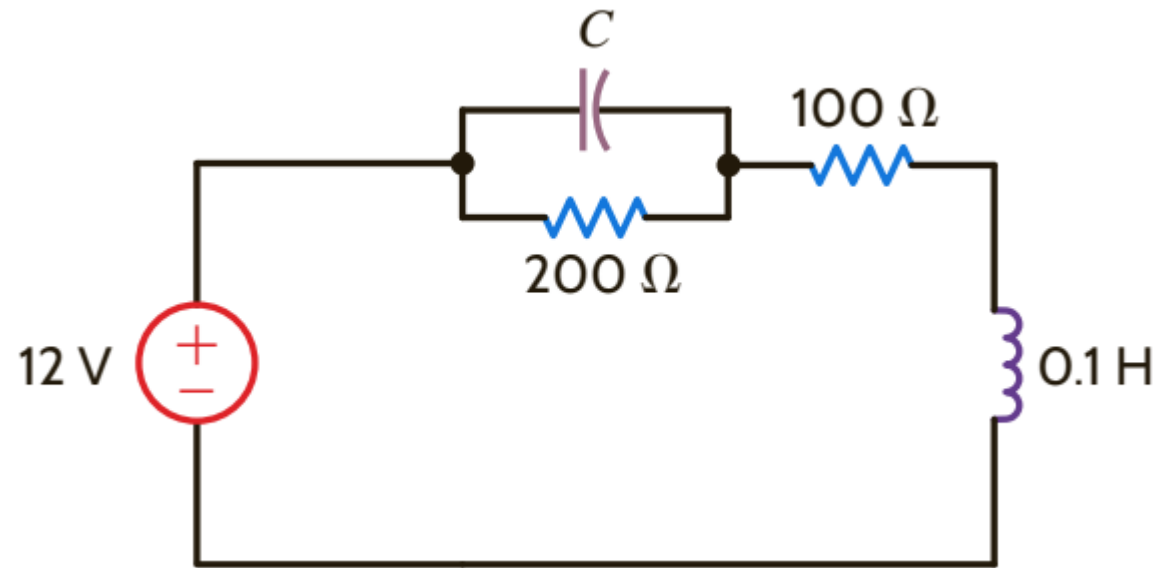5.

Find the value of  $C$  if the energy stored in the capacitor equals the energy stored in the inductor.



5.

Find the value of  $C$  if the energy stored in the capacitor equals the energy stored in the inductor.

$$I = \frac{12}{200 + 100} = 0.04 \quad \text{/current in resistors and inductor}$$


$$W_L = \frac{1}{2} \cdot 0.1 \cdot I^2 = 8 \times 10^{-5} \quad \text{/ energy in inductor}$$

$$V_C = I \cdot 200 = 8 \quad \text{/ voltage on capacitor}$$

$$W_C = \frac{1}{2} \cdot C \cdot (V_C)^2 \quad \text{/ energy in capacitor}$$

$$W_L = W_C$$

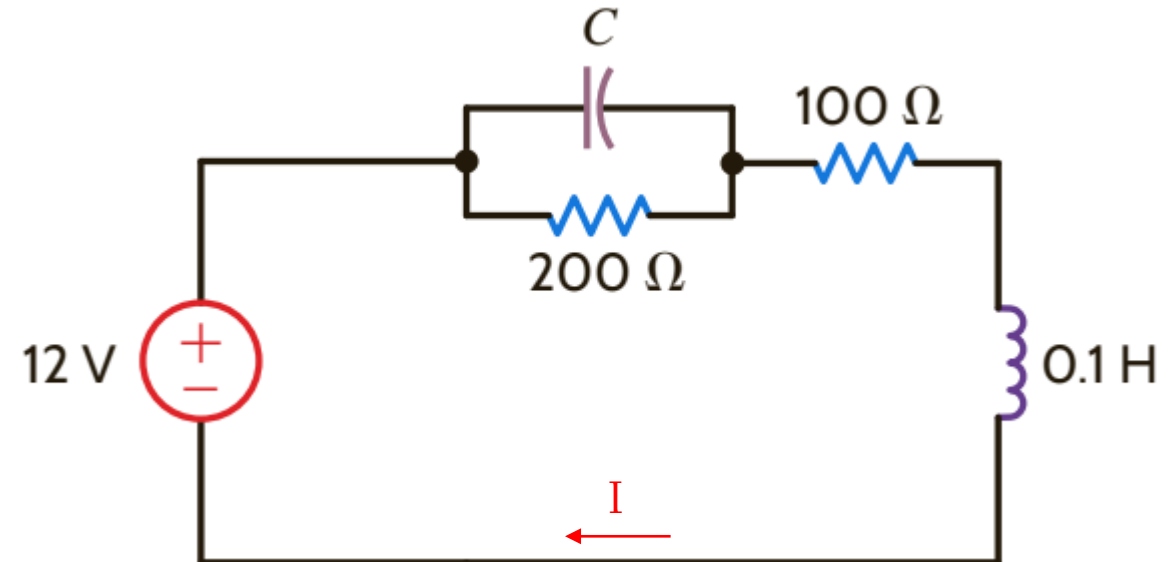
$$C = \frac{2 \cdot W_L}{(V_C)^2} = 2.5 \times 10^{-6}$$



Answer:  $2.5\ \mu\text{F}$

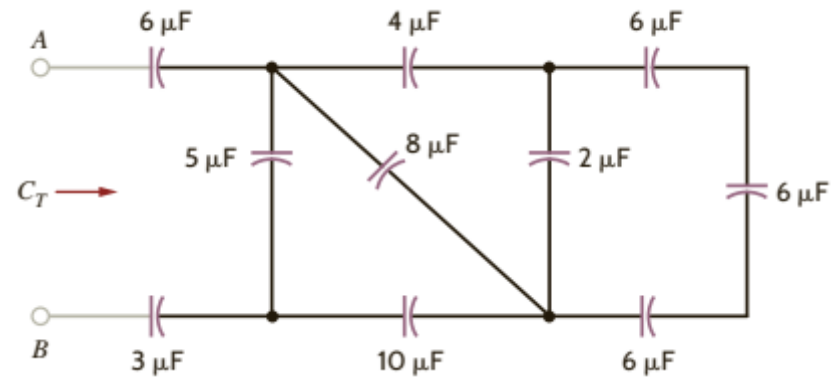6.


Compute the equivalent capacitance of the network



Answer:  $5/3\ \mu\text{F}$

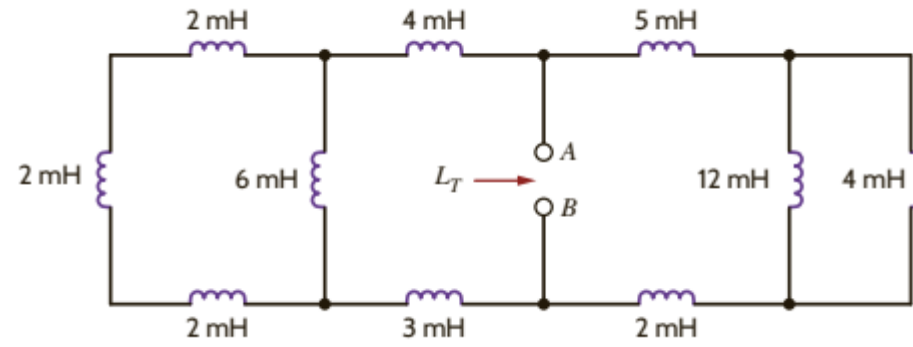7.

Compute the equivalent inductance of the network



Answer:  $5\text{ mH}$