



## Physics 2. Electrical Engineering Week 8.2 **Impedance**

INOPOLIS  
UNIVERSITY

Kirill Poletkin and Igor Gaponov

Institute of Robotics and Computer Vision

# Objectives


The main objectives of today's lecture are:

- Become familiar with the concept of **impedance**
- Practice finding **impedance of complex circuits**
- Apply phasors and impedance concepts to **analyze dynamic circuits**

**Impedance**
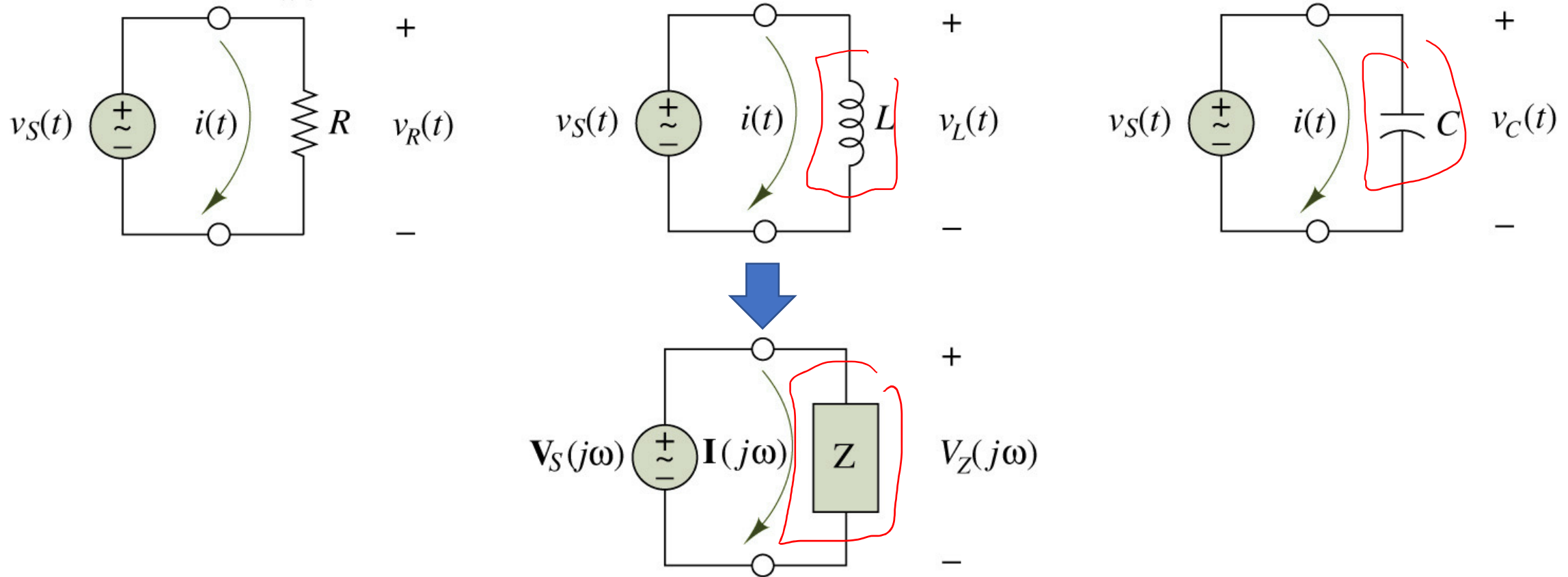
# What is Impedance?

Impedance is a **frequency-dependent resistance**.



AC circuits in  
phasor/impedance form

# Finding Impedance




Let the source voltage be defined by

$$v_S(t) = A \cos \omega t = Ae^{j0^\circ}$$

Let us examine the frequency-dependent properties of the

- resistor,
- inductor, and
- capacitor.
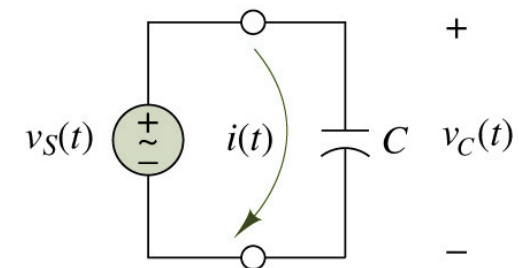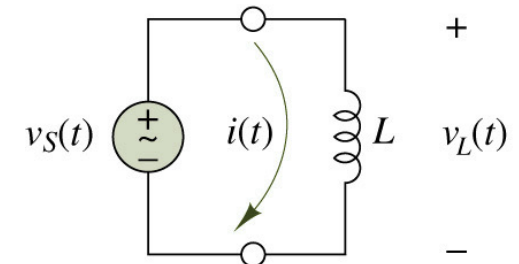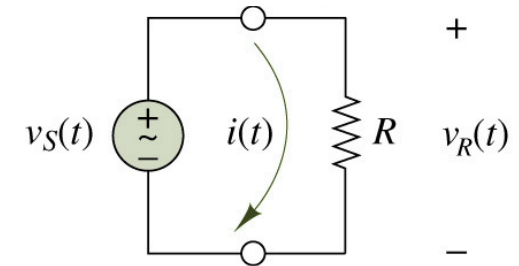
$$Z_R = \frac{V_S / i(\omega)}{I_R(j\omega)}$$




AC circuits

# Resistor Impedance

$$v_S(t) = A \cos \omega t = Ae^{j0^\circ}$$

According to Ohm's law, the current flowing through the resistor is
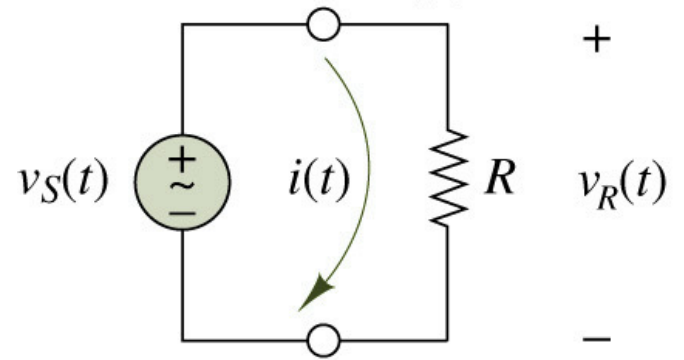
$$i(t) = \frac{v_S(t)}{R} = \frac{A}{R} \cos \omega t$$



- In phasor notation,

$$V_Z(j\omega) = A \angle 0$$

$$I_Z(j\omega) = \frac{A}{R} \angle 0$$

- Therefore, the impedance  $Z$  of a resistor is  $Z_R(j\omega) = \frac{V_Z(j\omega)}{I_Z(j\omega)} = R$



# Inductor Impedance (1)

Recall the current-voltage relationships for the ideal inductor:

- In phasor notation,

$$V_Z(j\omega) = A \angle 0$$


$$I(j\omega) = \frac{A}{\omega L} \angle -\frac{\pi}{2}$$

- Thus, the impedance of the inductor is

$$Z_L(j\omega) = \frac{V_Z(j\omega)}{I(j\omega)} = \omega L \angle \frac{\pi}{2} = j\omega L$$

$$\frac{Ae^{j0}}{\frac{A}{\omega L} e^{-j\frac{\pi}{2}}}$$
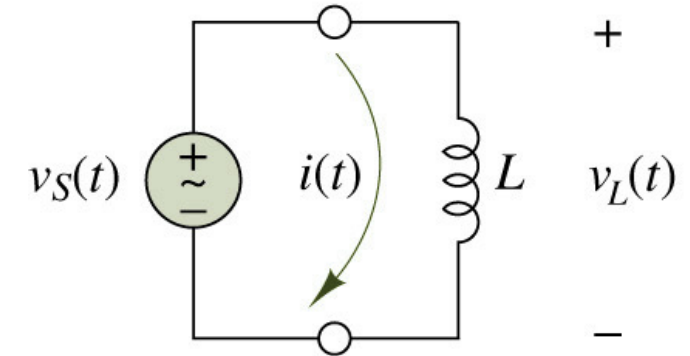
$$v_S(t) = A \cos \omega t = Ae^{j0^\circ}$$



$$i_L(t) = i(t) = \frac{1}{L} \int v_S(t') dt'$$

$$i_L(t) = \frac{1}{L} \int A \cos \omega t' dt'$$


$$= \frac{A}{\omega L} \sin \omega t = \frac{A}{\omega L} \cos \left( \omega t - \frac{\pi}{2} \right)$$

# Inductor Impedance (2)

Hence, the inductor behaves as a complex frequency-dependent resistor, and the magnitude of this complex resistor  $\omega L$  is proportional to the signal frequency  $\omega$ .

This means that

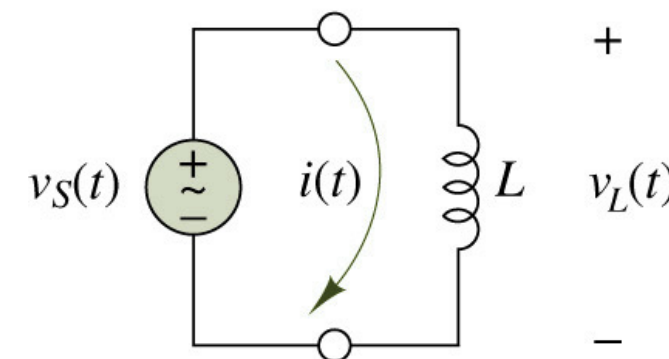- At **low** frequencies, an inductor acts as a **short circuit**,
- At **high** frequencies, an inductor acts as an **open circuit**.



$$Z_L(j\omega) = \omega L \angle \frac{\pi}{2} = j\omega L$$



# Capacitor Impedance (1)


Recall the current-voltage relationships for the ideal capacitor:

- In phasor notation,

$$\begin{aligned} V_Z(j\omega) &= A \angle 0 \\ I(j\omega) &= \omega C A \angle -\frac{\pi}{2} \end{aligned}$$

- Thus, the impedance of the capacitor is
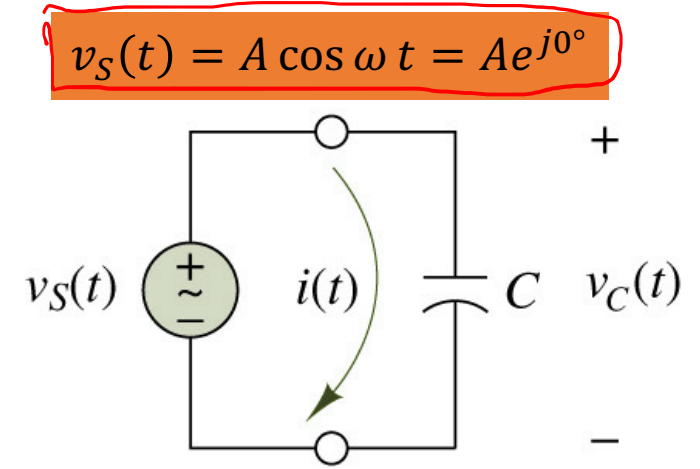
$$\begin{aligned} Z_C(j\omega) &= \frac{V_Z(j\omega)}{I(j\omega)} = \frac{1}{\omega C} \angle -\frac{\pi}{2} \\ &= \frac{-j}{\omega C} = \frac{1}{j\omega C} \end{aligned}$$




$$\begin{aligned} i_C(t) &= C \frac{dv_C(t)}{dt} \\ i_C(t) &= C \frac{d}{dt} (A \cos \omega t) \\ &= -CA\omega \sin \omega t \\ &= \omega C A \cos \left( \omega t + \frac{\pi}{2} \right) \end{aligned}$$

# Capacitor Impedance (2)

Thus, the impedance of a capacitor is also a frequency-dependent complex quantity, with the **impedance of the capacitor** varying as an **inverse function of frequency**.

Hence,

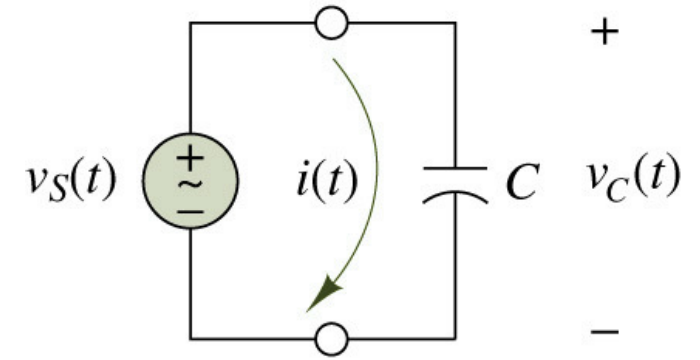- At **low** frequencies, a capacitor acts as an **open circuit**,
- At **high** frequencies, a capacitor acts as a **short circuit**.



$$Z_C(j\omega) = \frac{-j}{\omega C} = \frac{1}{j\omega C}$$


# Impedance

In its most general form, the **impedance** of a circuit element is defined as the sum of a real part and an imaginary part:

$$Z(j\omega) = R(j\omega) + jX(j\omega)$$

where the components are

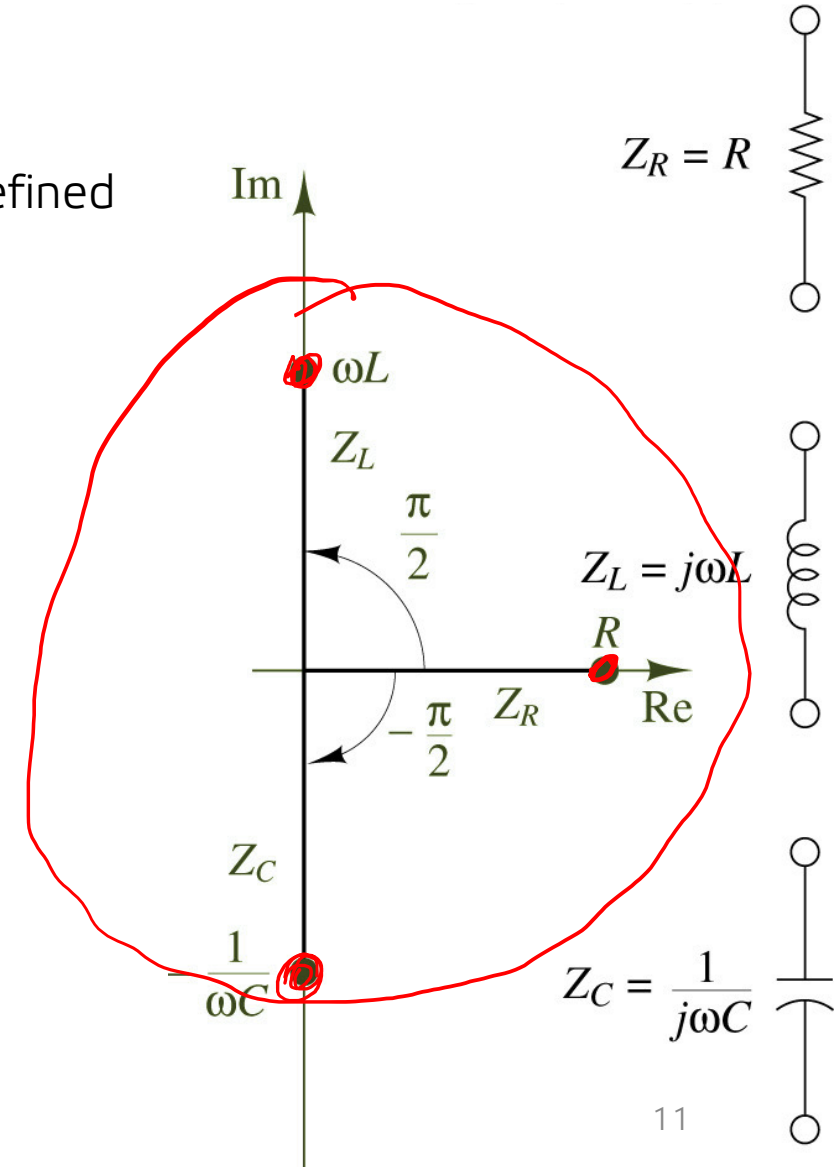- $R$ : resistance and
- $X$ : reactance.



# Impedance of Complex Circuits

# Impedance of Complex Circuits (1)


We can find impedance of rather complex-looking circuits, which may come in extremely handy in their analysis later. Have a look at this example.

**Problem:** Find the **equivalent impedance** of the circuit shown here.

**Known quantities:**  $\omega = 10^4 \text{ rad/s}$ ,  $R_1 = 100 \Omega$ ,  $L = 10 \text{ mH}$ ,  $R_2 = 50 \Omega$ ,  $C = 10 \mu\text{F}$ .

Just like we did when finding equivalent resistance, we can find  $Z_{RC}$  first as
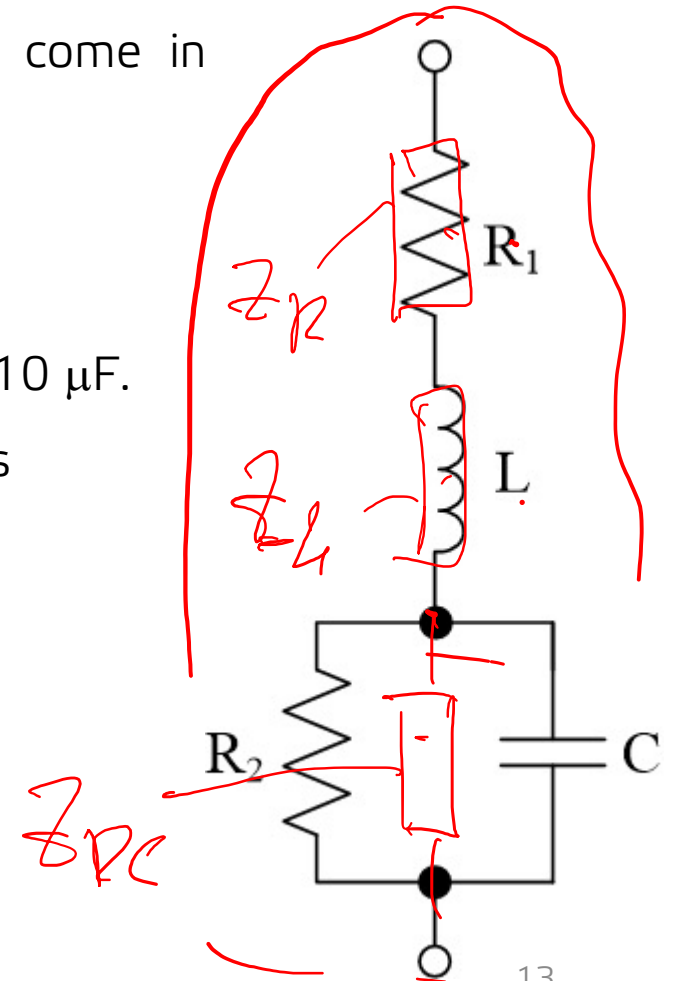
$$\begin{aligned} Z_{RC} &= Z_{R_2} \parallel Z_{C_1} = R_2 \parallel \frac{1}{j\omega C} \\ &= \frac{R_2(1/j\omega C)}{R_2 + 1/j\omega C} = \frac{R_2}{1 + j\omega C R_2} \end{aligned}$$




# Impedance of Complex Circuits (2)

Computation yields  $Z_{RC} = \frac{50}{1 + j5} = 1.92 - j9.62 = 9.81 \angle (-1.3734) \Omega$

Next, we determine the equivalent impedance  $Z_{eq}$ :

$$\begin{aligned} Z_{eq} &= R_1 + j\omega L + Z_{RC} = 100 + j10^4 \times 10^{-2} + 1.92 - j9.62 \\ &= 101.92 + j90.38 = 136.2 \angle 0.723 \Omega \end{aligned}$$

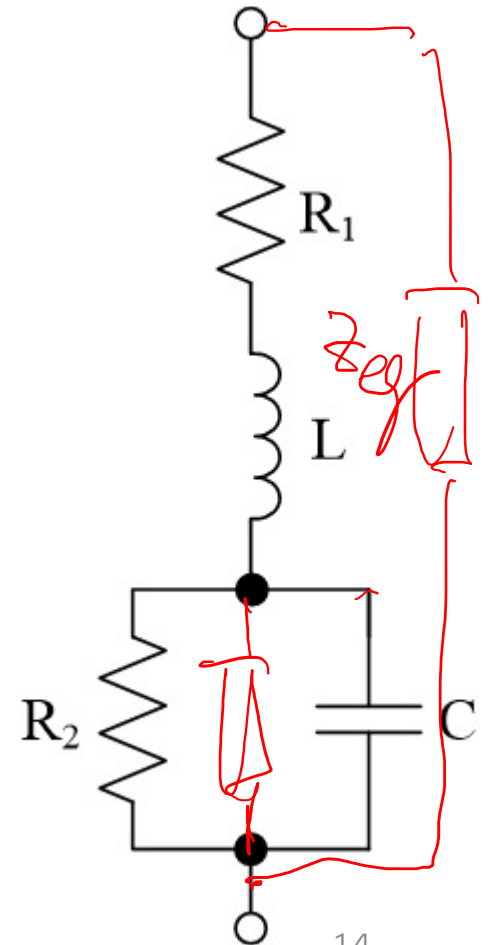**Q:** Is this impedance **inductive** or **capacitive**?



# Impedance of Complex Circuits (3)


Let us repeat the previous calculations for

1.  $\omega = 0$  rad/s (DC voltage):  $Z_{eq} = 150 \Omega$
2.  $\omega = 1000$  rad/s:  $Z_{eq} = 140 - j10 \Omega$
3.  $\omega = 2450$  rad/s:  $Z_{eq} = 120 \Omega$

**Q1:** Are impedance values **inductive or capacitive**?

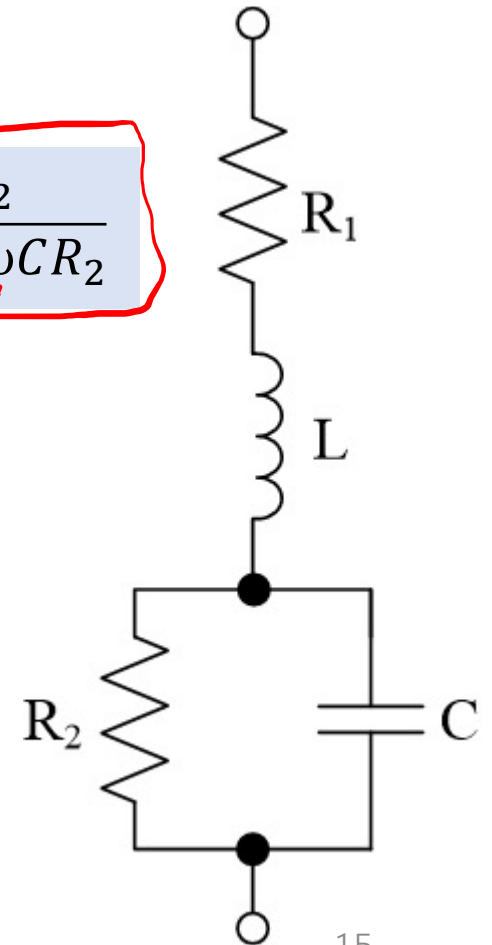**Q2:** What is the **equivalent circuit** for the last case?



$$Z_{eq} = R_1 + j\omega L + \frac{R_2}{1 + j\omega C R_2}$$




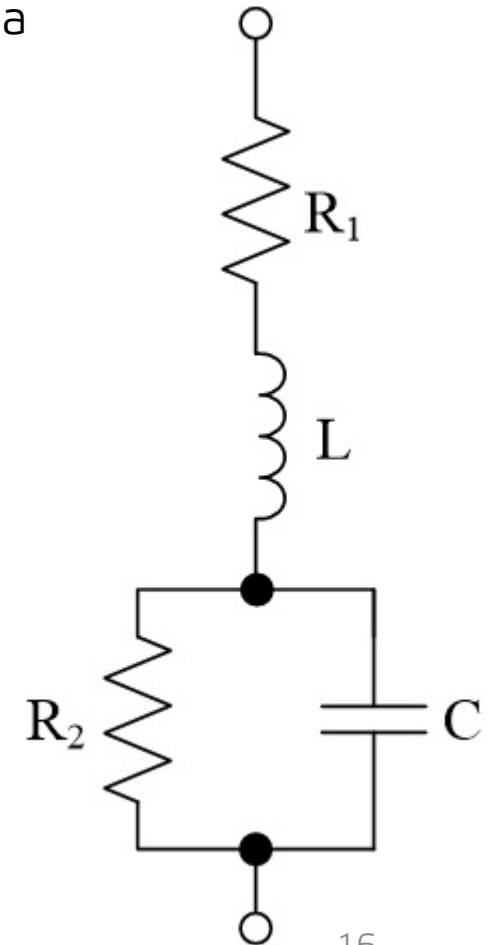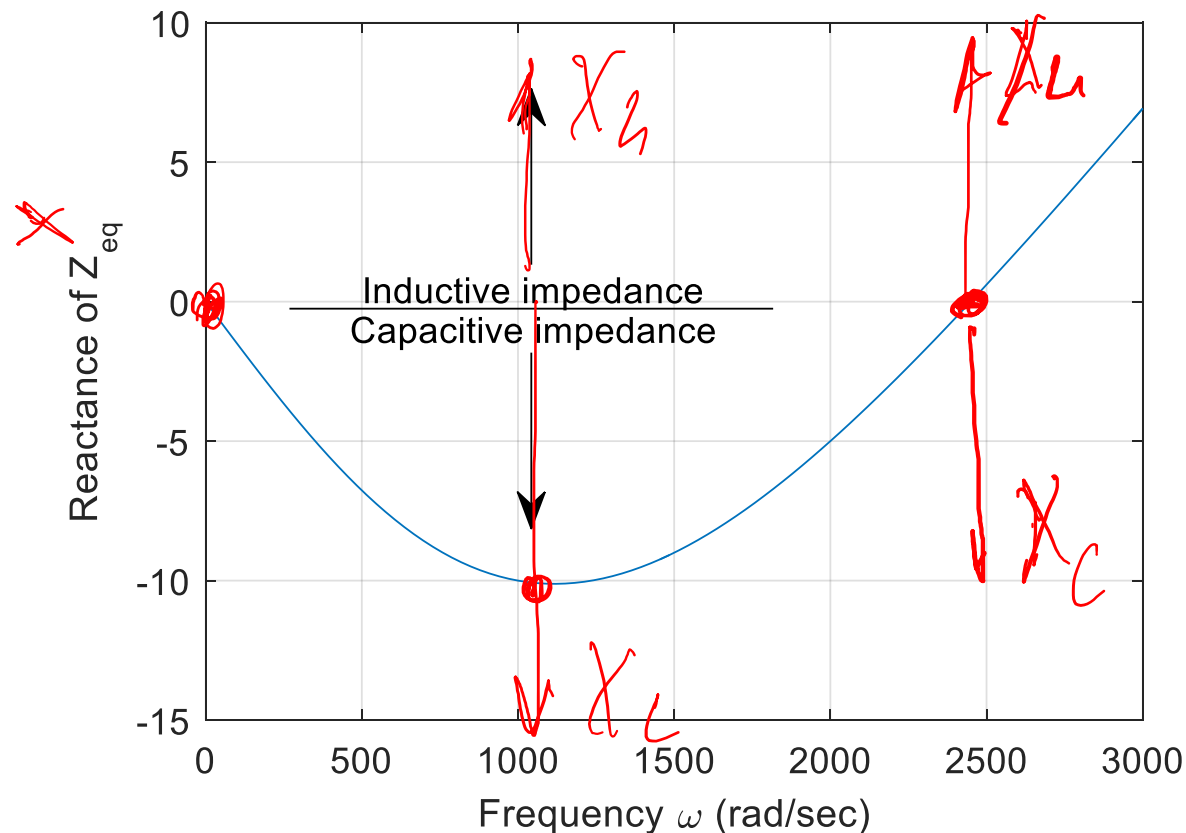
# Impedance of Complex Circuits (4)

We can conduct a small investigation and plot the reactance of this circuit as a function of frequency as follows:




# AC Circuit Analysis with Phasors and Impedance

# AC Circuit Analysis


Just like we did so in case of DC circuits, we often need to **analyze AC circuits** with energy storage elements.

One way of doing so is as follows:

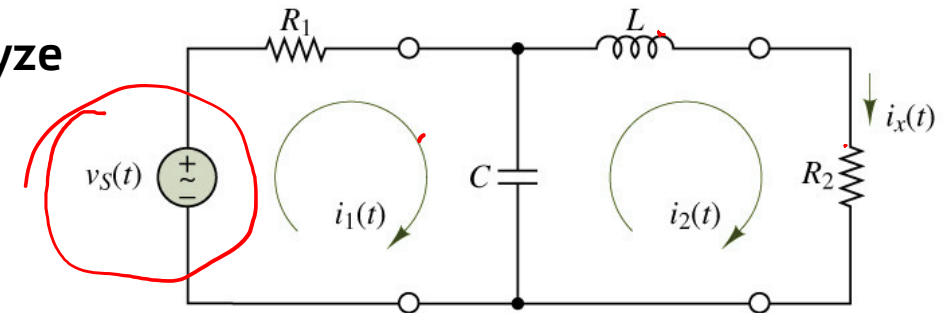1. Represent a sine wave **power source by a phasor**, and each **circuit element by an impedance**.
2. Obtain **solution in the phasor form** by applying the circuit analysis method studied previously (KVL/KCL, node voltage method, network current method, etc.)
3. **Convert the solution** from phasor (frequency) domain into **time domain**.



A sample circuit  
for AC analysis

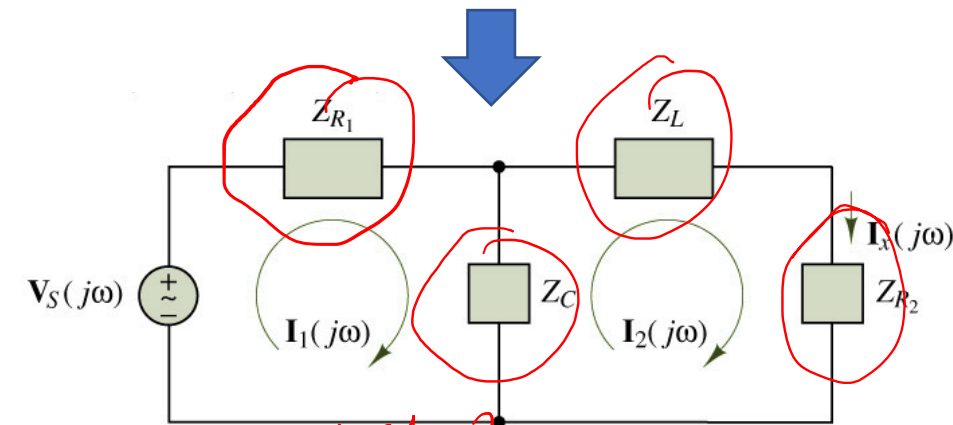

The same circuit  
in phasor form


$$I_1 = I_1 e^{j\theta_1(\omega)} \quad I_2 = I_2 e^{j\theta_2(\omega)}$$

# AC Circuit Analysis: Exercise (1)

Given the circuit below, find the source current  $i_s(t)$  at  $\omega = 100$  rad/sec.

Using the Ohm's law, one can write

$$i_s(t) = \frac{v_s(t) - v(t)}{R_1}$$

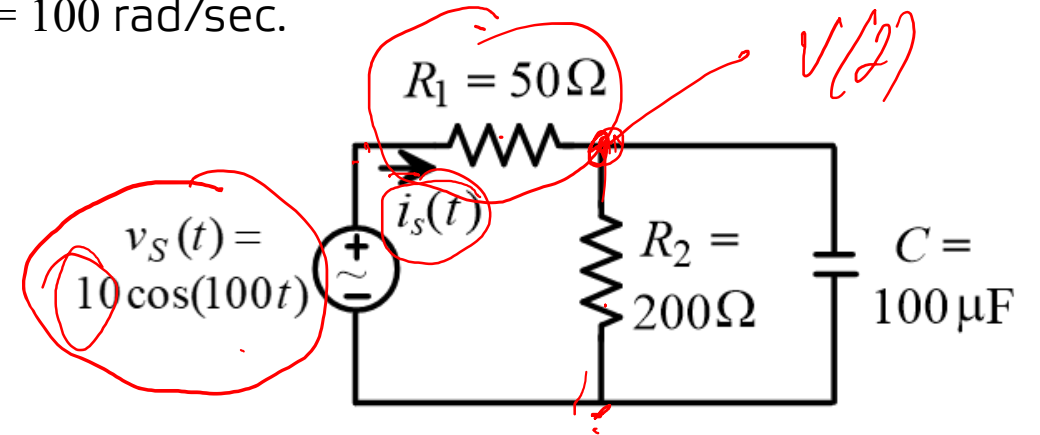


Now, let us **convert the voltage source into phasor form** and **find all the impedance values**

$$v_s(t) = 10 \cos \omega t, \quad \omega = 377 \text{ rad/s}$$


$$V_s(j\omega) = 10 \angle 0^\circ \text{ V}$$
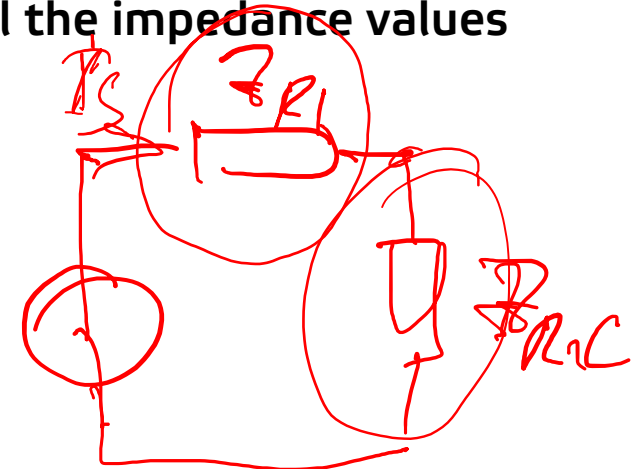
$$Z_{R_1} = R_1, \quad Z_{R_2} = R_2, \quad Z_C = \frac{1}{j\omega C}$$



# AC Circuit Analysis: Exercise (2)

The resulting circuit is then

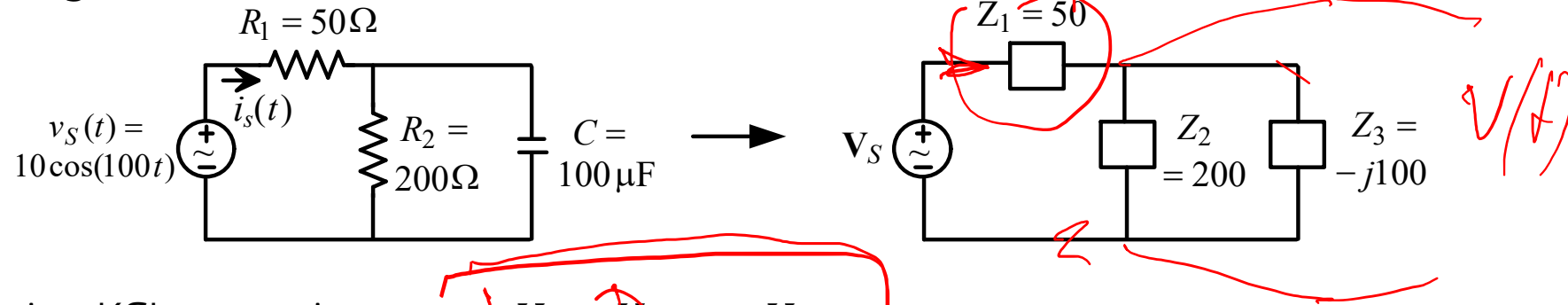

Finally, using KCL, we write

$$\frac{V_S - V}{Z_{R_1}} = \frac{V}{Z_{R_2} \parallel Z_C}$$

Solving yields

$$\begin{aligned} \frac{V_S}{Z_{R_1}} &= V \left( \frac{1}{Z_{R_2} \parallel Z_C} + \frac{1}{Z_{R_1}} \right) = V \left( \frac{1}{\frac{R_2(1/j\omega C)}{R_2 + (1/j\omega C)} + \frac{1}{R_1}} \right) \\ &= V \left( \frac{j\omega C R_2 + 1}{R_2} + \frac{1}{R_1} \right) = V \left( \frac{j\omega C R_2 R_1 + R_1 + R_2}{R_1 R_2} \right) \end{aligned}$$

# AC Circuit Analysis: Exercise (3)

Substituting all the values yields

$$\begin{aligned} V &= \left( \frac{j\omega CR_2R_1 + R_1 + R_2}{R_1R_2} \right)^{-1} \frac{V_S}{R_1} = \left( \frac{R_1R_2}{j\omega CR_2R_1 + R_1 + R_2} \right) \frac{V_S}{R_1} \\ &= \frac{50 \times 200}{j377 \times 10^{-4} \times 50 \times 200 + 50 + 200} \cdot \frac{V_S}{50} \\ &= 0.4221 \angle (-0.9852) V_S = 4.421 \angle (-0.9852). \end{aligned}$$

Thus,

$$I_S = \frac{V_S - V}{Z_{R_1}} = \frac{10 \angle 0 - 4.421 \angle (-0.9852)}{50} = 0.1681 \angle (0.4537)$$





**Thank you for your attention!**

**innopolis**  
UNIVERSITY

Igor Gaponov

[i.gaponov@innopolis.ru](mailto:i.gaponov@innopolis.ru)