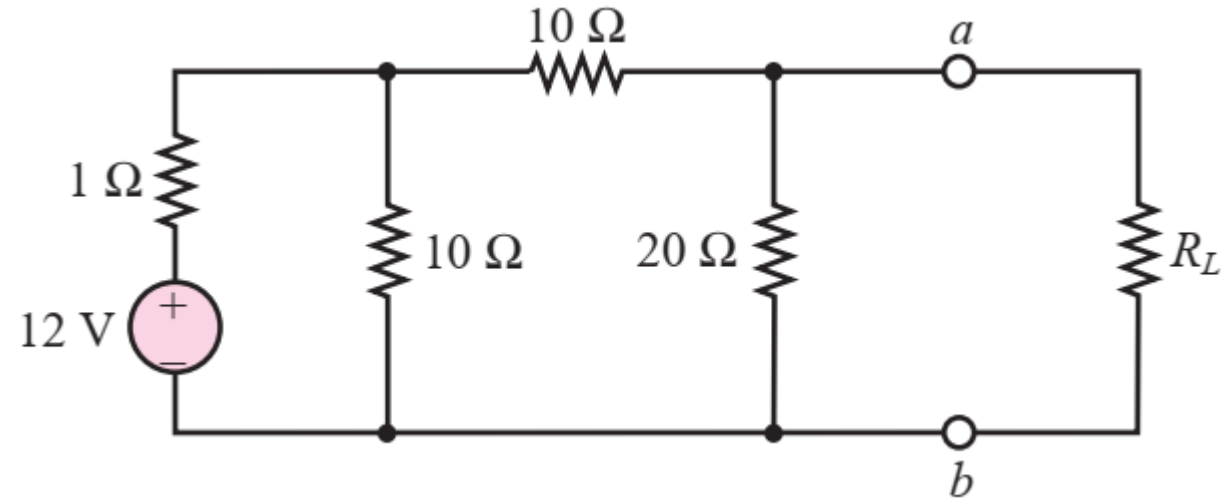



1.

For the circuit below, find the Thévenin equivalent resistance seen by the load resistor R_L .



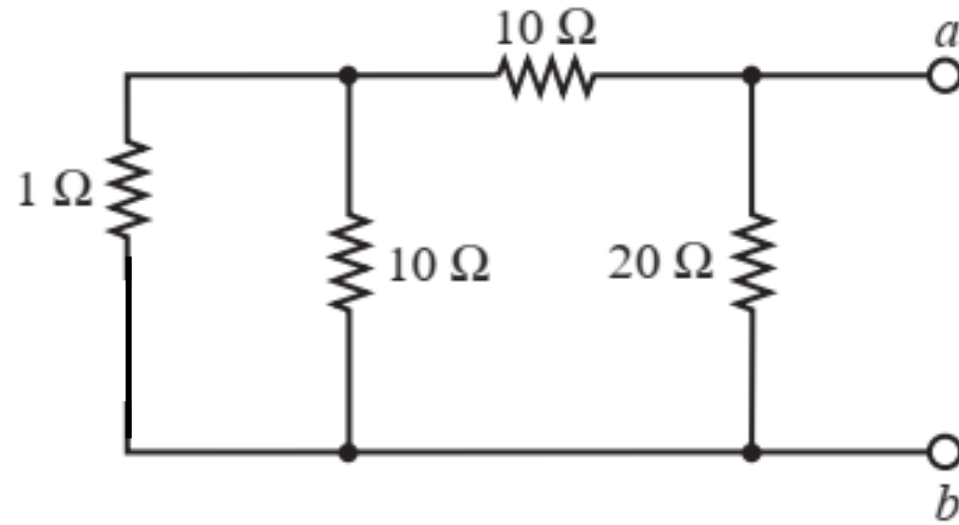1.


For the circuit below, find the Thévenin equivalent resistance seen by the load resistor R_L .



$$R_T = ((1\Omega \parallel 10\Omega) + 10\Omega) \parallel 20\Omega = \left[\frac{1}{\left[\left(1 + \frac{1}{10}\right)^{-1} + 10 \right]} + \frac{1}{20} \right]^{-1} = 7.059\Omega$$


1.

Find the Thevenin voltage V_T .

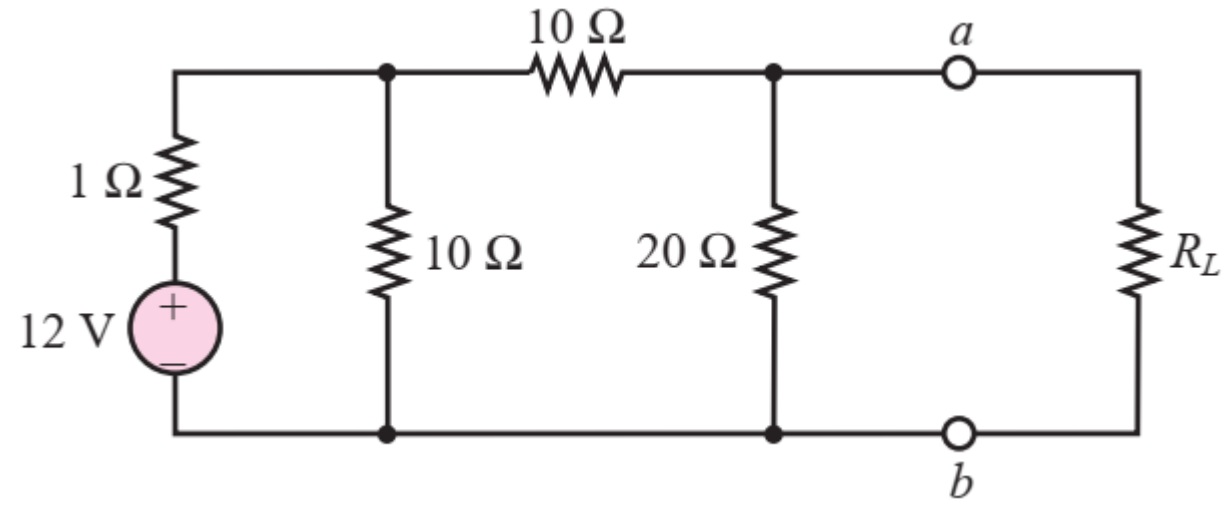

1.

Find the Thevenin voltage V_T .

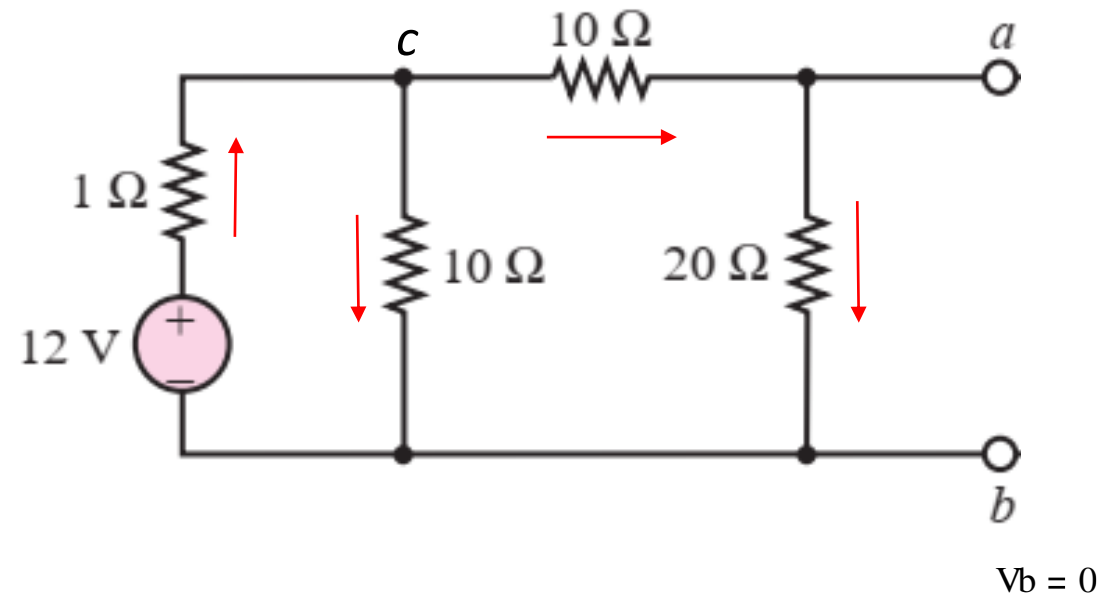


$$\begin{cases} \frac{12 - V_c}{1} - \frac{V_c - V_a}{10} - \frac{V_c}{10} = 0 \\ \frac{V_c - V_a}{10} - \frac{V_a}{20} = 0 \end{cases}$$

Answer: $V_T = V_a = 7.059 \text{ V}$


1.

Find the Norton Current I_N .

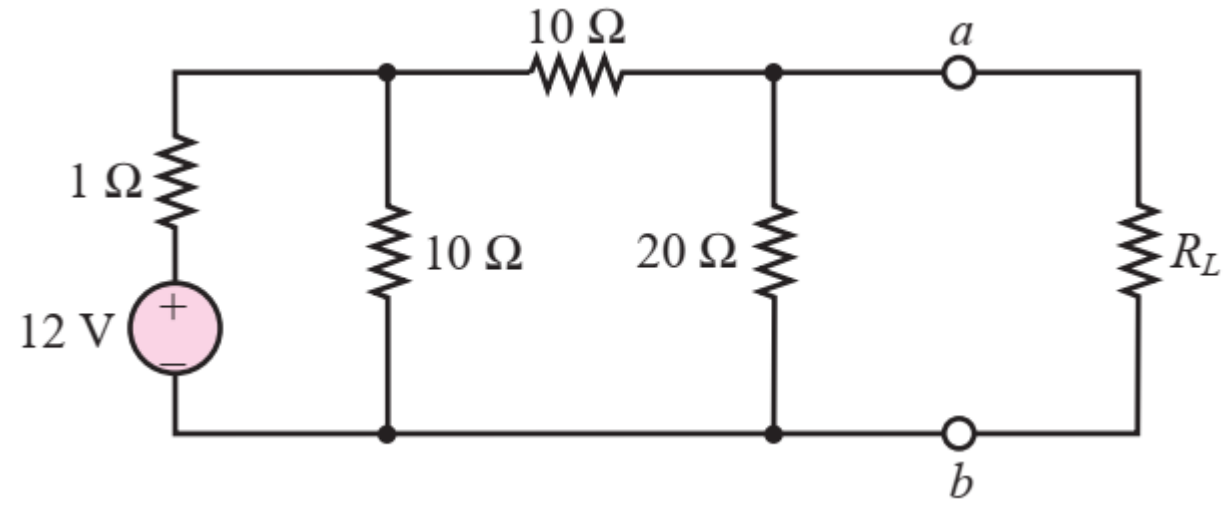


2.

Find the Norton Current I_N .

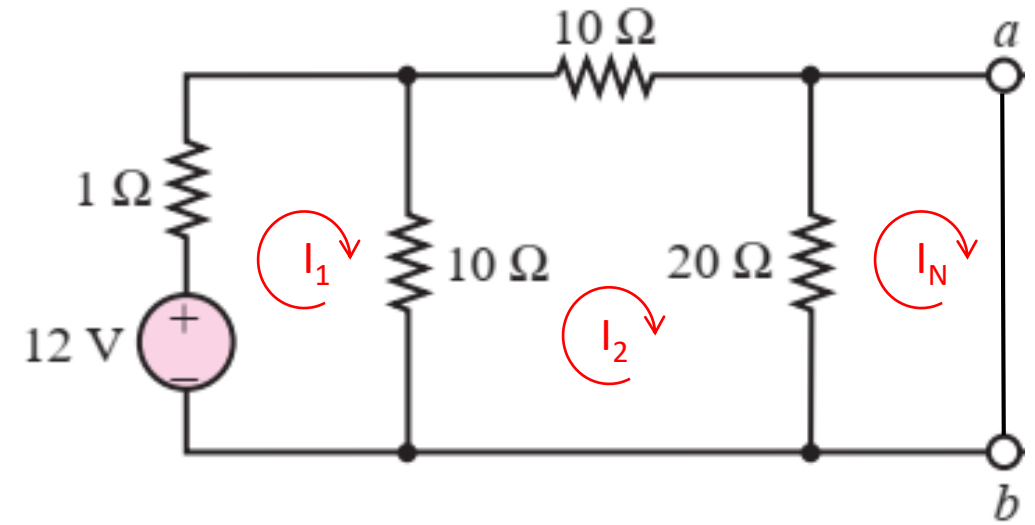


$$\begin{cases} 12 - I_1 \cdot 1 - (I_1 - I_N) \cdot 10 = 0 \\ -(I_N - I_1) \cdot 10 - I_N \cdot 10 = 0 \end{cases}$$
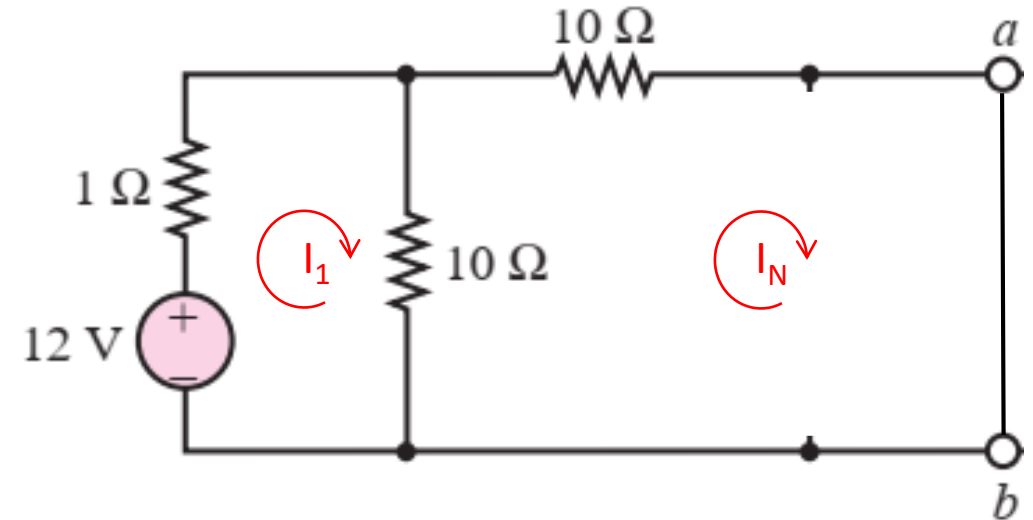
$$\left. \begin{array}{l} \text{Answer: } I_N = 1 \text{ A} \\ V_T = 7.059 \text{ V} \\ R_T = 7.059 \Omega \end{array} \right\} V_T = I_N R_T$$




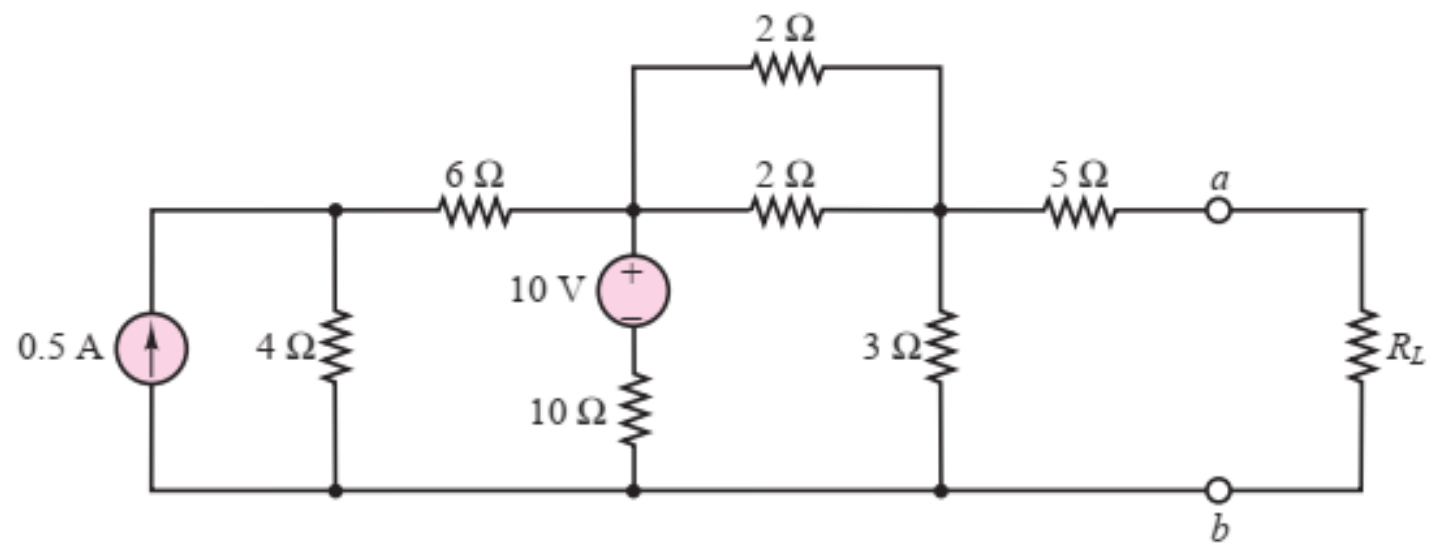2.

Find the Thévenin equivalent resistance seen by the load resistor R_L in the following circuit.




2.

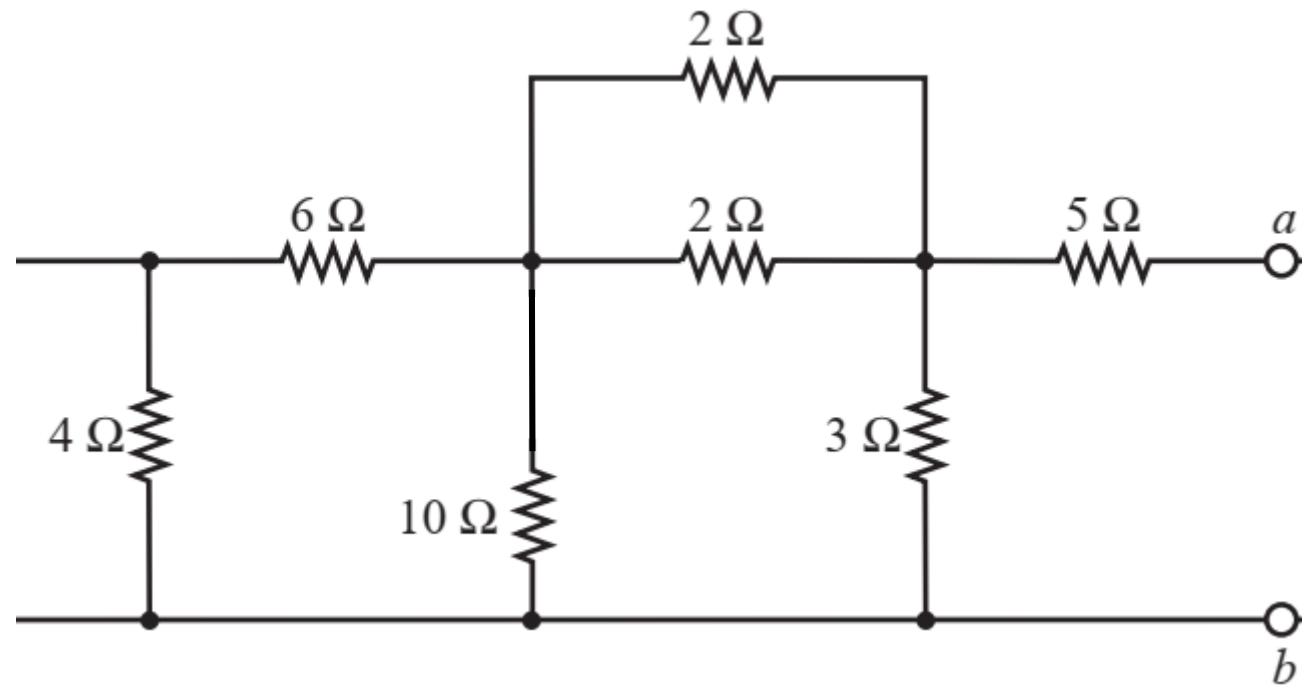

$$R_T = ((4\ \Omega + 6\ \Omega) \parallel 10\ \Omega) + (2\ \Omega \parallel 2\ \Omega) \parallel 3\ \Omega + 5\ \Omega = \left[\frac{1}{\left[\left(\frac{1}{4+6} + \frac{1}{10} \right)^{-1} + \left(\frac{1}{2} + \frac{1}{2} \right)^{-1} \right]} + \frac{1}{3} \right]^{-1} + 5 = 7\ \Omega$$

2.

Find the Thevenin voltage V_T .


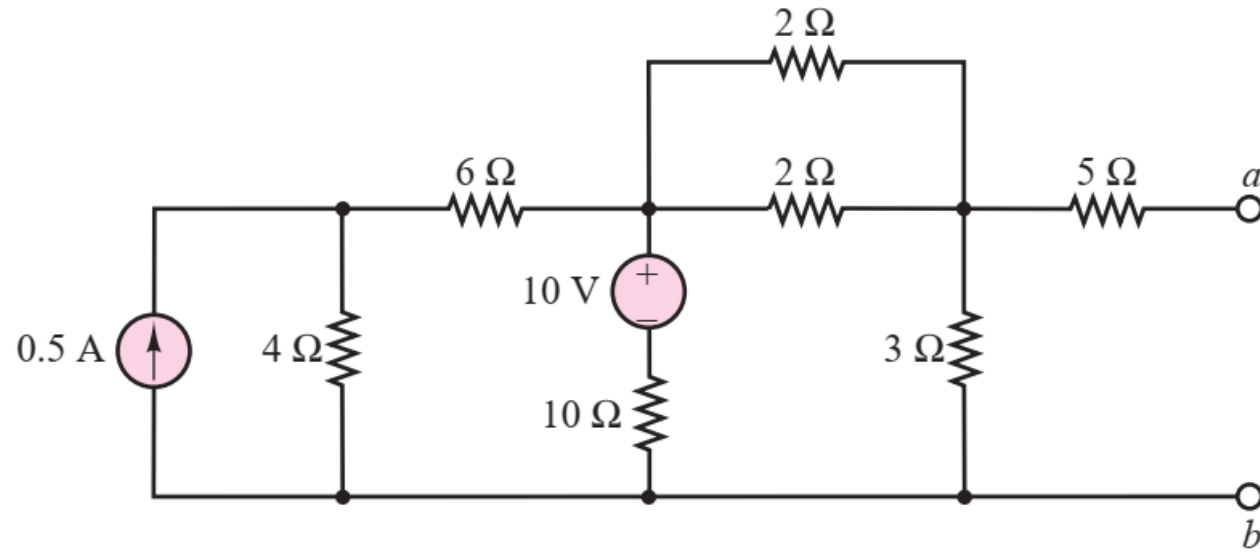


2.

Find the Thevenin voltage V_T .


$$\begin{cases} 0.5 - \frac{V_d}{4} - \frac{V_d - V_c}{6} = 0 \\ \frac{V_d - V_c}{6} + \frac{10 - V_c}{10} - \frac{V_c - V_a}{1} = 0 \\ \frac{V_c - V_a}{1} - \frac{V_a}{3} = 0 \end{cases}$$

Answer: $V_T = V_a = 2 \text{ V}$

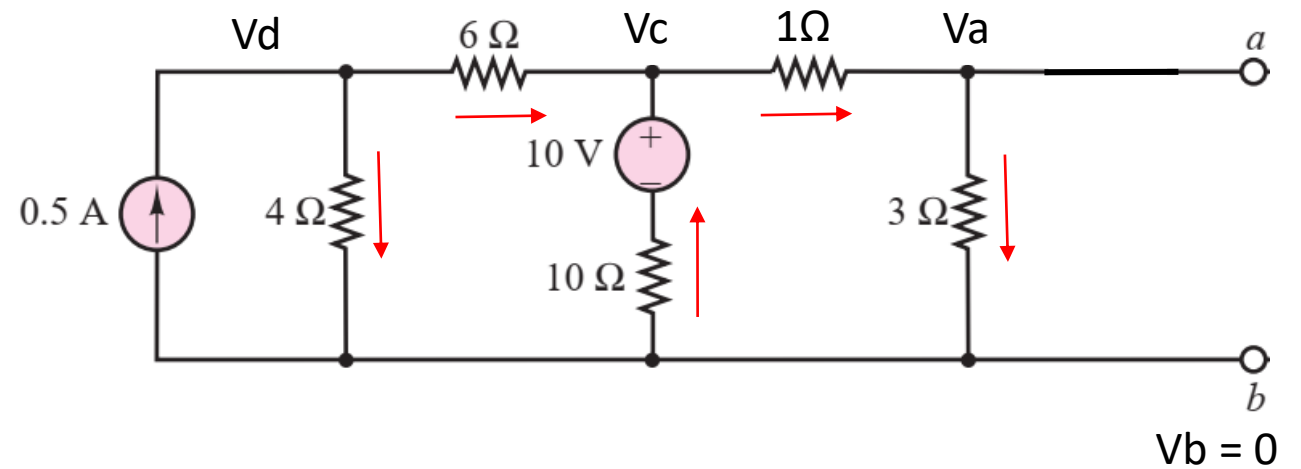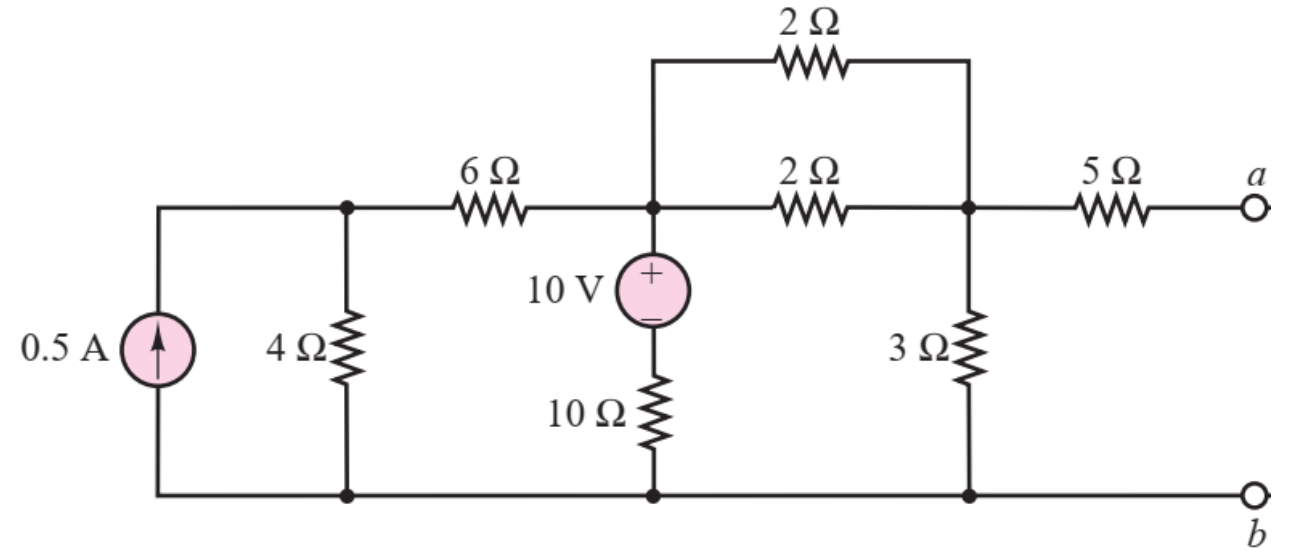

2.

Find the Norton Current I_N .

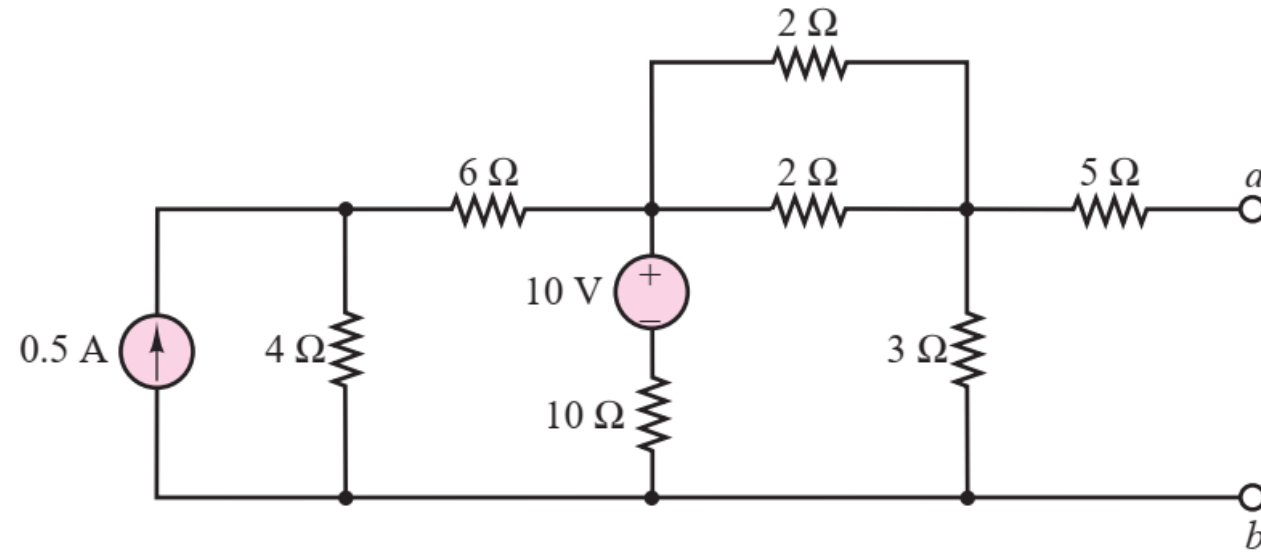

2.

Find the Norton Current I_N .



$$\begin{cases} -(I_2 - I_1) \cdot 4 - I_2 \cdot 6 - 10 - (I_2 - I_3) \cdot 10 = 0 \\ -(I_3 - I_3) \cdot 10 + 10 - I_3 \cdot 1 - (I_3 - I_N) \cdot 3 = 0 \\ -(I_N - I_3) \cdot 3 - I_N \cdot 5 = 0 \end{cases}$$

$$\text{Answer: } I_N = 0.286 \text{ A}$$

$$V_T = 2 \text{ V}$$


$$R_T = 7 \Omega$$

$$V_T = I_N R_T$$

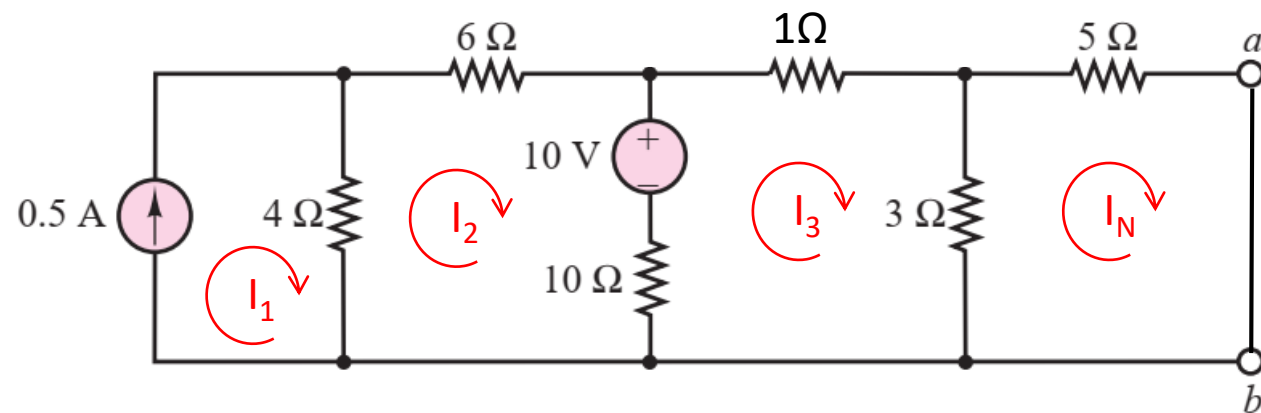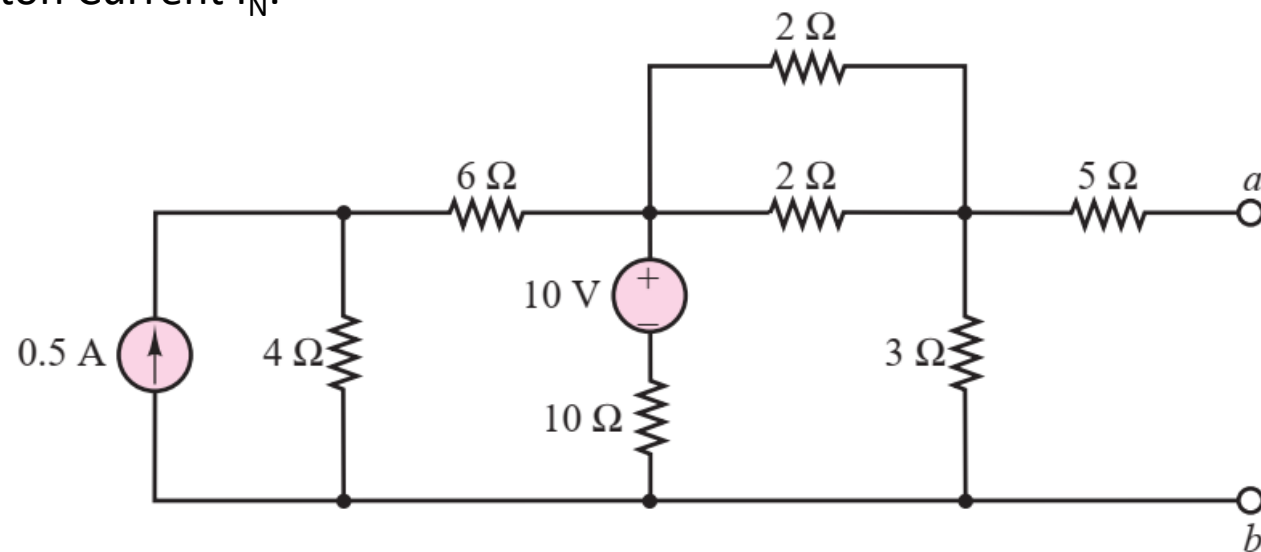

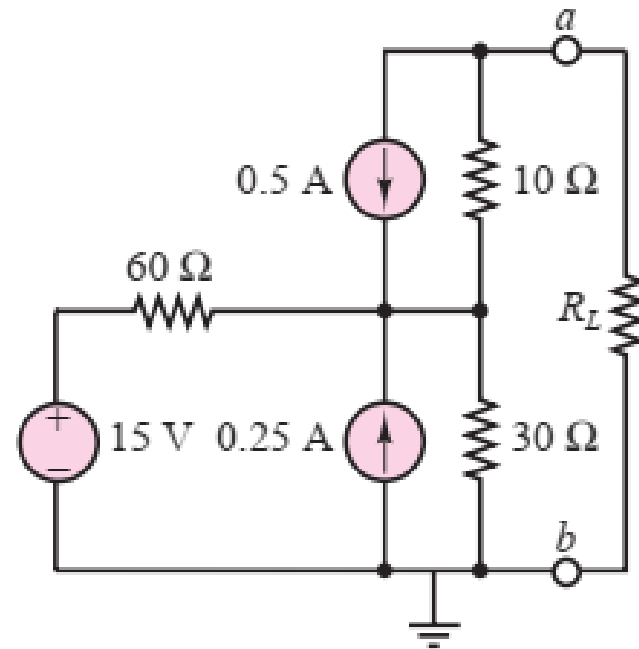3.


Find the Thevenin equivalent circuit for the circuit in the figure below



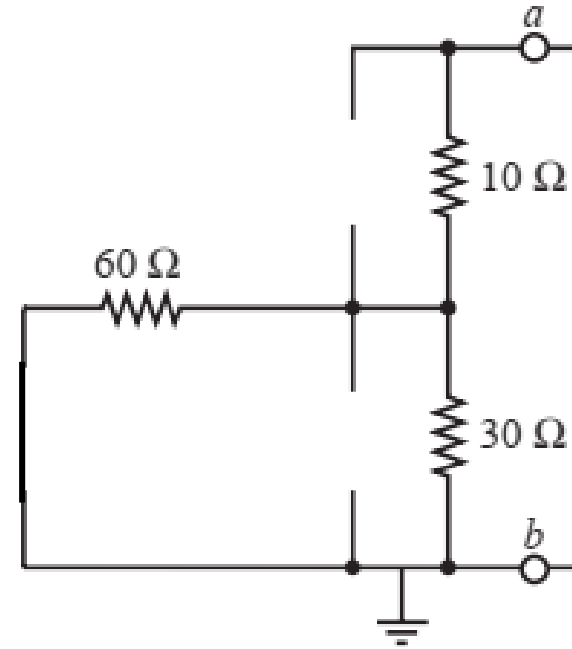3.

Find the Thevenin Resistance R_T .

$$R_T = (60\ \Omega \parallel 30\ \Omega) + 10\ \Omega = 20\ \Omega + 10\ \Omega = 30\ \Omega$$





3.

Find the Thevenin voltage V_T .

$$\begin{cases} \frac{15 - V_c}{60} + 0.5 + 0.25 - \frac{V_c - V_a}{10} - \frac{V_c}{30} = 0 \\ -0.5 + \frac{V_c - V_a}{10} = 0 \end{cases}$$

Answer: $V_T = V_a = 5 \text{ V}$

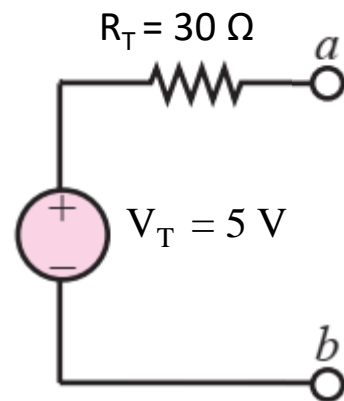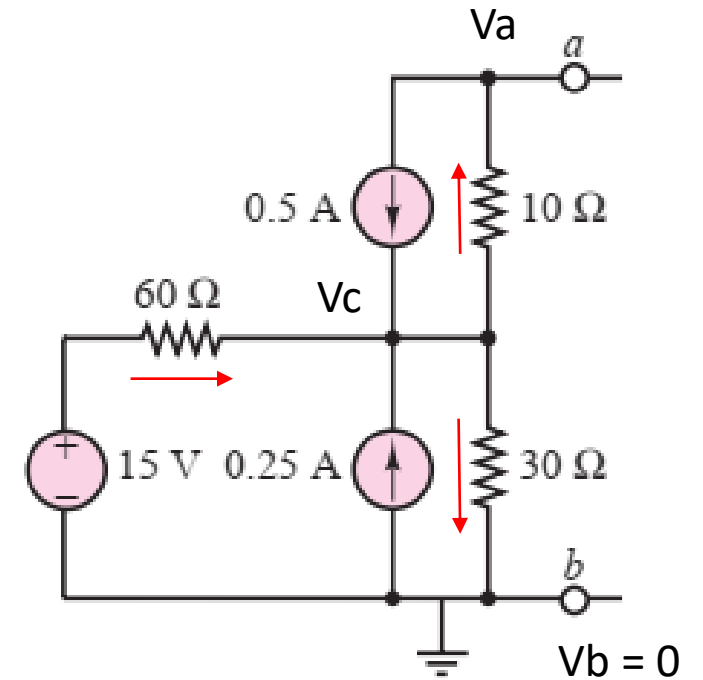


Thevenin equivalent circuit

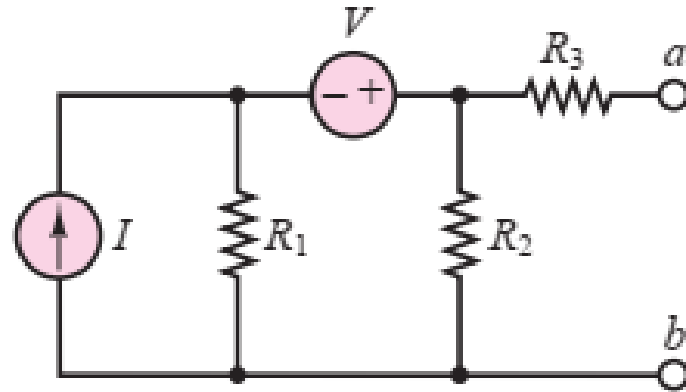4.

Determine the Norton current and the Norton equivalent for the circuit of Figure


$$V = 6 \text{ V}; I = 2 \text{ A}; R_1 = 6 \Omega; R_2 = 3 \Omega; R_3 = 2 \Omega.$$



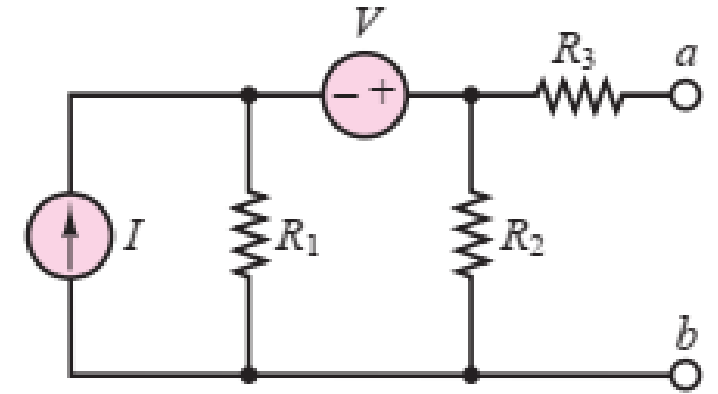
4.

Determine the Norton current and the Norton equivalent for the circuit of Figure

$$V = 6 \text{ V}; I = 2 \text{ A}; R_1 = 6 \Omega; R_2 = 3 \Omega; R_3 = 2 \Omega.$$


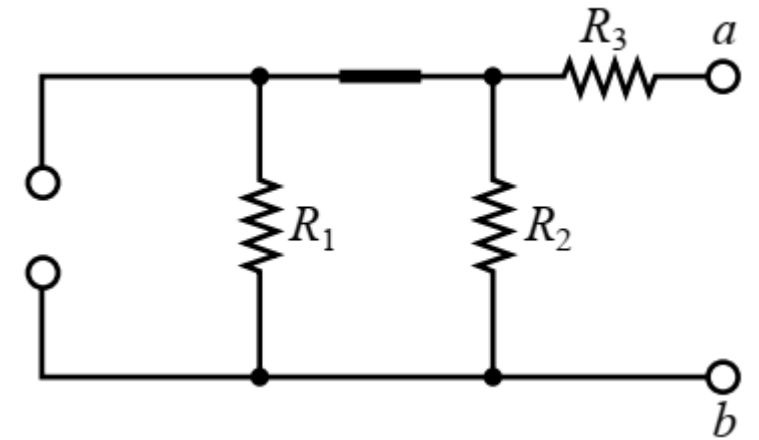
$$R_T = R_1 \parallel R_2 + R_3 = 6 \parallel 3 + 2 = 4 \Omega$$



4.

Determine the Norton current and the Norton equivalent for the circuit of Figure



$$V = 6 \text{ V}; I = 2 \text{ A}; R_1 = 6 \Omega; R_2 = 3 \Omega; R_3 = 2 \Omega.$$

$$\left\{ \begin{array}{ll} I - \frac{v_1}{R_1} - i = 0 & \text{node 1} \\ i - \frac{v_2}{R_2} - \frac{v_2}{R_3} = 0 & \text{node 2} \\ v_1 = v_2 - V \end{array} \right.$$

$$i = 2.5 \text{ A}$$

$$v_2 = 3 \text{ V.}$$
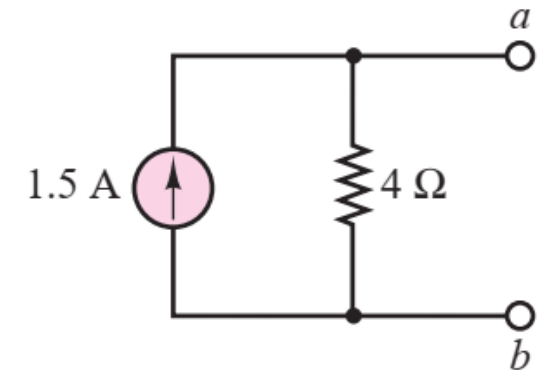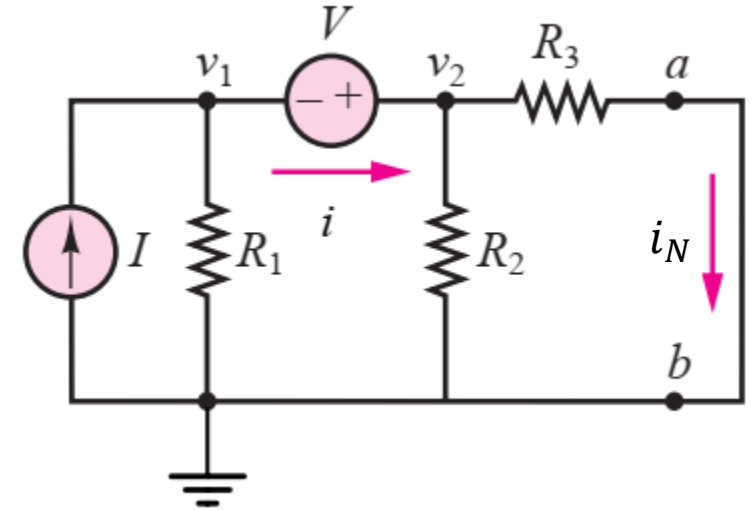
$$\text{Answer: } i_N = i \frac{\frac{1}{R_3}}{\frac{1}{R_2} + \frac{1}{R_3}} = 1.5 \text{ A}$$



Norton equivalent circuit