



Physics 2. Electrical Engineering  
Week 10 **Dynamic Circuits Analysis 2**

**INOPOLIS**  
UNIVERSITY

Igor Gaponov

Professor, Institute of Robotics and Computer Vision

# Objectives


The main objectives of today's lecture are:

- Review transient response of first-order circuits
- Study the transient response of second-order circuits
- Draw analogies between electrical and mechanical dynamic systems

# Transient Response of First-Order Circuits: Review
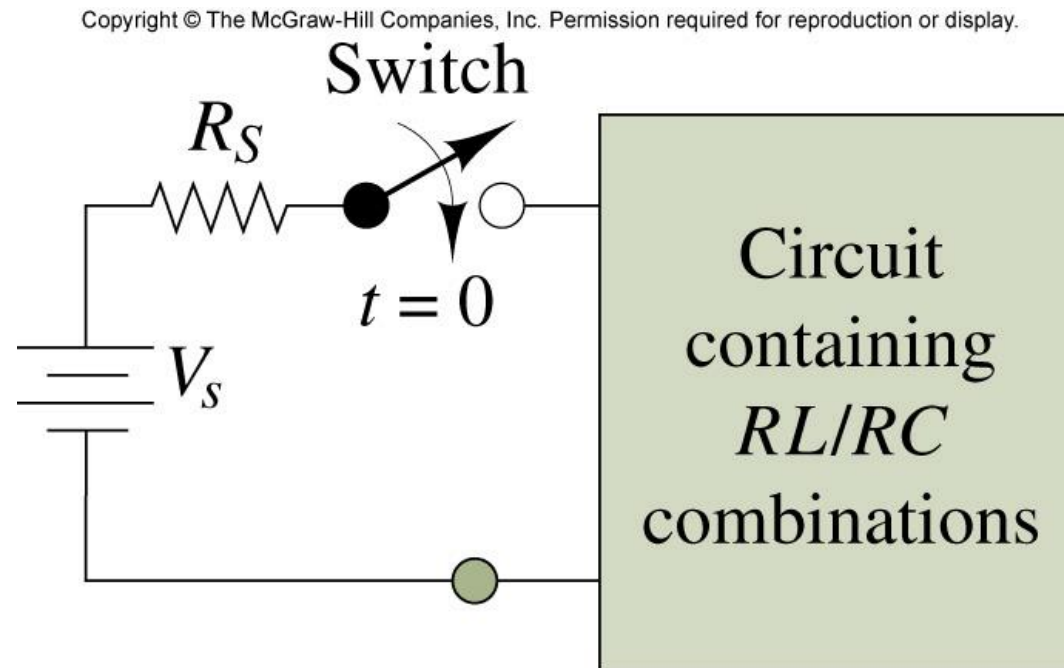
# Introduction to Transient Analysis

The object of transient analysis is to describe the behavior of a voltage or a current during the transition between two distinct steady-state conditions.



# Transient Analysis

The previous equation can be rewritten as

$$a_1 \frac{dx(t)}{dt} + a_0 x(t) = b_0 f(t)$$
$$\frac{a_1}{a_0} \frac{dx(t)}{dt} + x(t) = \frac{b_0}{a_0} f(t)$$

or

$$\tau \frac{dx(t)}{dt} + x(t) = K_S f(t)$$


The constants are

- $\tau$  - time constant
- $K_S$  - DC gain.

# Transient Response (1)

The transient response of a circuit consists of three parts:

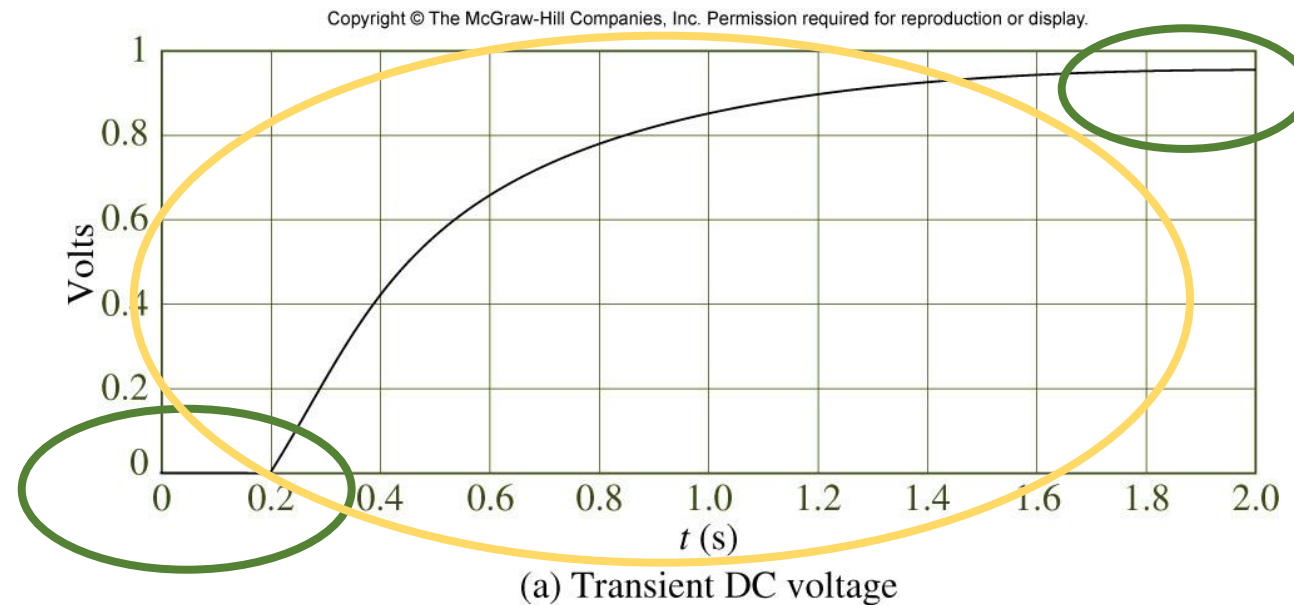1. The steady-state response prior to the transient.
2. The transient response.
3. The steady-state response after the end of the transient.



# Transient Response (3)

The steps to find a first-order transient response are:

1. Solve for the steady-state response  $x(0)$  of the circuit before the switch changes state ( $t = 0^-$ ) and after the transient has died out ( $x(\infty), t \rightarrow \infty$ ).
2. Identify the initial conditions for the circuit.
3. Write the differential equation of the circuit for  $t = 0^+$ .
4. Solve for the time constant of the circuit:  $\tau = RC$  or  $\tau = L/R$ .
5. Write the complete solution for the circuit in the form

$$x(t) = x(\infty) + [x(0) - x(\infty)]e^{-t/\tau}$$




# Transient Response: Example (1)

Determine an expression for the capacitor voltage in the circuit shown.

Given:  $v_C(t = 0^-) = 5 \text{ V}$ ,  $v_B = 12 \text{ V}$ .

- When the switch has been closed for a long time, the capacitor current becomes zero (capacitor = open circuit). Hence,

$$v_C(\infty) = V_B = 12 \text{ V}$$

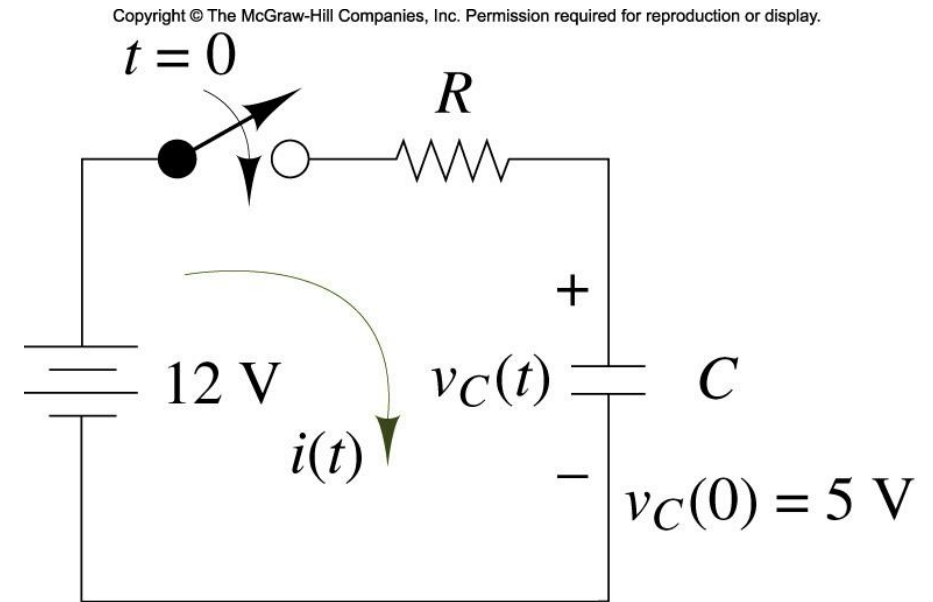



# Transient Response: Example (2)


Using KVL, we can write

$$V_B - Ri_C(t) - v_C(t) = V_B - RC \frac{dv_C(t)}{dt} - v_C(t) = 0$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = V_B, \quad t \geq 0$$

- Time constant is  $\tau = RC$
- Hence,
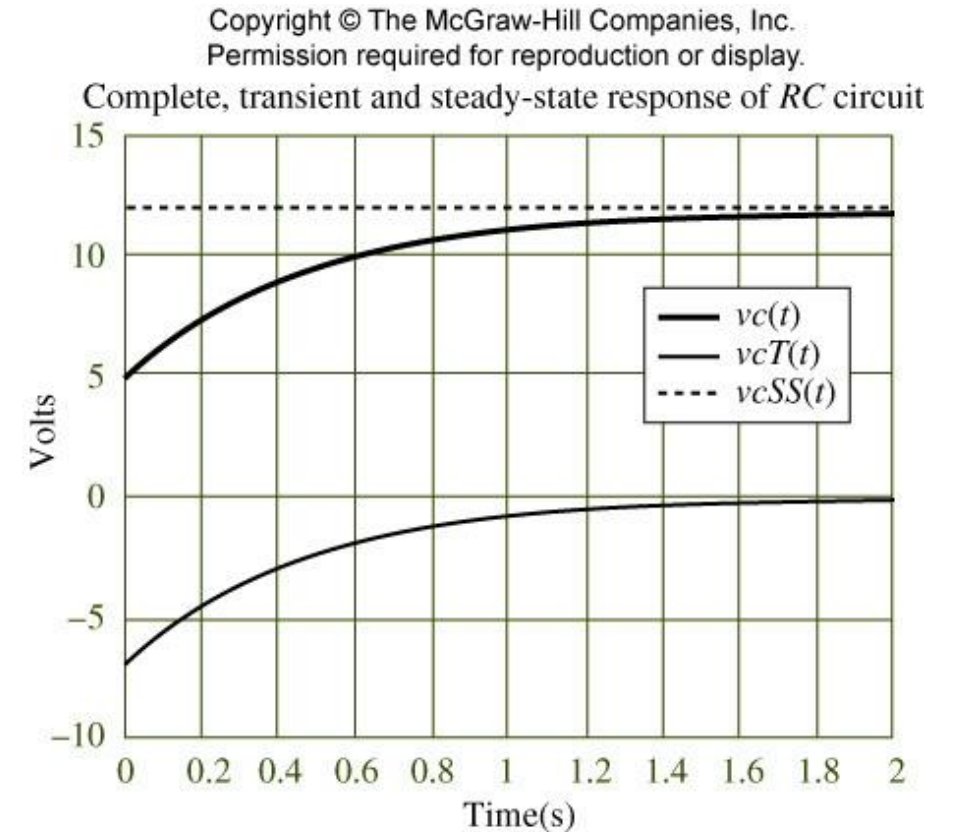
$$v_C(t) = v_C(\infty) + [v_C(0) - v_C(\infty)]e^{-t/\tau}$$





(a)


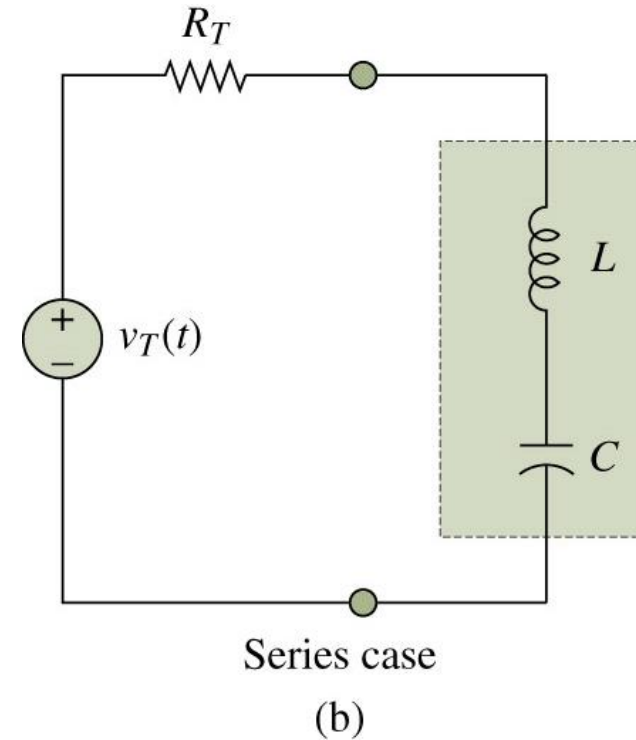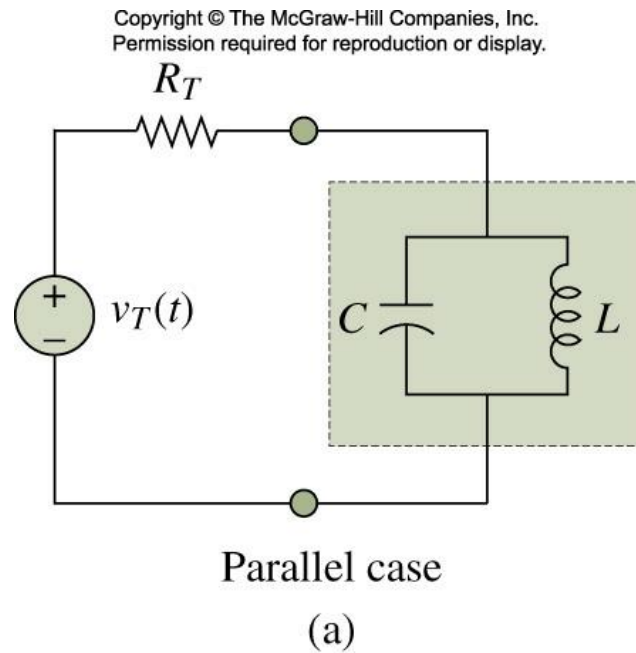
# Second-Order Circuits (1)

A simple second-order circuit is a circuit containing R-L-C elements.



# Second-Order Circuits: Parallel Case (1)

Let us consider the parallel case first.


- Starting with KVL around the left-hand loop,

$$v_T(t) - R_T i_S(t) - v_C(t) = 0$$

- Then apply KCL to the top node to obtain  $i_S(t) - i_C(t) - i_L(t) = 0$

- We know that  $v_C(t) = v_L(t)$

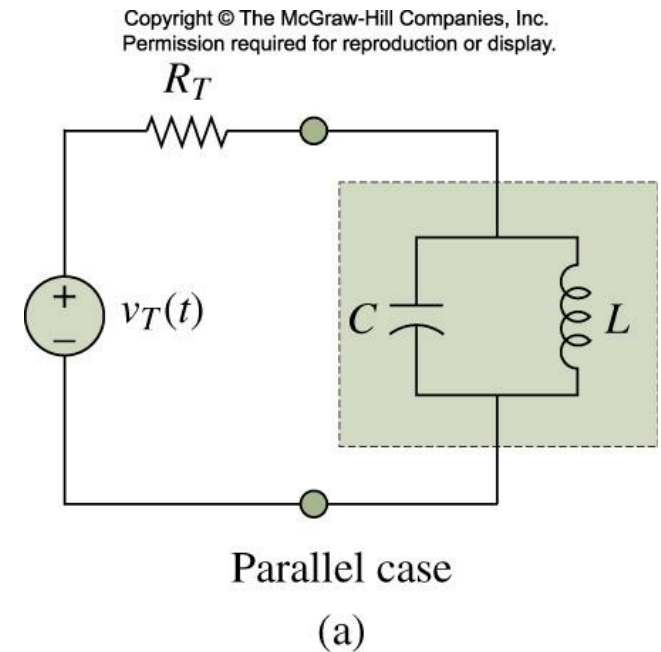- Hence
$$\frac{v_T(t) - v_C(t)}{R_T} - C \frac{dv_C(t)}{dt} - i_L(t) = 0,$$
$$v_C(t) = L \frac{di_L(t)}{dt}$$



# Second-Order Circuits: Parallel Case (2)

Finally, we obtain


$$\frac{1}{R_T} v_T(t) - \frac{L}{R_T} \frac{di_L(t)}{dt} = LC \frac{d^2 i_L(t)}{dt^2} + i_L(t)$$

or

$$LC \frac{d^2 i_L(t)}{dt^2} + \frac{L}{R_T} \frac{di_L(t)}{dt} + i_L(t) = \frac{1}{R_T} v_T(t)$$

- This equation can be written in the following form:
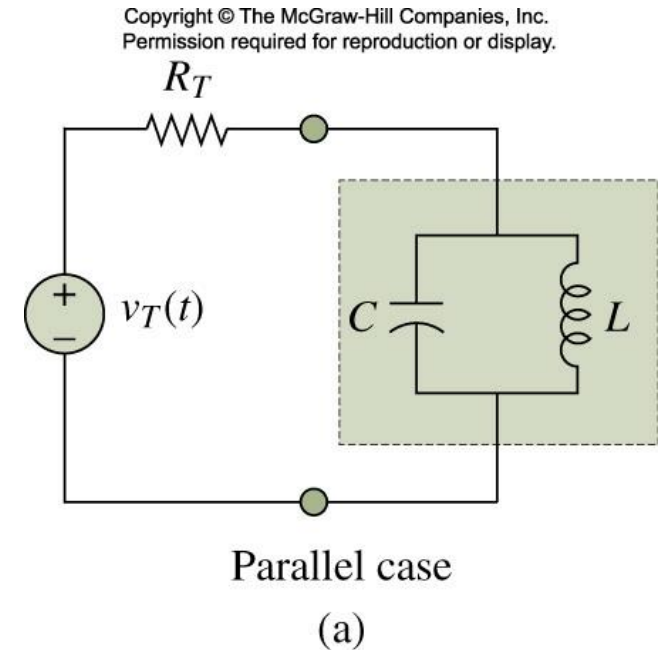
$$\frac{1}{\omega_n^2} \frac{d^2 x(t)}{dt^2} + \frac{2\zeta}{\omega_n} \frac{dx(t)}{dt} + x(t) = K_S f(t)$$




# Second-Order Circuits (2)

The equations of this type are called second-order linear ordinary differential equations

$$\frac{1}{\omega_n^2} \frac{d^2 x(t)}{dt^2} + \frac{2\zeta}{\omega_n} \frac{dx(t)}{dt} + x(t) = K_S f(t)$$

The parameters are:

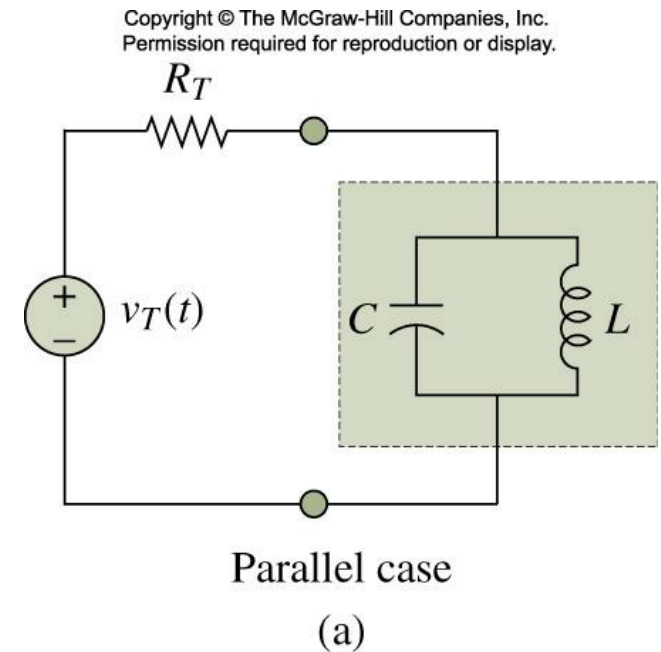- $\omega_n$  – the natural frequency
- $\zeta$  – the damping ratio
- $K_S$  – DC gain.



# Second-Order Circuits: Series Case

Now, let us derive the equations for the series RLC circuit.

- Starting with KVL around the loop,


$$v_T - R_T i_L - v_C - v_L = 0$$

- Recalling the equations for capacitor and inductor,

$$v_T - R_T i_L - v_C - L \frac{di_L}{dt} = 0, \quad i_L = i_C = C \frac{dv_C}{dt}$$

- Hence, writing for  $v_C$  yields
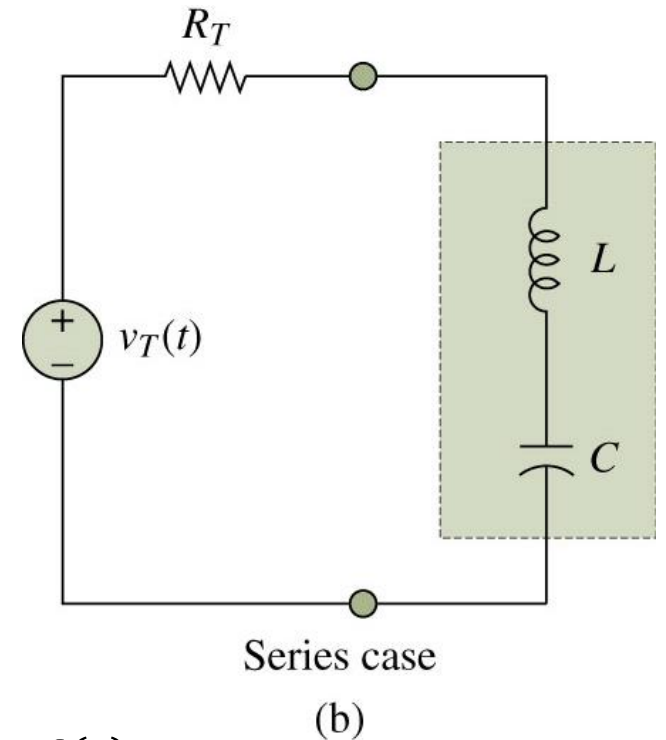
$$LC \frac{d^2 v_C}{dt^2} + R_T C \frac{dv_C}{dt} + v_C = v_T \rightarrow \frac{1}{\omega_n^2} \frac{d^2 x(t)}{dt^2} + \frac{2\zeta}{\omega_n} \frac{dx(t)}{dt} + x(t) = K_S f(t)$$






# Second-Order Circuits (3)

A typical response of switched second-order system is shown here for different values of  $\zeta$ .

We immediately note three important characteristics of the response:

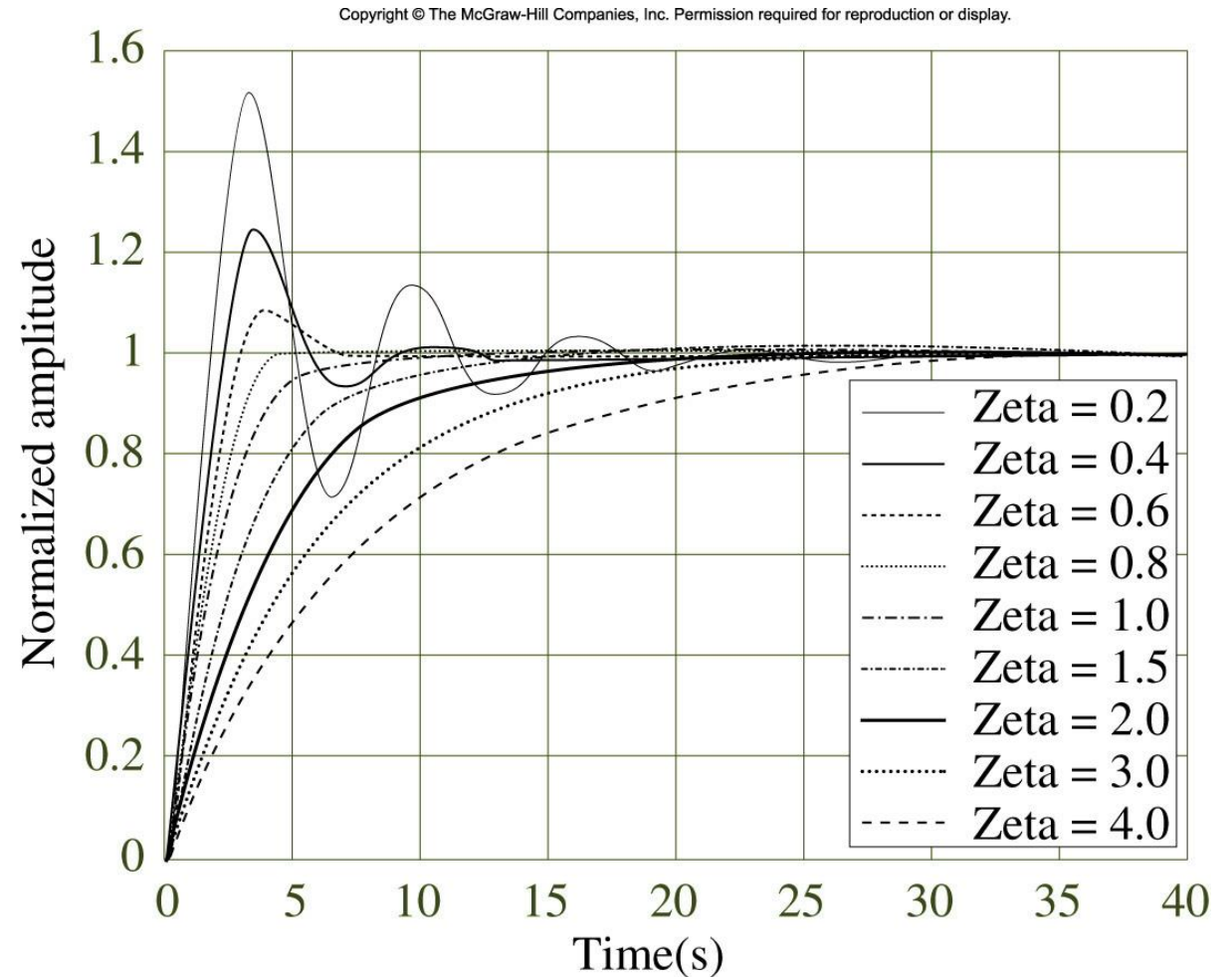1. The response asymptotically tends to a constant value.
2. The response oscillates.
3. The oscillations decay (and eventually disappear) as time progresses.



# Second-Order Circuits: Natural Response

The natural response is found by setting the excitation equal to zero.

$$\frac{1}{\omega_n^2} \frac{d^2 x(t)}{dt^2} + \frac{2\zeta}{\omega_n} \frac{dx(t)}{dt} + x(t) = K_S f(t)$$

- Thus, we solve the equation

$$\frac{1}{\omega_n^2} \frac{d^2 x_N(t)}{dt^2} + \frac{2\zeta}{\omega_n} \frac{dx_N(t)}{dt} + x_N(t) = 0$$

- The solution is known to be of exponential form:  $x_N(t) = \alpha e^{st}$
- Substituting into the initial equation yields

$$\frac{1}{\omega_n^2} s^2 \alpha e^{st} + \frac{2\zeta}{\omega_n} s \alpha e^{st} + \alpha e^{st} = 0 \rightarrow \frac{s^2}{\omega_n^2} + \frac{2\zeta}{\omega_n} s + 1 = 0$$

# Second-Order Circuits: Natural Response

This polynomial in the variable  $s$  is called the characteristic polynomial of the differential equation, and it gives rise to two characteristic roots,  $s_1$  and  $s_2$ .

$$\frac{s^2}{\omega_n^2} + \frac{2\zeta}{\omega_n}s + 1 = 0$$

$$x_N(t) = \alpha_1 e^{s_1 t} + \alpha_2 e^{s_2 t}$$


$$s_{1,2} = -\zeta\omega_n \pm \omega_n\sqrt{\zeta^2 - 1}$$

For the roots of second-order systems, three cases exist:

1. Real and distinct roots ( $\zeta > 1$ ). This leads to an overdamped response  
 $s_{1,2} = -\zeta\omega_n \pm \omega_n\sqrt{\zeta^2 - 1}$
2. Real and repeated roots ( $\zeta = 1$ ) - critically damped response  
 $s_{1,2} = -\zeta\omega_n = -\omega_n$
3. Complex conjugate roots ( $0 < \zeta < 1$ ) - underdamped response  
 $s_{1,2} = -\zeta\omega_n \pm j\omega_n\sqrt{1 - \zeta^2}$

# Second-Order Circuits: Overdamped

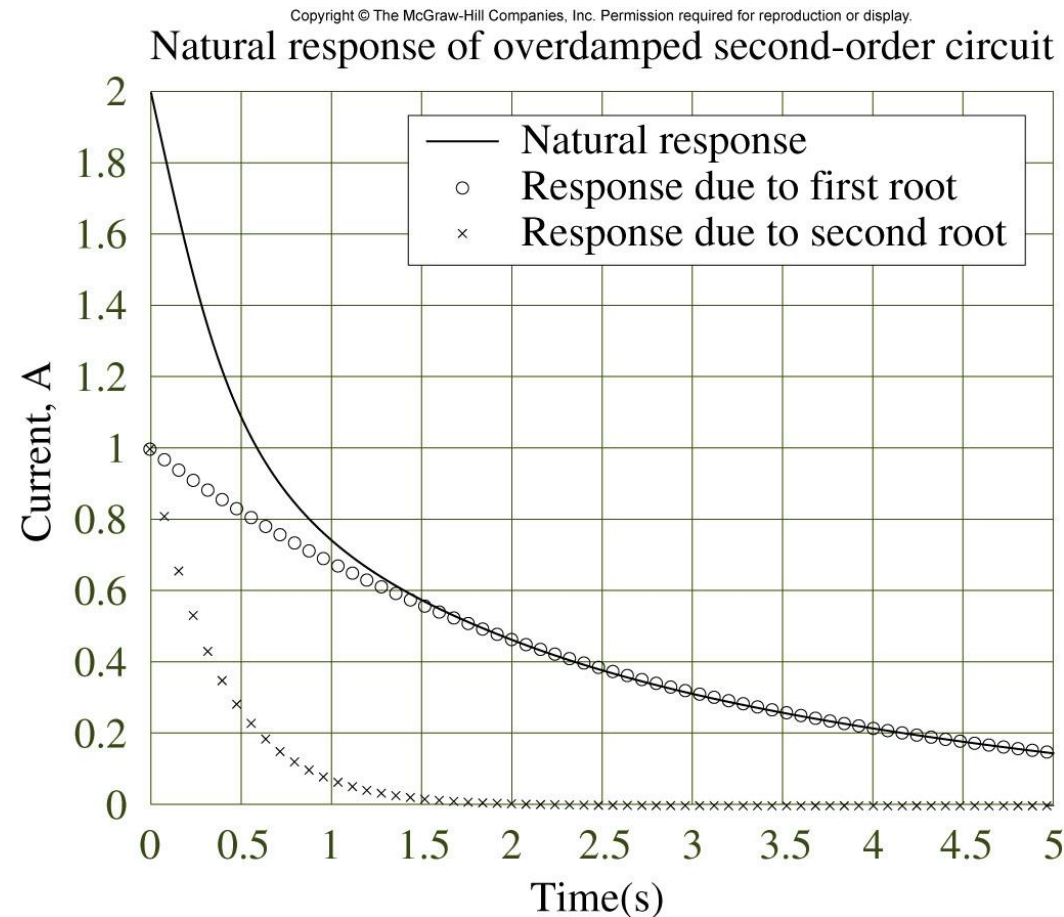1. Real and distinct roots ( $\zeta > 1$ ) - overdamped response




$$s_{1,2} = -\zeta\omega_n \pm \omega_n\sqrt{\zeta^2 - 1}$$

$$x_N(t) = \alpha_1 e^{s_1 t} + \alpha_2 e^{s_2 t}$$

# Second-Order Circuits: Critically Damped

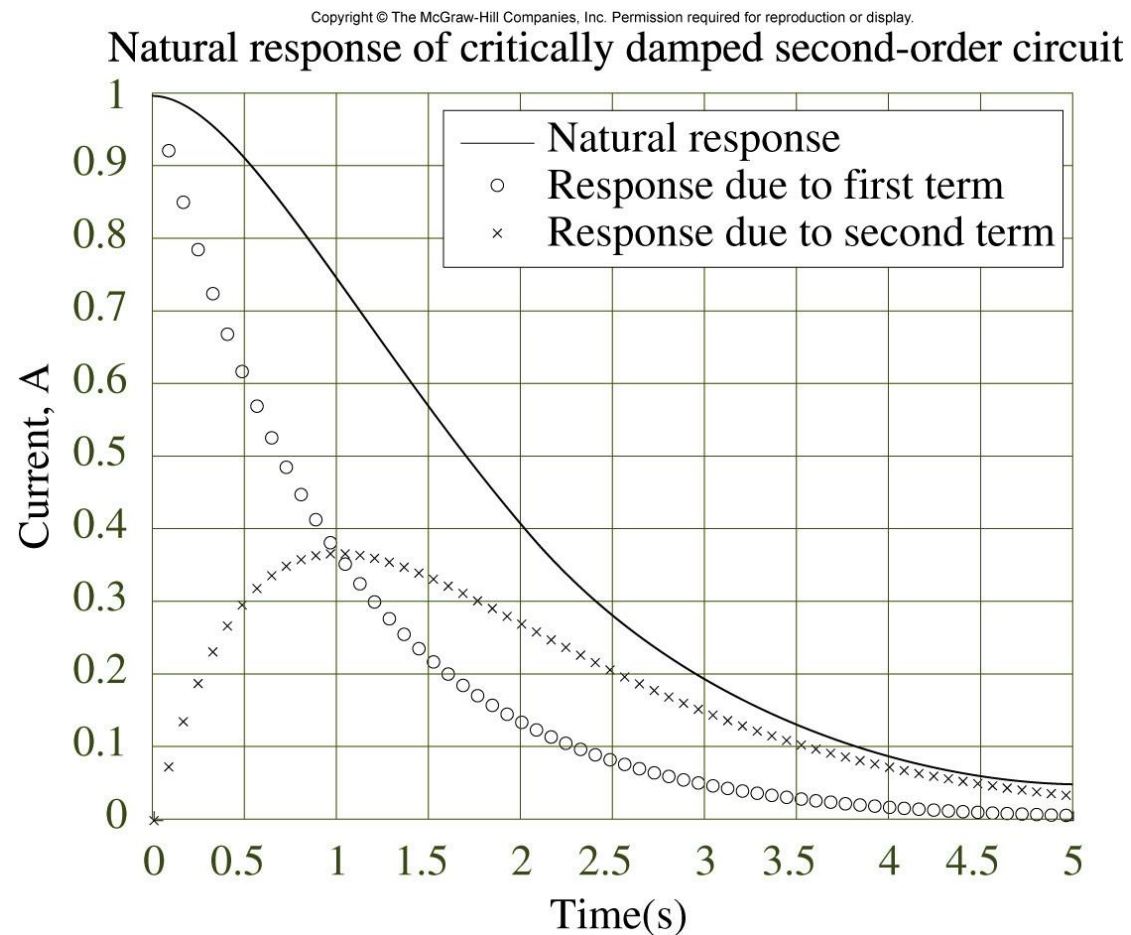2. Real and repeated roots ( $\zeta = 1$ ) - critically damped response




$$s_{1,2} = -\zeta\omega_n = -\omega_n$$

$$x_N(t) = \alpha_1 e^{s_1 t} + \alpha_2 e^{s_2 t}$$

# Second-Order Circuits: Underdamped

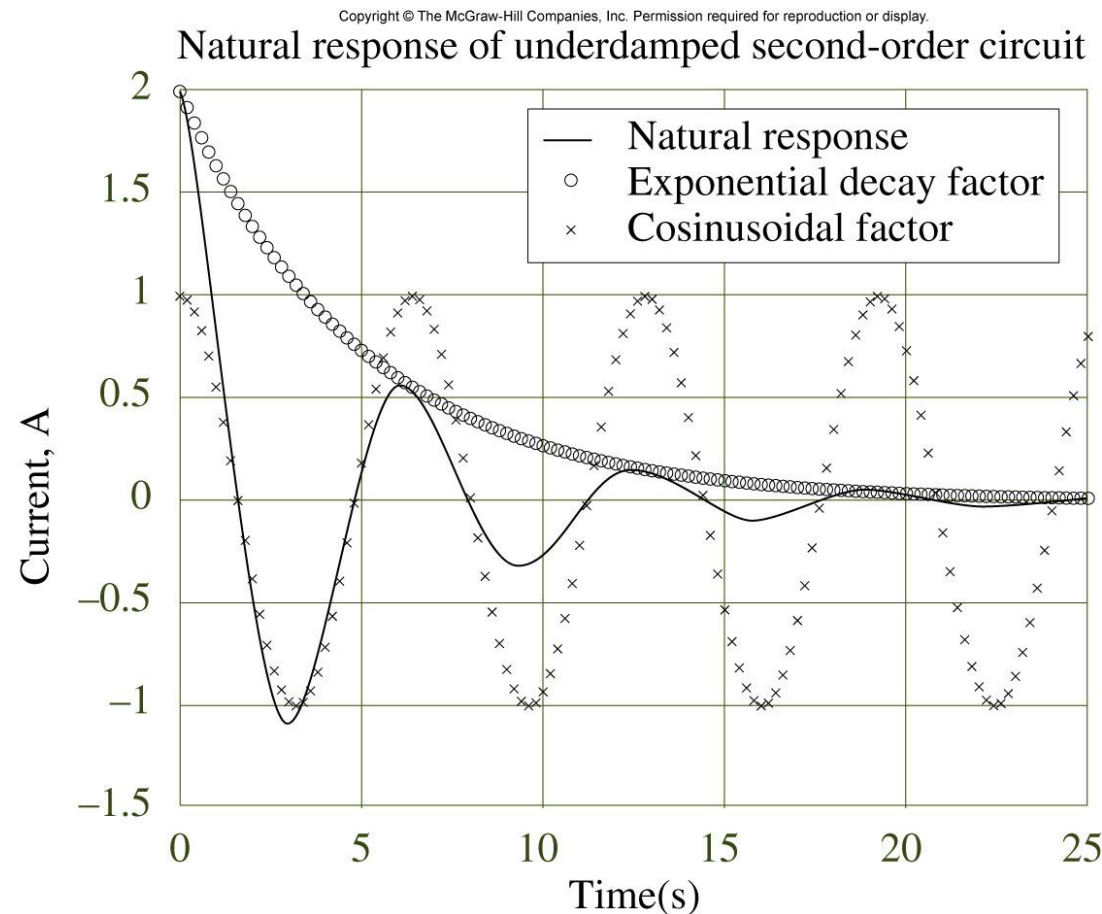3. Complex conjugate roots ( $0 < \zeta < 1$ ) - underdamped response



$$s_{1,2} = -\zeta\omega_n \pm j\omega_n\sqrt{1-\zeta^2}$$

$$x_N(t) = \alpha_1 e^{s_1 t} + \alpha_2 e^{s_2 t}$$

# Second-Order Circuits: Complete Response

The forced response is the solution of the equation

$$\frac{1}{\omega_n^2} \frac{d^2 x(t)}{dt^2} + \frac{2\zeta}{\omega_n} \frac{dx(t)}{dt} + x(t) = K_S f(t)$$

After the transient settles,

$$x_F(t) = K_S f(t)$$


- The complete response is then

$$x(t) = x_N(t) + x_F(t)$$



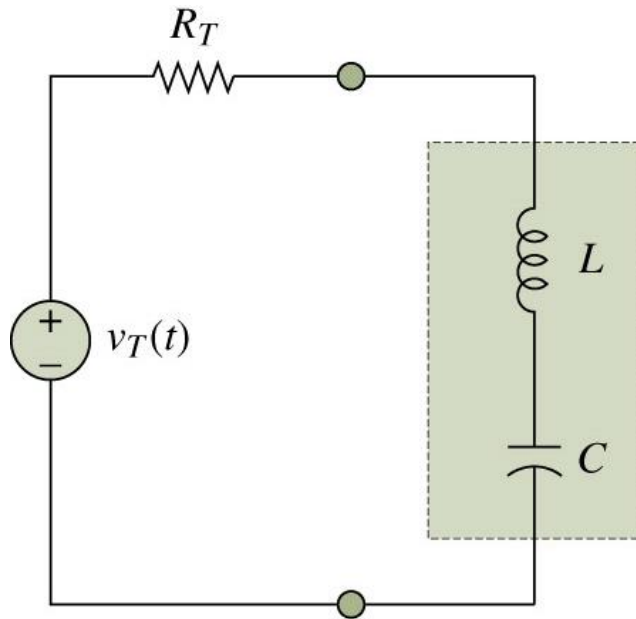
# Second-Order Systems: Analogies (1)

Now, let us compare two systems: electrical and mechanical


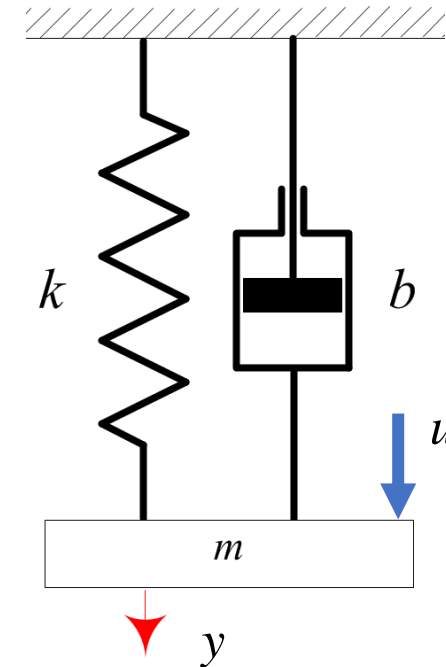
$$L \frac{d^2 v_C}{dt^2} + R_T \frac{dv_C}{dt} + \frac{1}{C} v_C = \frac{1}{C} v_T$$



$$m \frac{d^2 y}{dt^2} + b \frac{dy}{dt} + ky = u$$

# Second-Order Systems: Analogies (2)

Upon comparing the equations, one can readily identify the analogies between the electrical and mechanical worlds:

Electrical System	Mechanical System
Inductance $L$	Mass $m$
Resistance $R$	Damping coeff. $b$
Capacitance $C$	Compliance $1/k$

$$L \frac{d^2 v_C}{dt^2} + R_T \frac{dv_C}{dt} + \frac{1}{C} v_C = \frac{1}{C} v_T$$

$$m \frac{d^2 y}{dt^2} + b \frac{dy}{dt} + ky = u$$


# Second-Order Systems: Oscillations

Lastly, let us return to an RLC circuit we have started with. Recall the corresponding differential equations:

$$LC \frac{d^2 v_C}{dt^2} + R_T C \frac{dv_C}{dt} + v_C = v_T$$
$$\rightarrow \frac{1}{\omega_n^2} \frac{d^2 x(t)}{dt^2} + \frac{2\zeta}{\omega_n} \frac{dx(t)}{dt} + x(t) = K_S f(t)$$

Q: Given that  $\zeta = 0$  creates a purely oscillatory response,

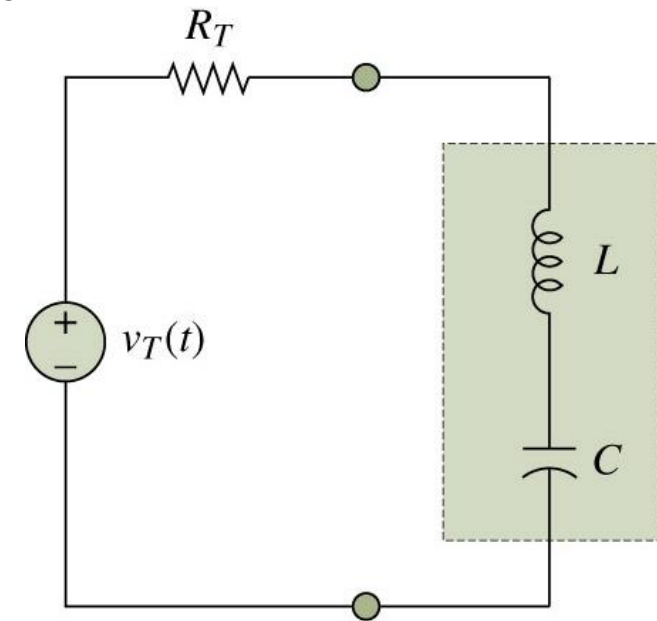- how to turn this circuit into an oscillator?





Thank you for your attention!

innopolis  
UNIVERSITY

Igor Gaponov

[i.gaponov@innopolis.ru](mailto:i.gaponov@innopolis.ru)