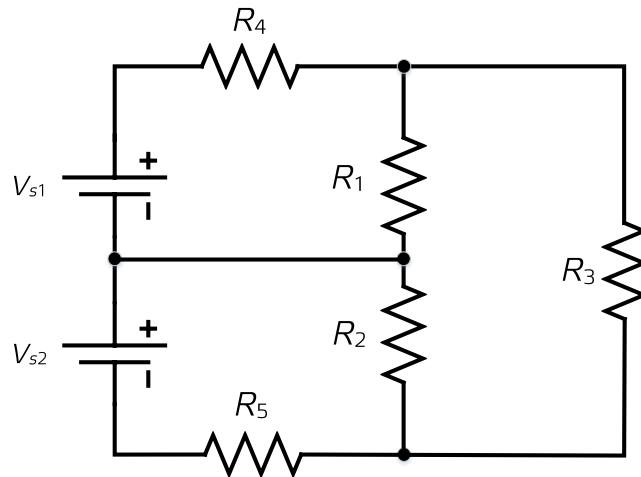


Homework Assignment 2 – Network Analysis

Problem 1 (25 pts) – Node Voltage Method


Use node voltage method to **determine the voltage on R_3** . The known quantities are:

$V_{S1} = V_{S2} = 450 \text{ V}$, $R_4 = R_5 = 0.25 \Omega$, $R_1 = 8 \Omega$, $R_2 = 5 \Omega$, $R_3 = 32 \Omega$.



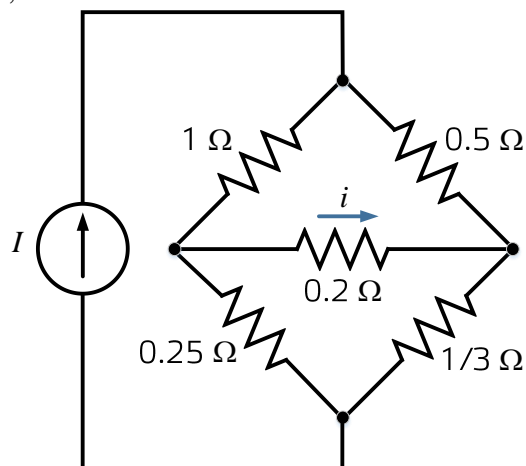
Problem 2 (25 pts) – Mesh Current Method

Using mesh current method, **find the current i** in the circuit shown below.



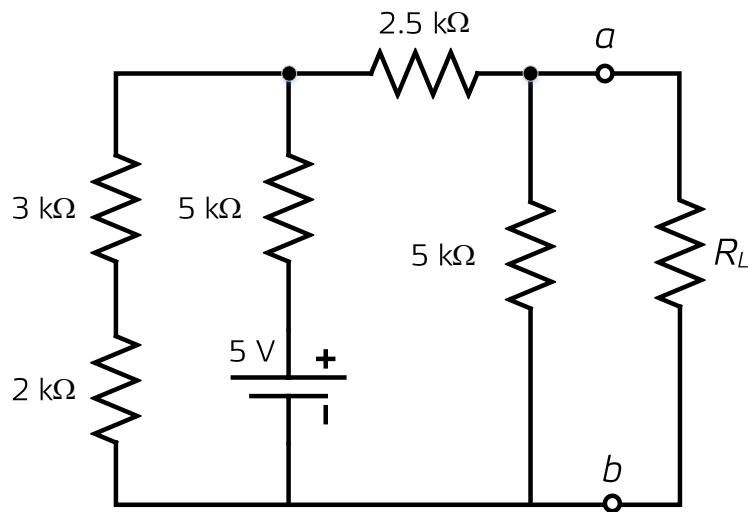Problem 3 (25 points) – Thevenin Circuits

Find the Thevenin equivalent circuit for the network shown below, as seen by the load resistor R_L .



Problem 4 (25 points) – Norton Circuit

Find the Norton equivalent circuit for the network shown below, as seen by the load resistor R_L .

