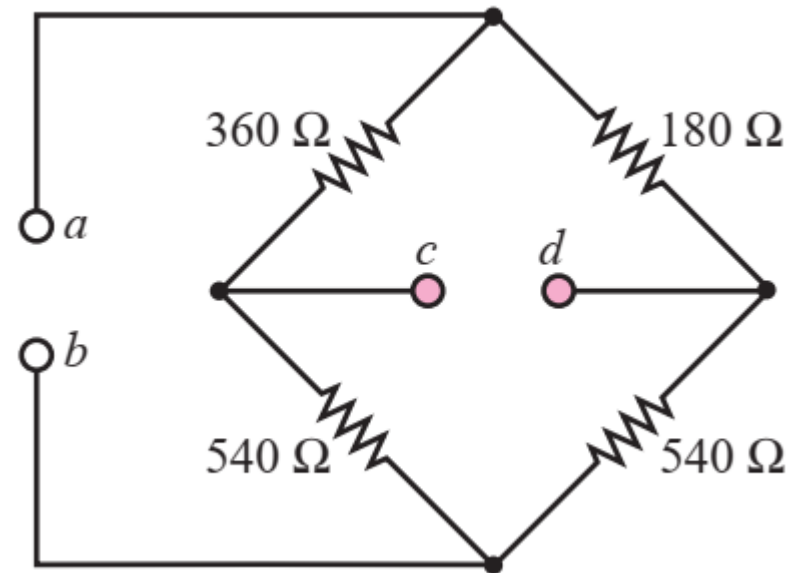


1.


Find the equivalent resistance looking in at terminals a and b if terminals c and d are open and again if terminals c and d are shorted together. Also, find the equivalent resistance looking in at terminals c and d if terminals a and b are open and if terminals a and b are shorted together.



1.

$$R_{\text{eq}} = \left(\frac{1}{360 + 540} + \frac{1}{180 + 540} \right)^{-1} = 400 \ \Omega$$


Terminals (c – d) open

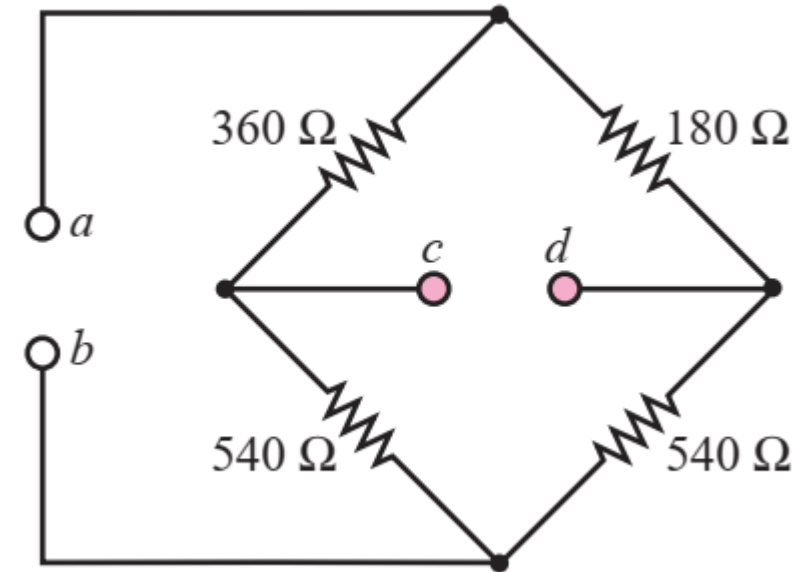

1.

$$R_{\text{eq}} = \left(\frac{1}{360} + \frac{1}{180} \right)^{-1} + \left(\frac{1}{540} + \frac{1}{540} \right)^{-1} = 390 \ \Omega$$


Terminals (c – d) shorted

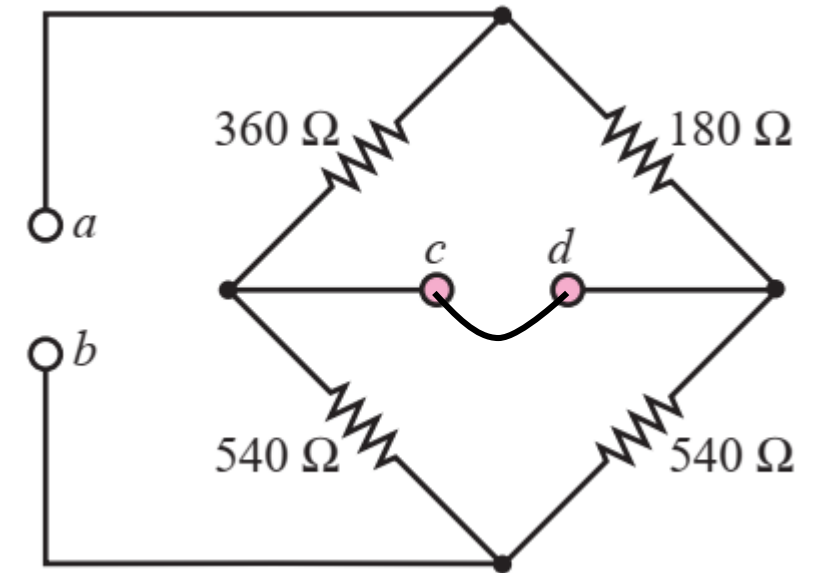

1.

$$R_{\text{eq}} = \left(\frac{1}{540 + 540} + \frac{1}{360 + 180} \right)^{-1} = 360 \text{ } \Omega$$


terminals (a – b) open

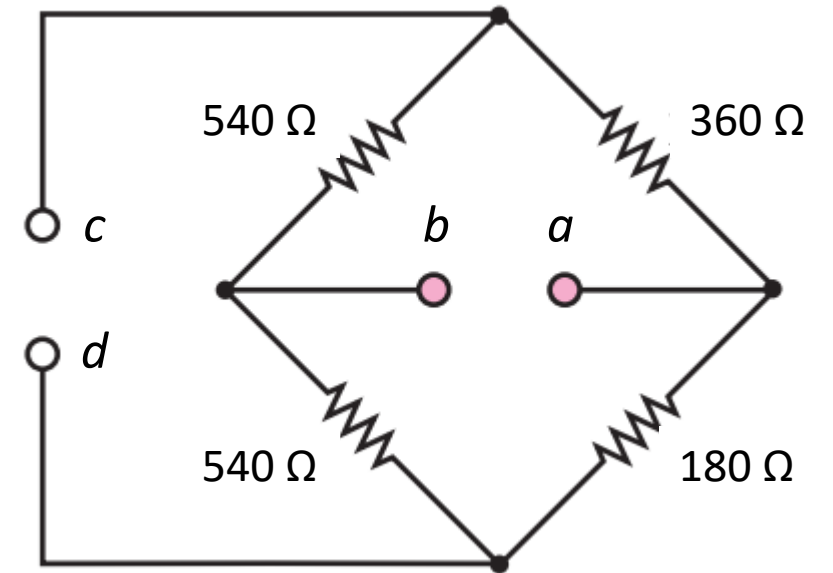

1.

$$R_{\text{eq}} = \left(\frac{1}{540} + \frac{1}{360} \right)^{-1} + \left(\frac{1}{540} + \frac{1}{180} \right)^{-1} = 351 \ \Omega$$

Terminals (a – b) shorted

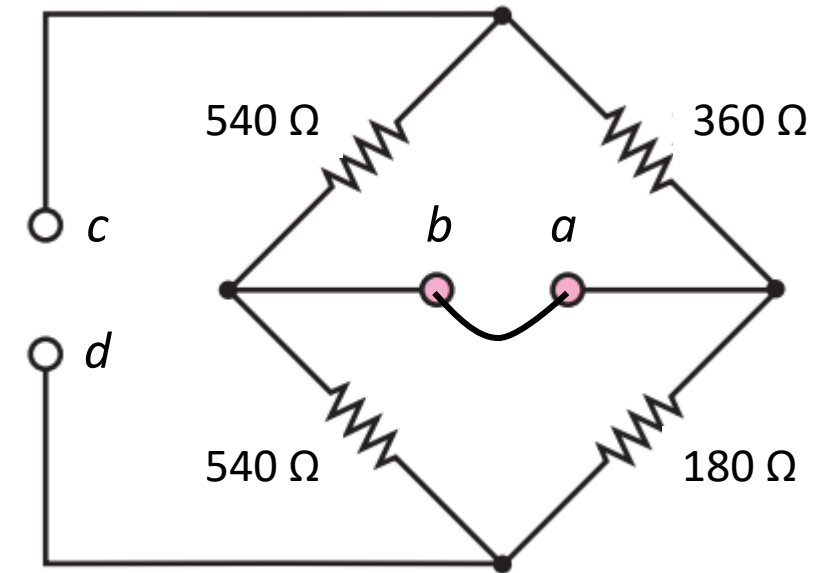

2.

Determine the voltage between nodes A and B in the circuit


$$V_S = 12 \text{ V}$$

$$R_1 = 11 \text{ k}\Omega$$

$$R_3 = 6.8 \text{ k}\Omega$$

$$R_2 = 220 \text{ k}\Omega$$

$$R_4 = 0.22 \text{ M}\Omega$$

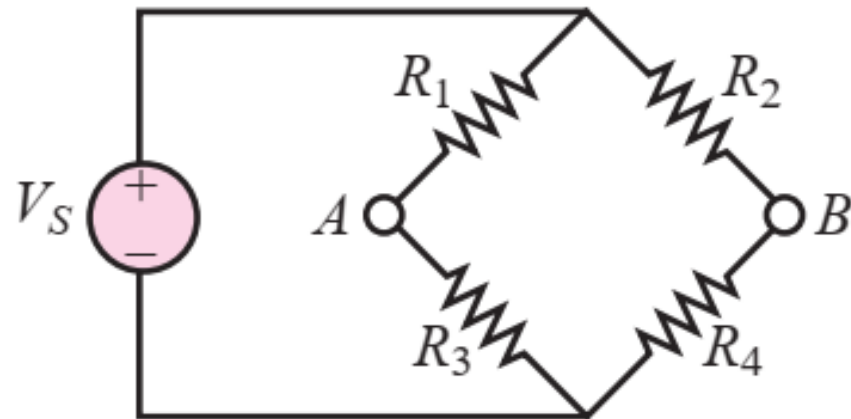

2.

Determine the voltage between nodes *A* and *B* in the circuit

$$V_3 := V_S \cdot \frac{R_3}{R_1 + R_3} = 4.58 \text{ V}$$

$$V_4 := V_S \cdot \frac{R_4}{R_2 + R_4} = 6 \text{ V}$$

Answer: $V_3 - V_4 = -1.41 \text{ V}$


$$V_S = 12 \text{ V}$$

$$R_1 = 11 \text{ k}\Omega$$

$$R_3 = 6.8 \text{ k}\Omega$$

$$R_2 = 220 \text{ k}\Omega$$


$$R_4 = 0.22 \text{ M}\Omega$$

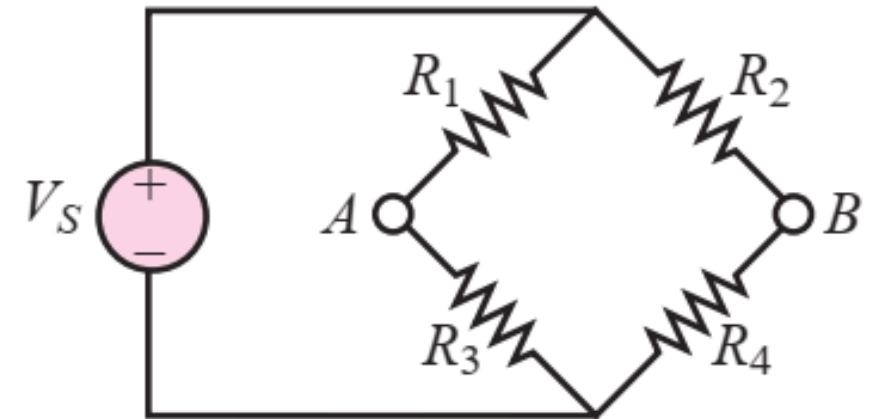

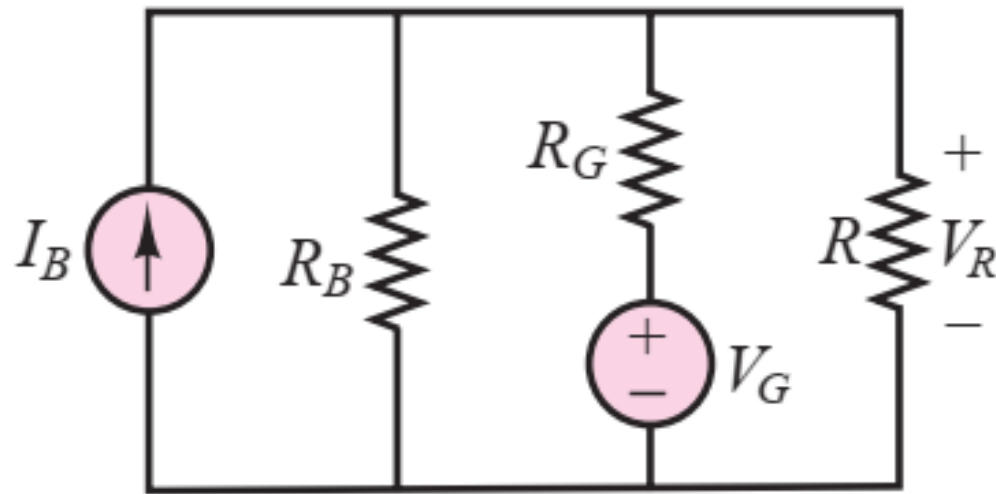3.

Determine the voltage across resistor R in the circuit

$$I_B = 12 \text{ A}; V_G = 12 \text{ V}; R_B = 1 \Omega; R_G = 0.3 \Omega; R = 0.23 \Omega$$




3.

$$I_B = 12 \text{ A}; V_G = 12 \text{ V}; R_B = 1 \Omega; R_G = 0.3 \Omega; R = 0.23 \Omega$$


$$-I_B + \frac{V_{R-I}}{R_B} + \frac{V_{R-I}}{R_G} + \frac{V_{R-I}}{R} = 0$$
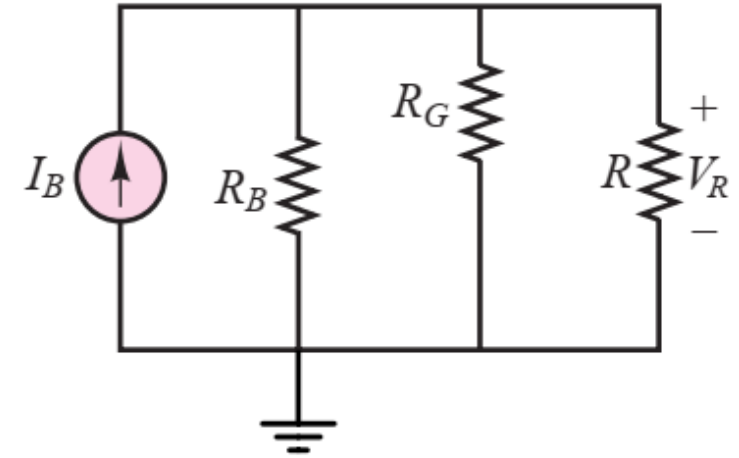
$$V_{R-I} = \frac{I_B}{1/R_B + 1/R_G + 1/R} = \frac{12}{1/1 + 1/0.3 + 1/0.23} = 1.38 \text{ V}$$



$$\frac{V_{R-V}}{R_B} + \frac{V_{R-V} - V_G}{R_G} + \frac{V_{R-V}}{R} = 0$$
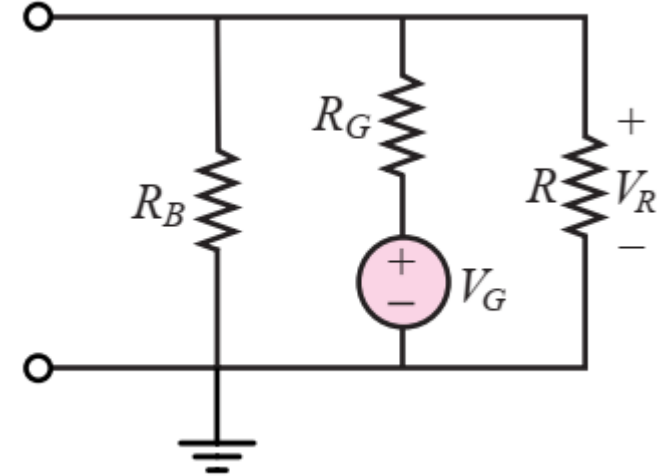
$$V_{R-V} = \frac{V_G/R_G}{1/R_B + 1/R_G + 1/R} = \frac{12/0.3}{1/1 + 1/0.3 + 1/0.23} = 4.61 \text{ V}$$



Answer: $V_R = V_{R-I} + V_{R-V} = 5.99 \text{ V}$


4.

Find the mesh currents in the circuit using superposition

$$V_1 = 10 \text{ V}; V_2 = 9 \text{ V}; V_3 = 1 \text{ V};$$

$$R_1 = 5 \, \Omega; R_2 = 10 \, \Omega; R_3 = 5 \, \Omega;$$

$$R_4 = 5 \, \Omega.$$

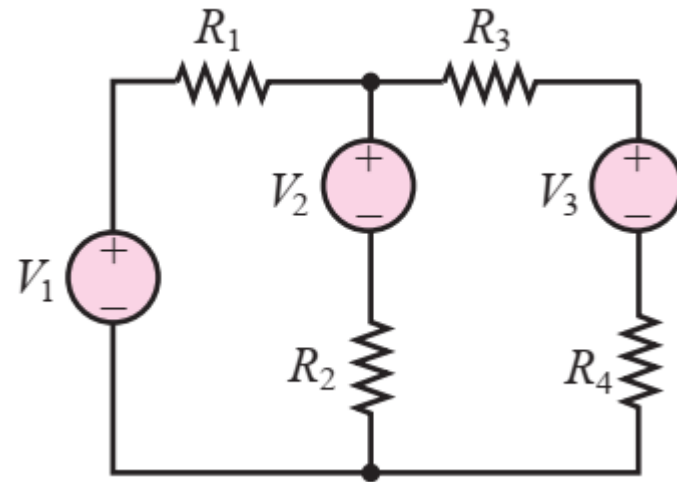


4.

Find the mesh currents in the circuit using superposition

$$V_1 = 10 \text{ V}; V_2 = 9 \text{ V}; V_3 = 1 \text{ V};$$

$$R_1 = 5 \Omega; R_2 = 10 \Omega; R_3 = 5 \Omega;$$


$$R_4 = 5 \Omega.$$

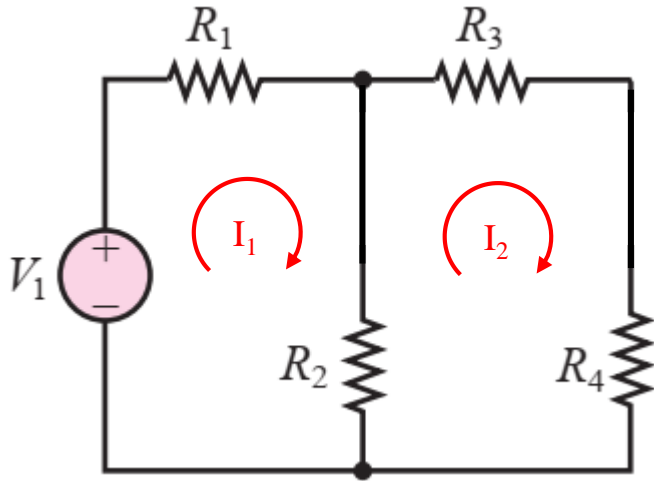

$$\begin{cases} V_1 - R_1 \cdot I_1 - R_2(I_1 - I_2) = 0 \\ R_2 \cdot (I_2 - I_1) + R_3 \cdot I_2 + R_4 \cdot I_2 = 0 \end{cases}$$

$$I_1 = 1 \text{ A}$$


$$I_2 = 0.5 \text{ A}$$

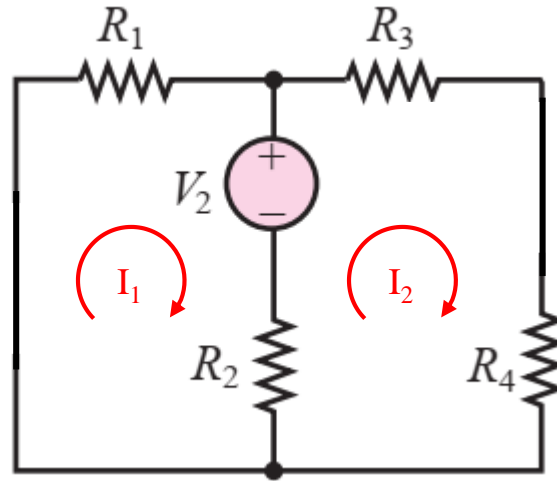

$$\begin{cases} -R_1 \cdot I_1 - V_2 - R_2 \cdot (I_1 - I_2) = 0 \\ -R_2 \cdot (I_2 - I_1) + V_2 - R_3 \cdot I_2 - R_4 \cdot I_2 = 0 \end{cases}$$

$$I_1 = -0.45 \text{ A}$$

$$I_2 = 0.225 \text{ A}$$

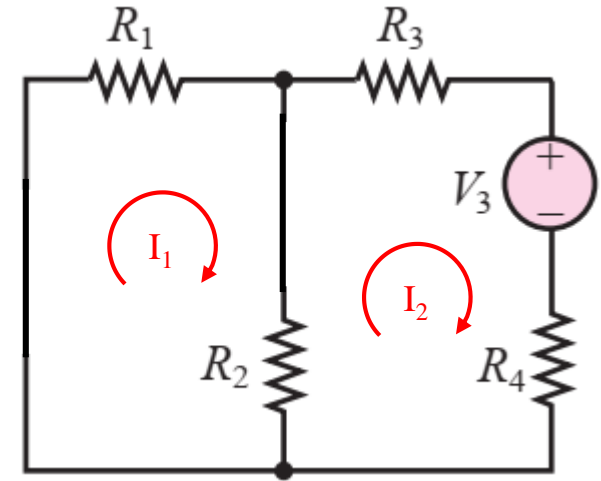

$$\begin{cases} R_1 \cdot I_1 + R_2 \cdot (I_1 - I_2) = 0 \\ -R_2 \cdot (I_2 - I_1) - R_3 \cdot I_2 - V_3 - R_4 \cdot I_2 = 0 \end{cases}$$

$$I_1 = -0.05 \text{ A}$$

$$I_2 = -0.075 \text{ A}$$

Answer: $I_{1\text{tot}} = 1 - 0.45 - 0.05 = 0.5 \text{ A}$

$$I_{2\text{tot}} = 0.5 + 0.225 - 0.075 = 0.65 \text{ A}$$


5.

Using superposition, determine the component of the current through R_3 that is due to V_{S2} .

$$V_{S1} = V_{S2} = 450 \text{ V}$$

$$R_1 = 7 \, \Omega \quad R_2 = 5 \, \Omega$$
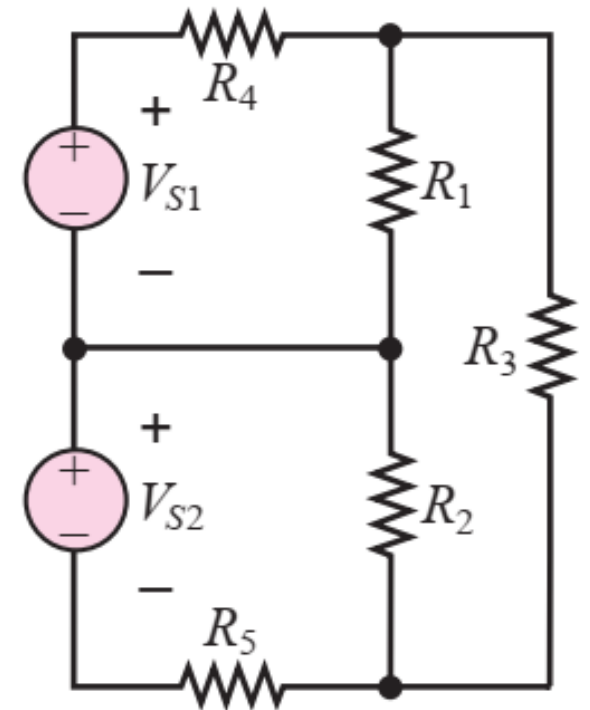
$$R_3 = 10 \, \Omega \quad R_4 = R_5 = 1 \, \Omega$$



5.

Using superposition, determine the component of the current through R_3 that is due to V_{S2} .

$$R_{41} := \left(\frac{1}{R_4} + \frac{1}{R_1} \right)^{-1} = 0.875 \text{ } \Omega$$

$$\begin{cases} V_{S2} - (I_1 - I_2) \cdot R_2 - I_1 \cdot R_5 = 0 \\ R_{41} \cdot I_2 + R_3 \cdot I_2 + (I_2 - I_1) \cdot R_2 = 0 \end{cases}$$

Answer:

$$I_1 = 101.7 \text{ A}$$

$$I_2 = 32.0 \text{ A}$$

$$V_{S1} = V_{S2} = 450 \text{ V}$$

$$R_1 = 7 \text{ } \Omega \quad R_2 = 5 \text{ } \Omega$$

$$R_3 = 10 \text{ } \Omega \quad R_4 = R_5 = 1 \text{ } \Omega$$

